

## 8 Function diagrams

### Basic functions

	Page
Sheet 1 Overview .....	8-4
<b>Inputs and outputs</b>	
Sheet 2 Binary inputs, terminals 36 to 39 .....	8-5
Sheet 3 Binary inputs, terminals 40 to 43 .....	8-6
Sheet 4 Binary outputs, terminals 46/47 and 48/54 .....	8-7
Sheet 4 Binary outputs, terminals 50/51 and 52/53 .....	8-7
Sheet 5 Analog inputs, terminals 4/5, 6/7 and 103/104 .....	8-8
Sheet 6 Analog inputs, terminals 8/9 and 10/11 .....	8-9
Sheet 7 Analog outputs, terminals 14/15 and 16/17 .....	8-10
Sheet 8 Analog outputs, terminals 18/19 and 20/21 .....	8-11
<b>Setpoint generation</b>	
Sheet 9 Fixed values .....	8-12
Sheet 9 Fixed control bits .....	8-12
Sheet 9 Constant fixed values and control bits .....	8-12
Sheet 9 Connector and binector displays .....	8-12
Sheet 10 Motorized potentiometer .....	8-13
Sheet 11 Fixed setpoint .....	8-14
Sheet 12 Forcing, oscillation .....	8-15
Sheet 13 Inching setpoint .....	8-16
Sheet 14 Crawling setpoint .....	8-17
Sheet 15 Setpoint processing .....	8-18
Sheet 16 Ramp-function generator .....	8-19
<b>Actual speed value</b>	
Sheet 17 Pulse generator evaluation .....	8-20
<b>Controllers</b>	
Sheet 18 Speed controller .....	8-21
Sheet 19 Friction compensation .....	8-22
Sheet 19 Compensation of moment of inertia (dv/dt injection) .....	8-22
Sheet 20 Torque limitation .....	8-23
Sheet 21 Current limitation .....	8-24
Sheet 22 Closed-loop armature current control, auto-reversing stage, armature gating unit .....	8-25
Sheet 23 Closed-loop EMF control .....	8-26
Sheet 24 Closed-loop field current control, field gating unit .....	8-27
<b>Serial interfaces</b>	
Sheet 25 USS interface 1 .....	8-28
Sheet 26 USS interface 2 .....	8-29
Sheet 27 USS interface 3 .....	8-30
Sheet 28 Peer-to-Peer interface 2 .....	8-31
Sheet 29 Peer-to-Peer interface 3 .....	8-32
<b>Dual Port RAM</b>	
Sheet 30 Data exchange with a technology board (TB) or the 1 <sup>st</sup> communications board (CB) .....	8-33
Sheet 31 Data exchange with the 2 <sup>nd</sup> communications board (CB) .....	8-34
<b>Program structure</b>	
Sheet 32 Data sets .....	8-35
<b>Control words, status words</b>	
Sheet 33 Control word 1 .....	8-36
Sheet 34 Control word 2 .....	8-37
Sheet 35 Status word 1 .....	8-38
Sheet 36 Status word 2 .....	8-39
<b>Miscellaneous</b>	
Sheet 37 Motor interface (1) .....	8-40
Sheet 38 Motor interface (2) / binary inputs, terminals 211 to 214 .....	8-41
Sheet 39 Signals .....	8-42
Sheet 40 Fault memory .....	8-43
Sheet 41 Paralleling interface .....	8-44
Sheet 42 Field reversal with SIMOREG 6RA70 single-quadrant converter .....	8-45

## Freely assignable function blocks (Technology software in the basic converter, S00 option)

		Page
Sheet B1	1 Voltage monitor for electronics power supply.....	8-47
Sheet B1	4 Fault message triggers.....	8-47
Sheet B1	4 Alarm message triggers .....	8-47
Sheet B2	3 Connector / binector converters .....	8-48
Sheet B3	3 Binector / connector converters.....	8-49
Sheet B4	12 Adders / subtractors .....	8-50
Sheet B4	4 Sign inverters.....	8-50
Sheet B4	2 Switchable sign inverters.....	8-50
Sheet B5	3 Dividers.....	8-51
Sheet B5	4 Multipliers .....	8-51
Sheet B5	3 High-resolution multipliers / dividers.....	8-51
Sheet B6	4 Absolute-value generators with filter .....	8-52
Sheet B6	3 Limiters .....	8-53
Sheet B7	3 Limit-value monitors with filter .....	8-53
Sheets B8/B9	7 Limit-value monitors without filter .....	54/55
Sheet B10	1 Maximum selection.....	8-56
Sheet B10	1 Minimum selection.....	8-56
Sheet B10	2 Tracking / storage elements .....	8-56
Sheet B10	2 Analog signal memories .....	8-56
Sheet B11	10 Analog signal selector switches.....	8-57
Sheet B12	3 Integrators .....	8-58
Sheet B12	3 DT1 elements .....	8-58
Sheet B13	3 Characteristic blocks .....	8-59
Sheet B13	3 Dead zones .....	8-59
Sheet B13	1 Setpoint branching.....	8-59
Sheet B14	1 Simple ramp-function generator .....	8-60
Sheet B15	1 Technology controller .....	8-61
Sheet B16	1 Velocity / speed calculator ( $n \rightarrow v$ and $v \rightarrow n$ calculator) .....	8-62
Sheet B17	2 Decoders / demultiplexers, binary to 1 of 8 .....	8-63
Sheet B18	28 AND elements with 3 inputs each.....	8-64
Sheet B19	20 OR elements with 3 inputs each.....	8-65
Sheet B19	4 EXCLUSIV OR elements with 2 inputs each .....	8-65
Sheet B20	16 Inverters.....	8-66
Sheet B20	12 NAND elements with 3 inputs each.....	8-66
Sheet B21	14 RS flipflops .....	8-67
Sheet B22	4 D flipflops.....	8-68
Sheet B23	6 Timers (0,000...60,000s) .....	8-69
Sheet B24	4 Timers (0,00...600,00s) .....	8-70
Sheet B24	5 Binary signal selector switches.....	8-70


### NOTE

Freely assignable function blocks are enabled in parameter U977.  
For enabling instructions, please refer to Section 11, Parameter List, description of parameters U977 and n978.


## Optional supplementary boards

	Page
Bl. Z1      1 <sup>st</sup> EB1: Analog inputs .....	8-71
Bl. Z2      1 <sup>st</sup> EB1: Analog outputs .....	8-72
Bl. Z3      1 <sup>st</sup> EB1: 4 bidirectional inputs- / outputs, 3 digital inputs .....	8-73
Bl. Z4      2 <sup>nd</sup> EB1: Analog inputs .....	8-74
Bl. Z5      2 <sup>nd</sup> EB1: Analog outputs .....	8-75
Bl. Z6      2 <sup>nd</sup> EB1: 4 bidirectional inputs- / outputs, 3 digital inputs .....	8-76
Bl. Z7      1 <sup>st</sup> EB2: Analog input, Analog output, 2 digital inputs, 4 relay outputs .....	8-77
Bl. Z8      2 <sup>nd</sup> EB2: Analog input, Analog output, 2 digital inputs, 4 relay outputs.....	8-78
Bl. Z9      SBP pulse encoder evaluation .....	8-79
Bl. Z10     SIMOLINK board: Configuration, diagnosis.....	8-80
Bl. Z11     SIMOLINK board: Receiving, transmitting.....	8-81
Bl. Z12     OP1S operator panel .....	8-82


Sheet 1    Overview

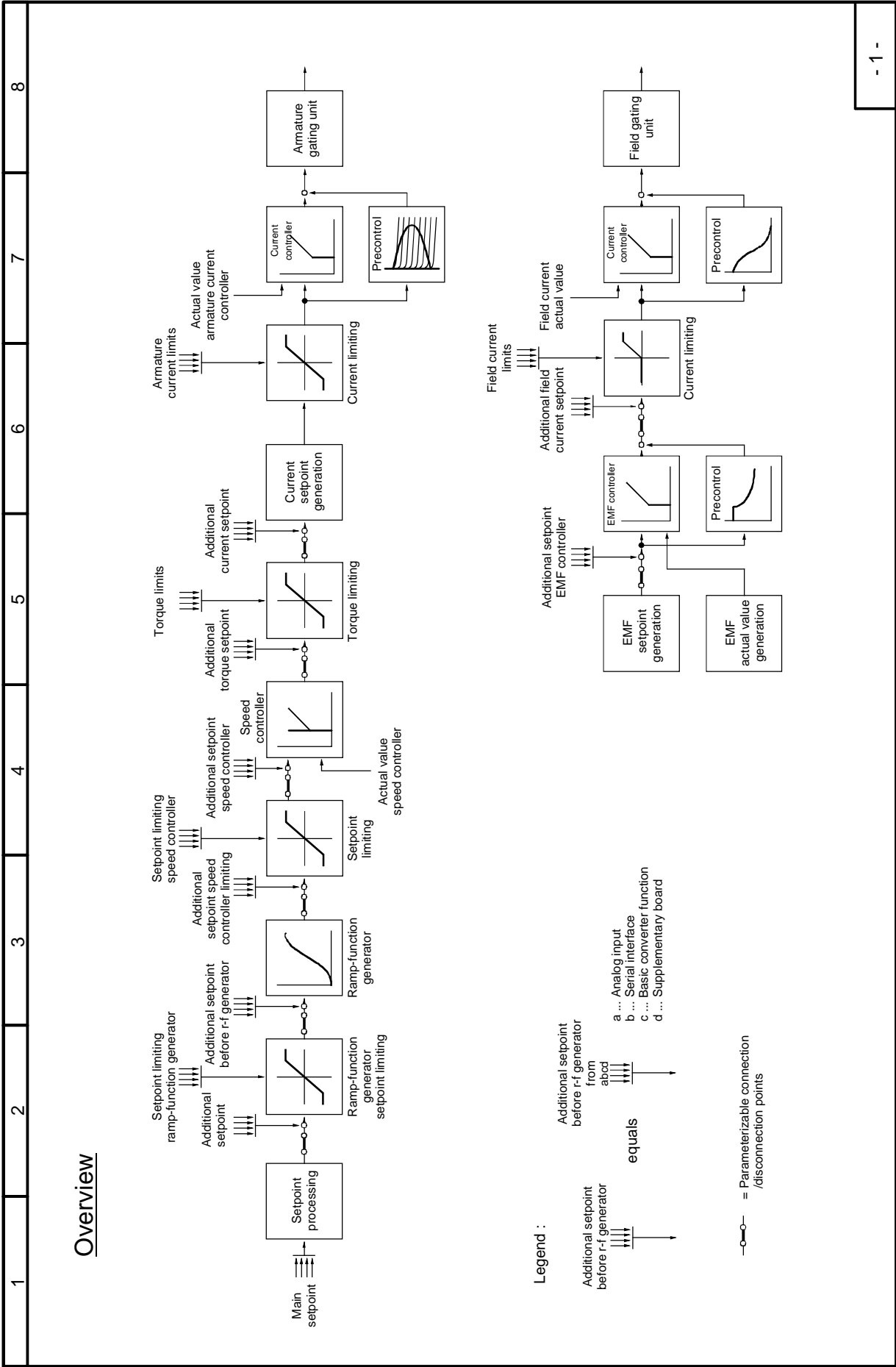

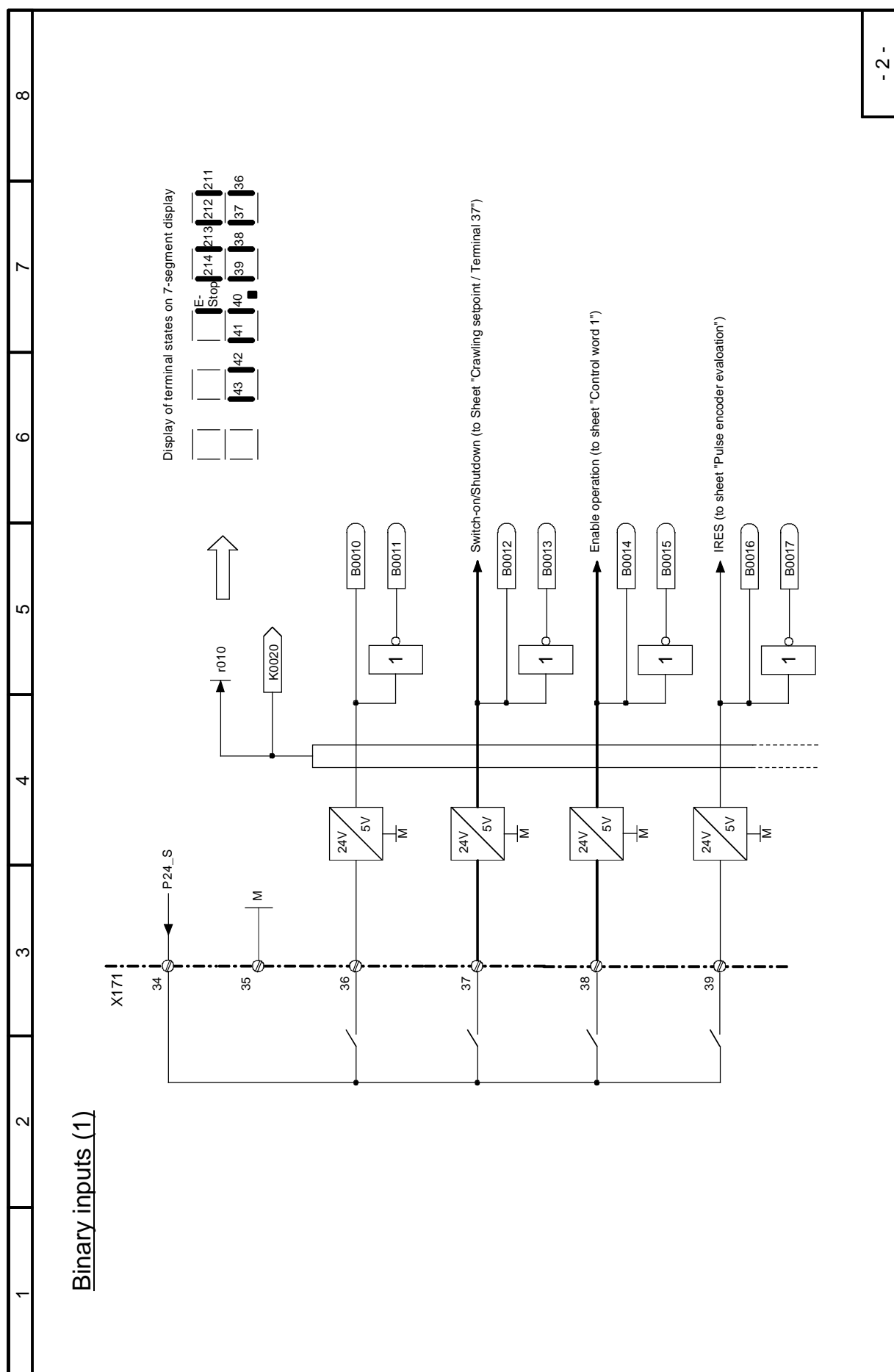
## Sheet 2 Binary inputs, terminals 36 to 39



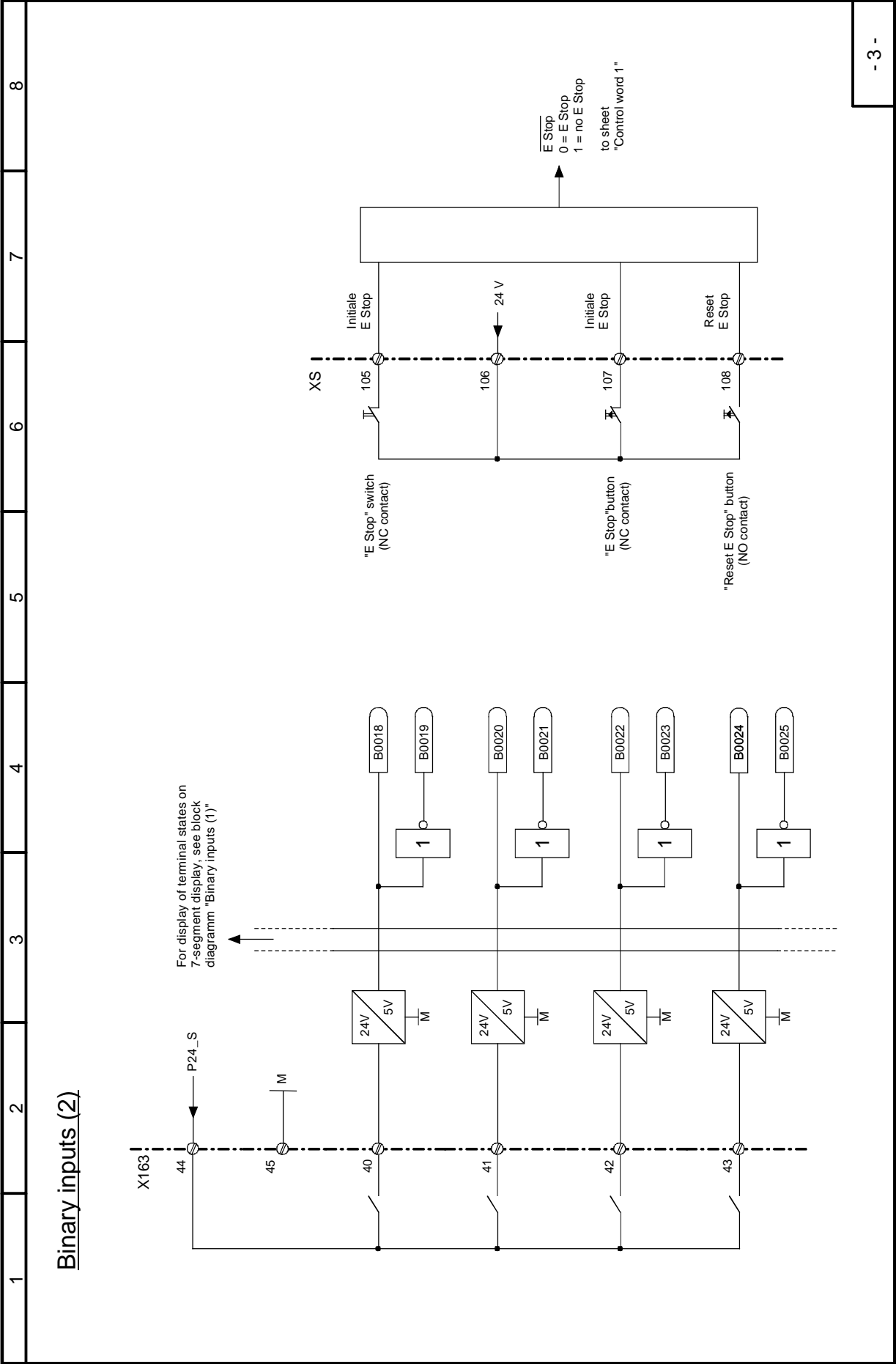
Sheet 3    Binary inputs, terminals 40 to 43


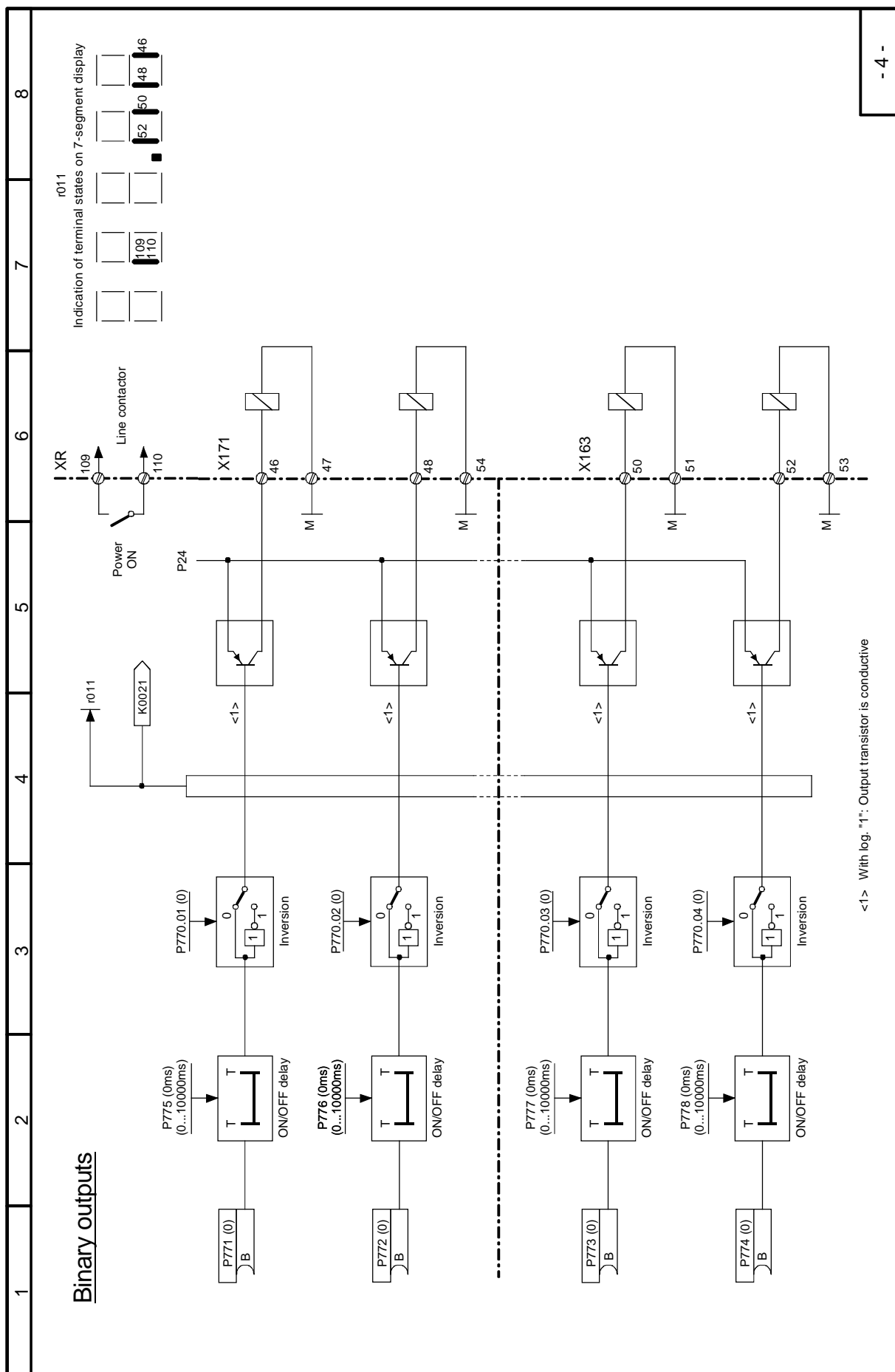
# Sheet 4 Binary outputs, terminals 46/47 and 48/49 Binary outputs, terminals 50/51 and 52/53




## 8-8

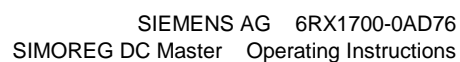



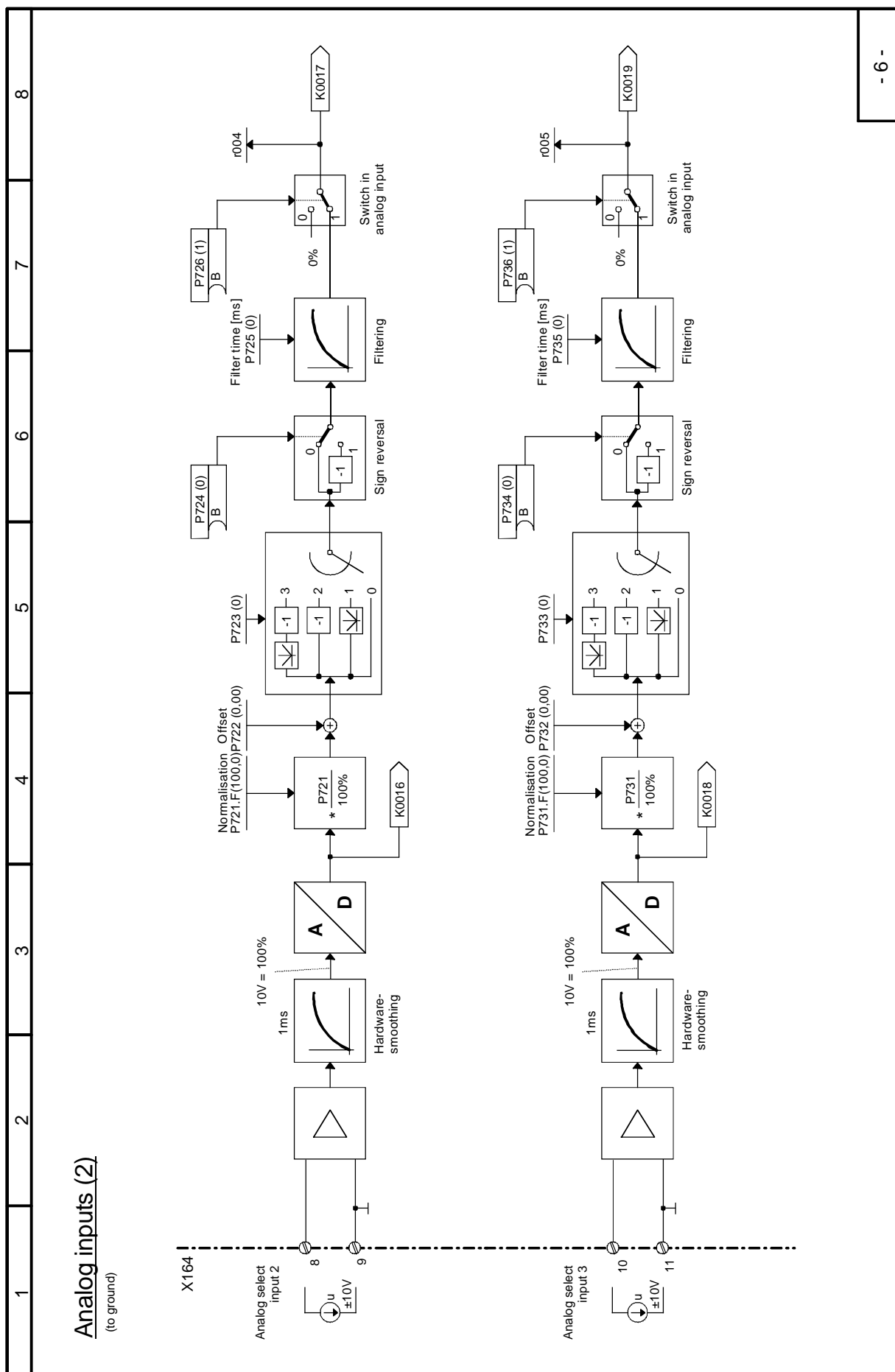
## Sheet 6 Analog inputs, terminals 8/9 and 10/11




- 6 -

8-10

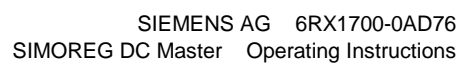

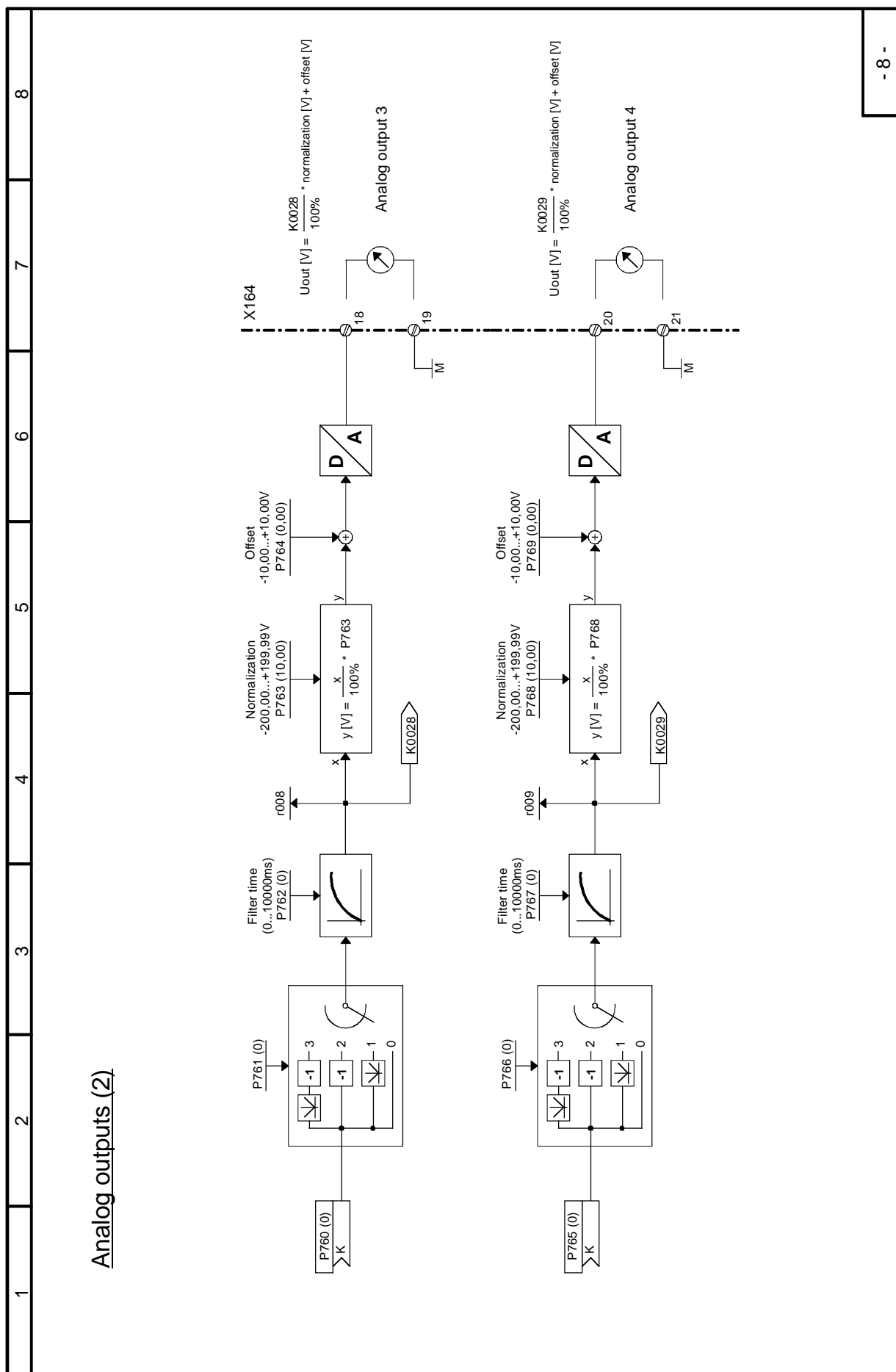
## Sheet 8 Analog outputs, terminals 18/19 and 20/21




- 8 -

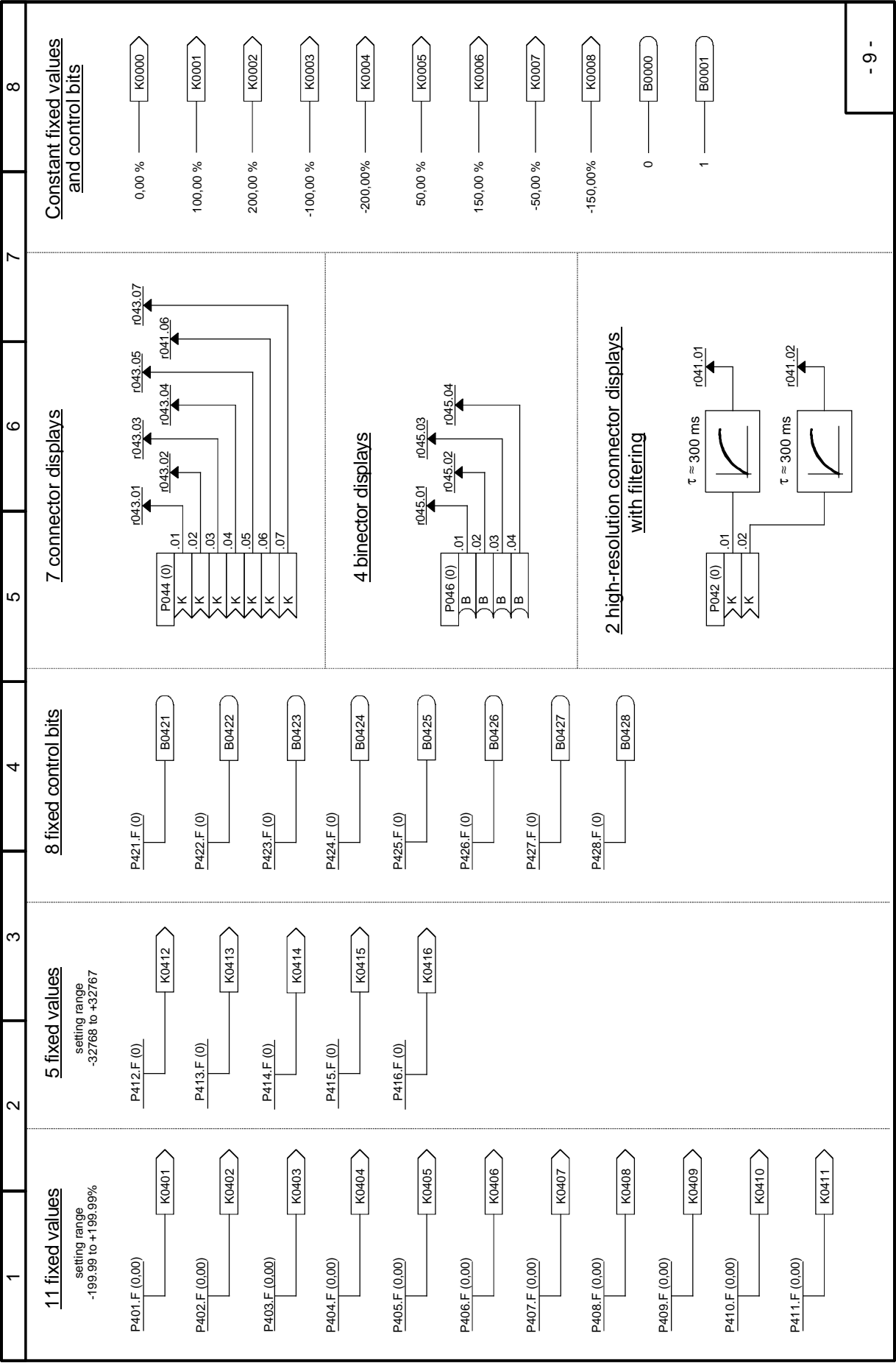Sheet 9    Fixed values, fixed control bits, constant fixed values and control bits, connector and binector displays




## Sheet 10 Motorized potentiometer

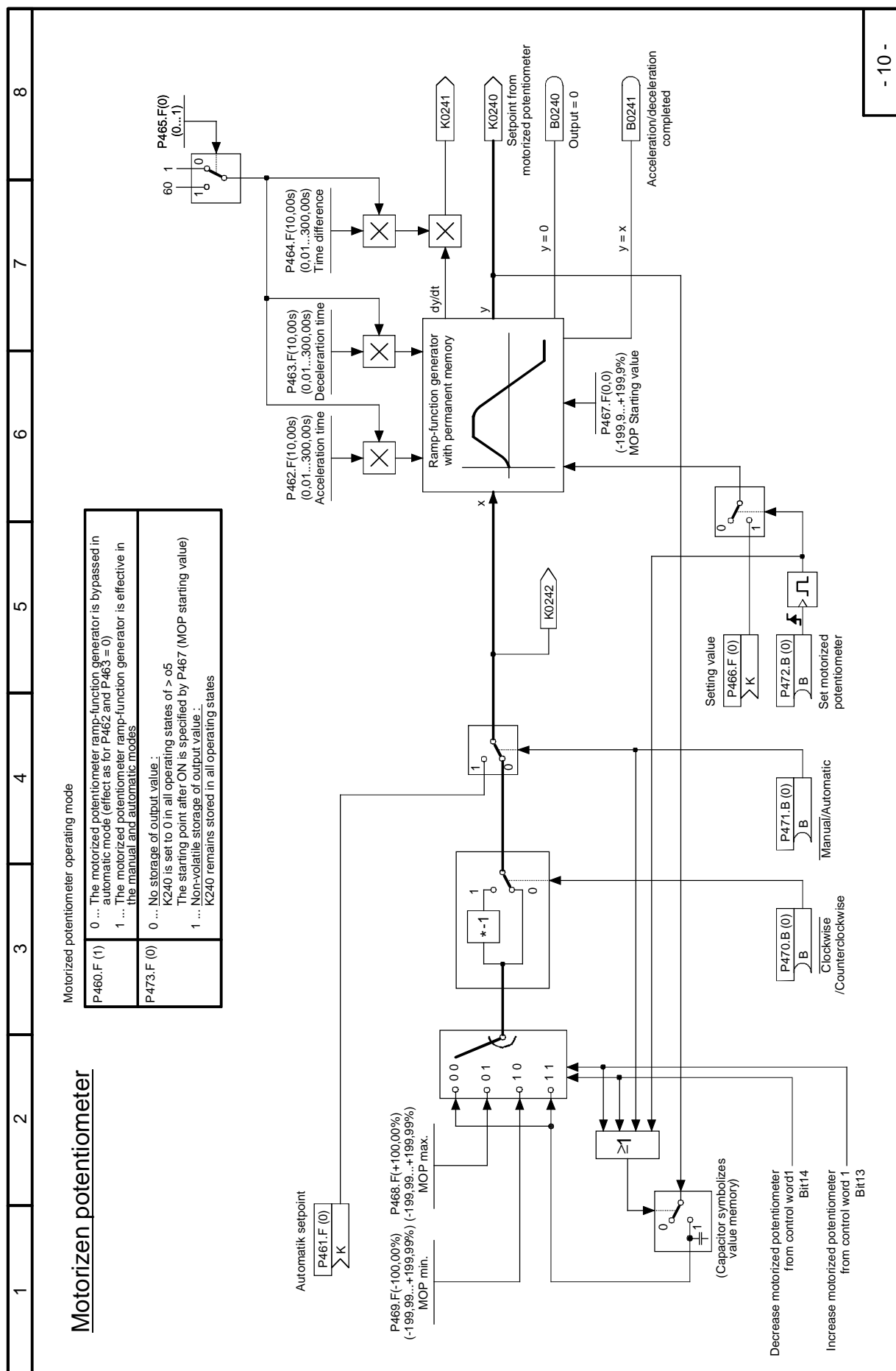


- 10 -

Sheet 11 Fixed setpoint

Fixed setpoint

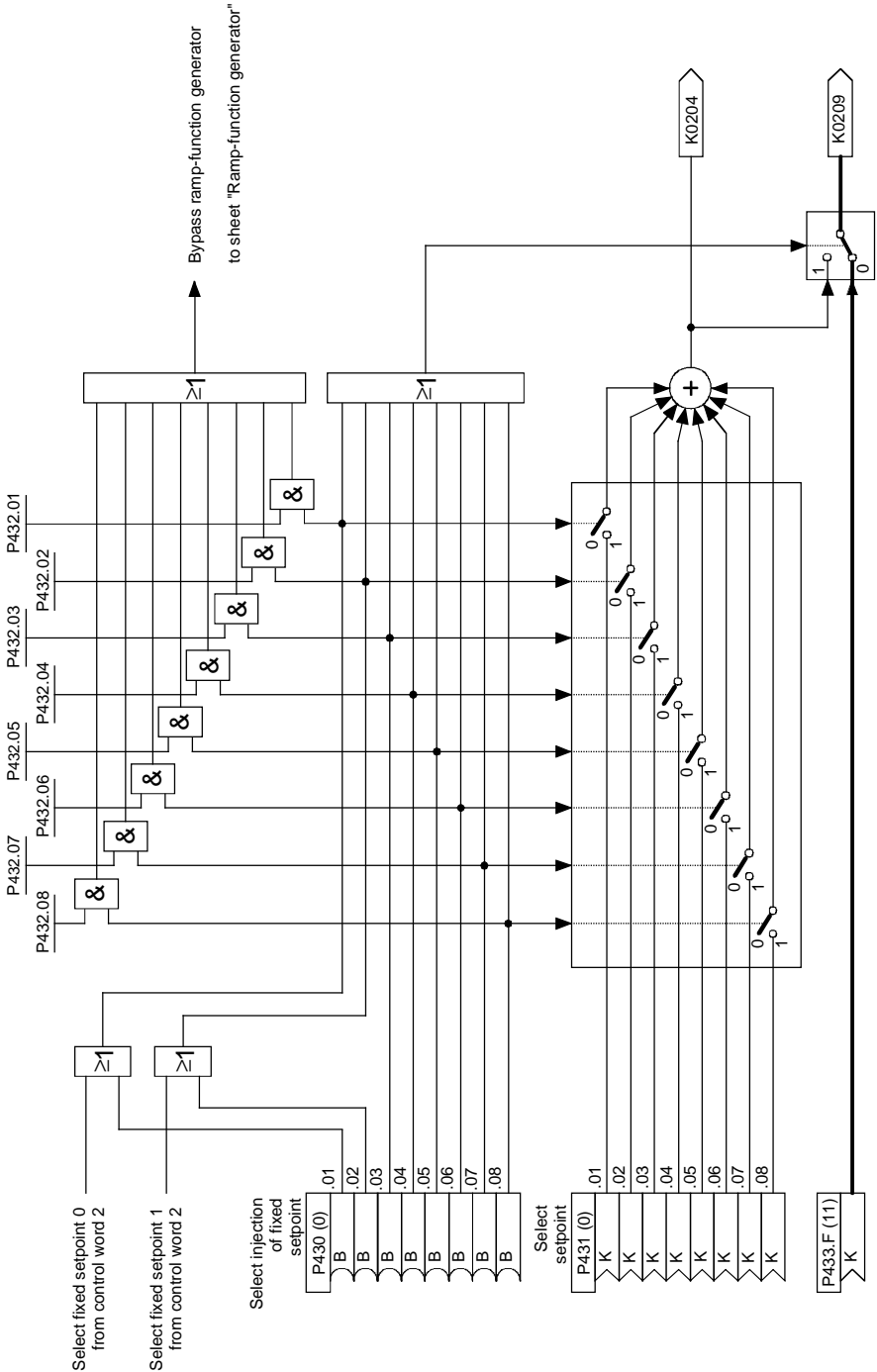


## Sheet 12 Forcing, oscillation

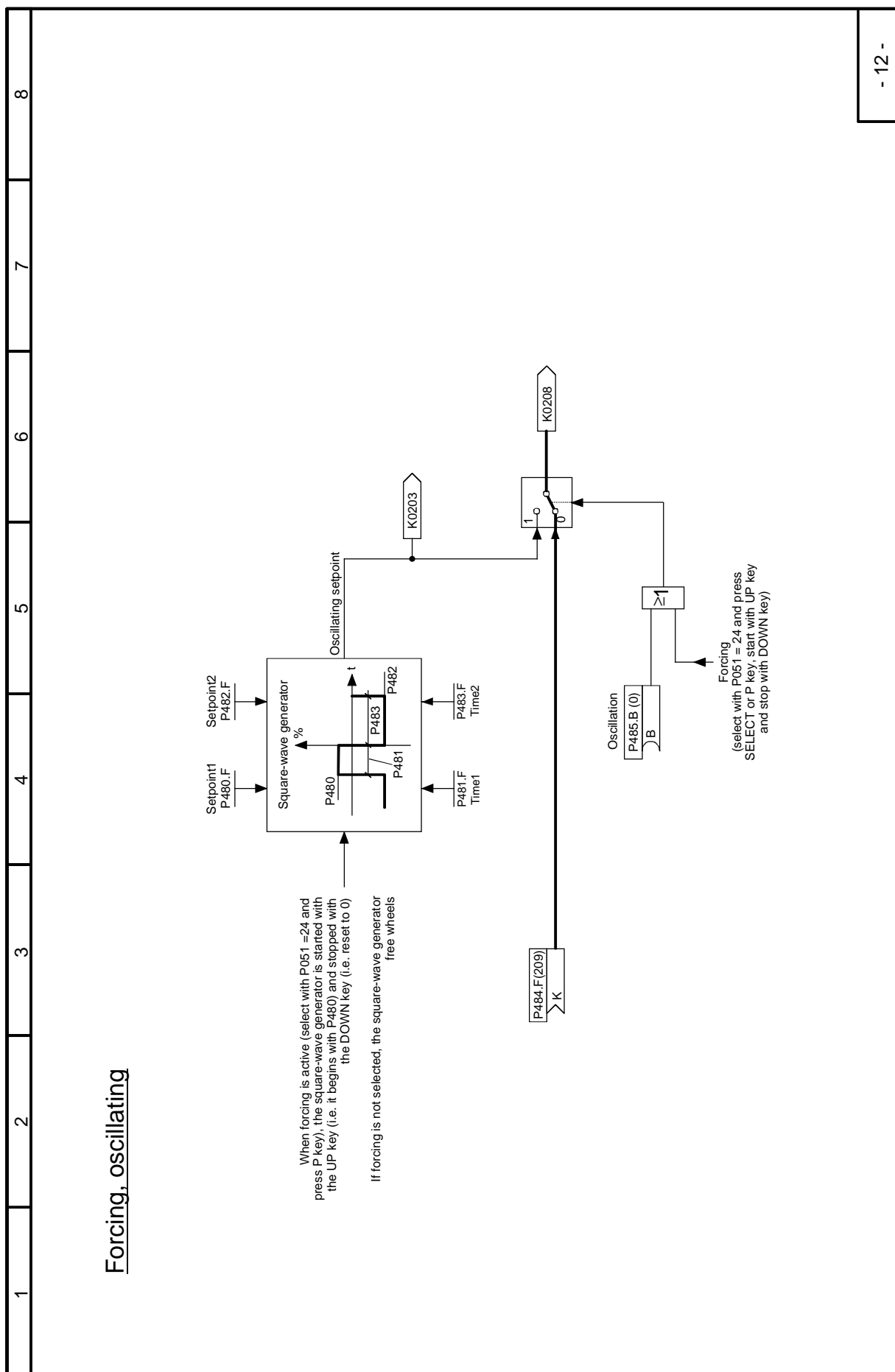


- 12 -

8-16

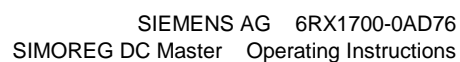





## Sheet 14 Crawling setpoint

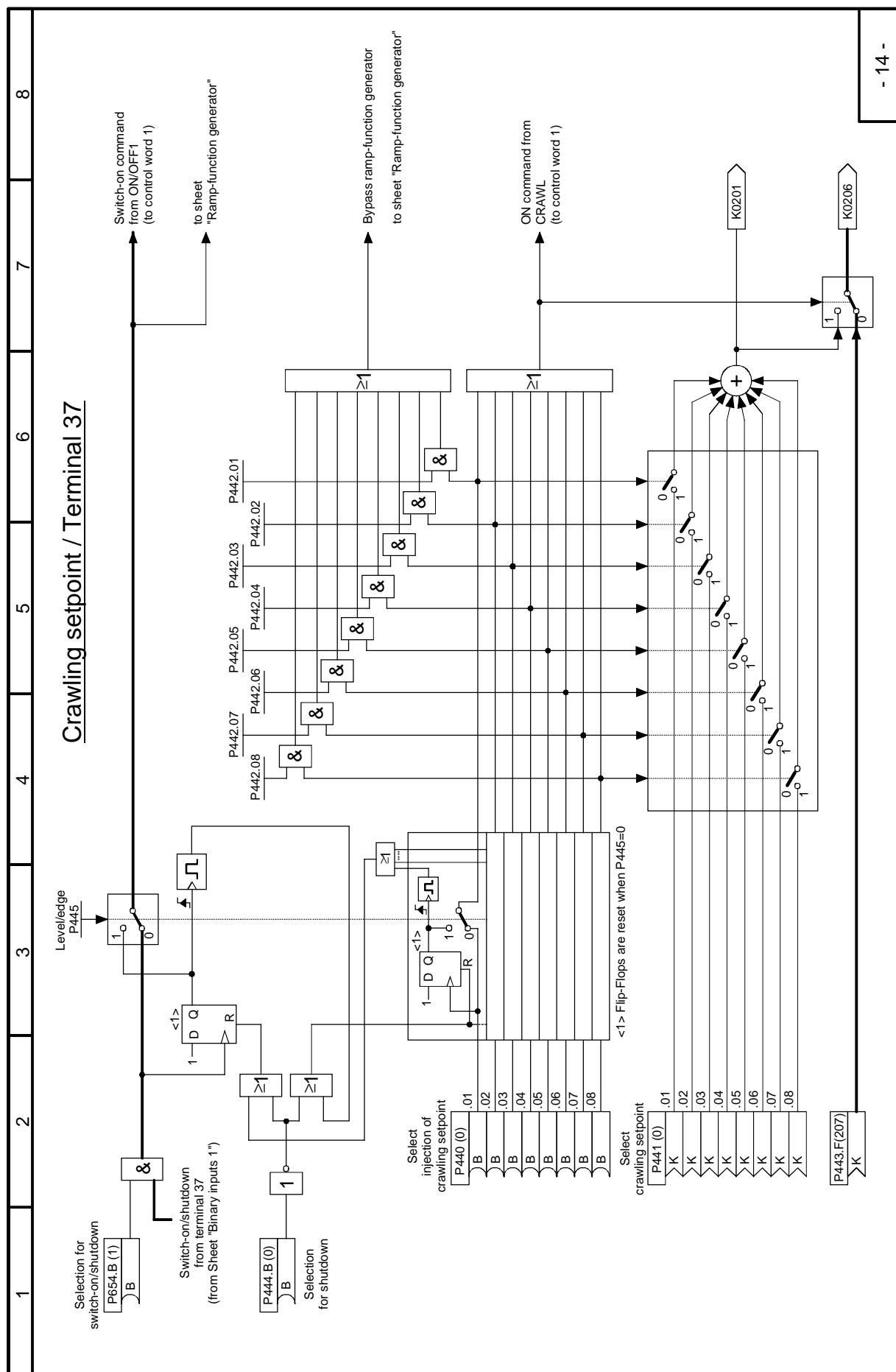

8-18

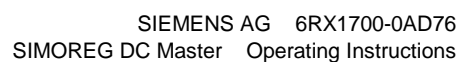


## Sheet 16 Ramp-function generator

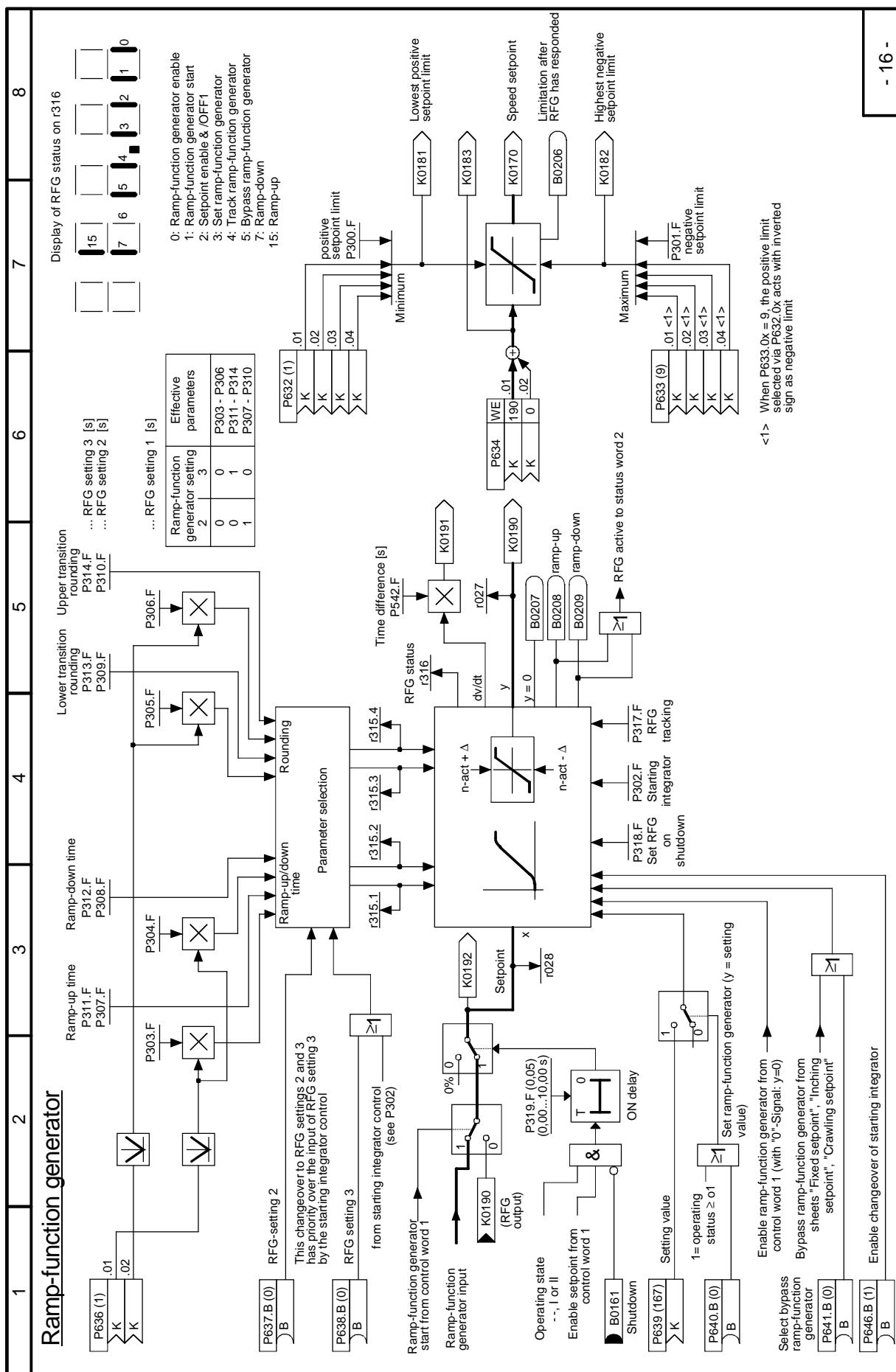

Sheet 17 Pulse encoder evaluation


Pulse encoder evaluation

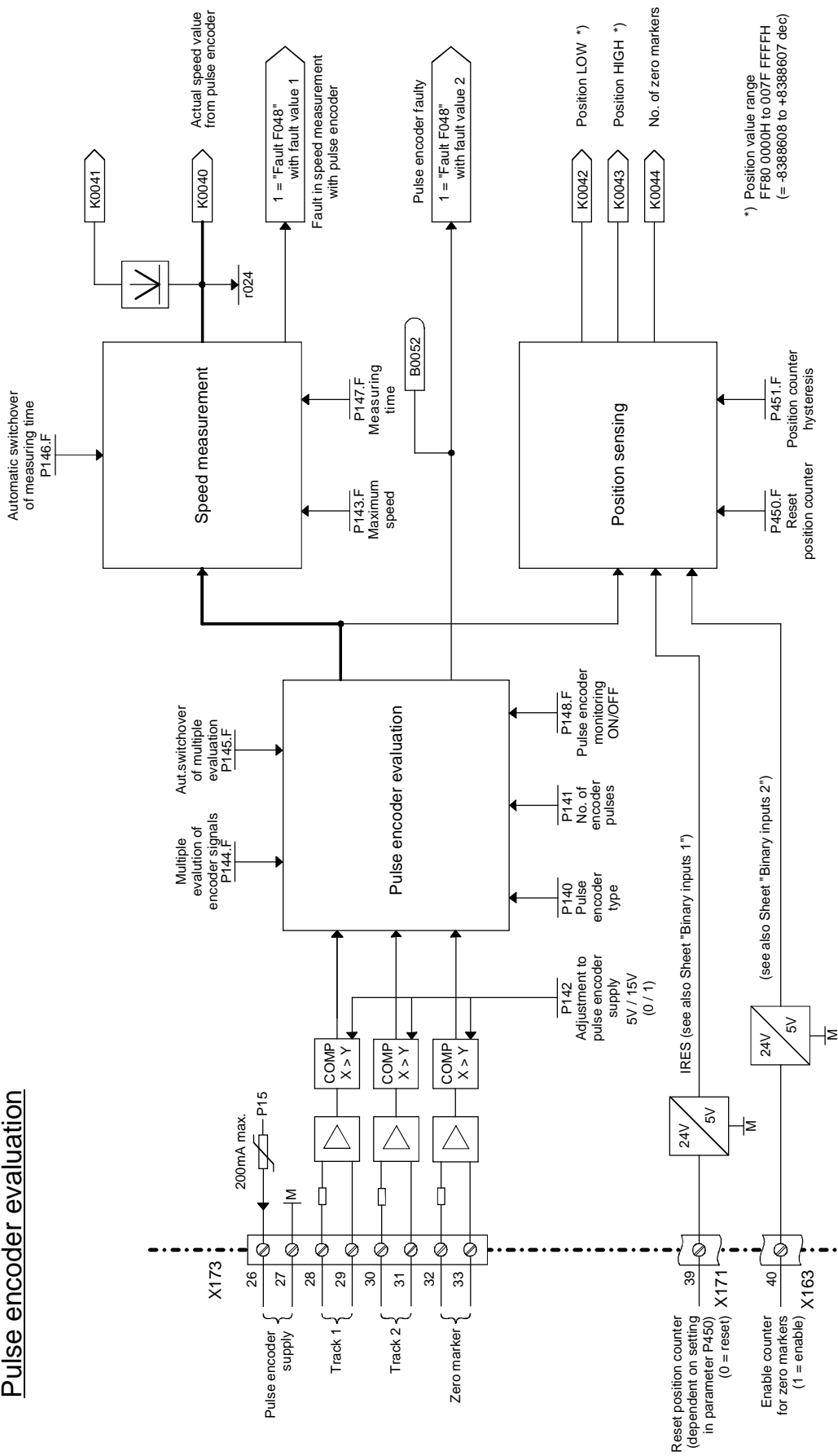

SIEMENS AG 6RX1700-0AD76  
SIMOREG DC Master Operating Instructions



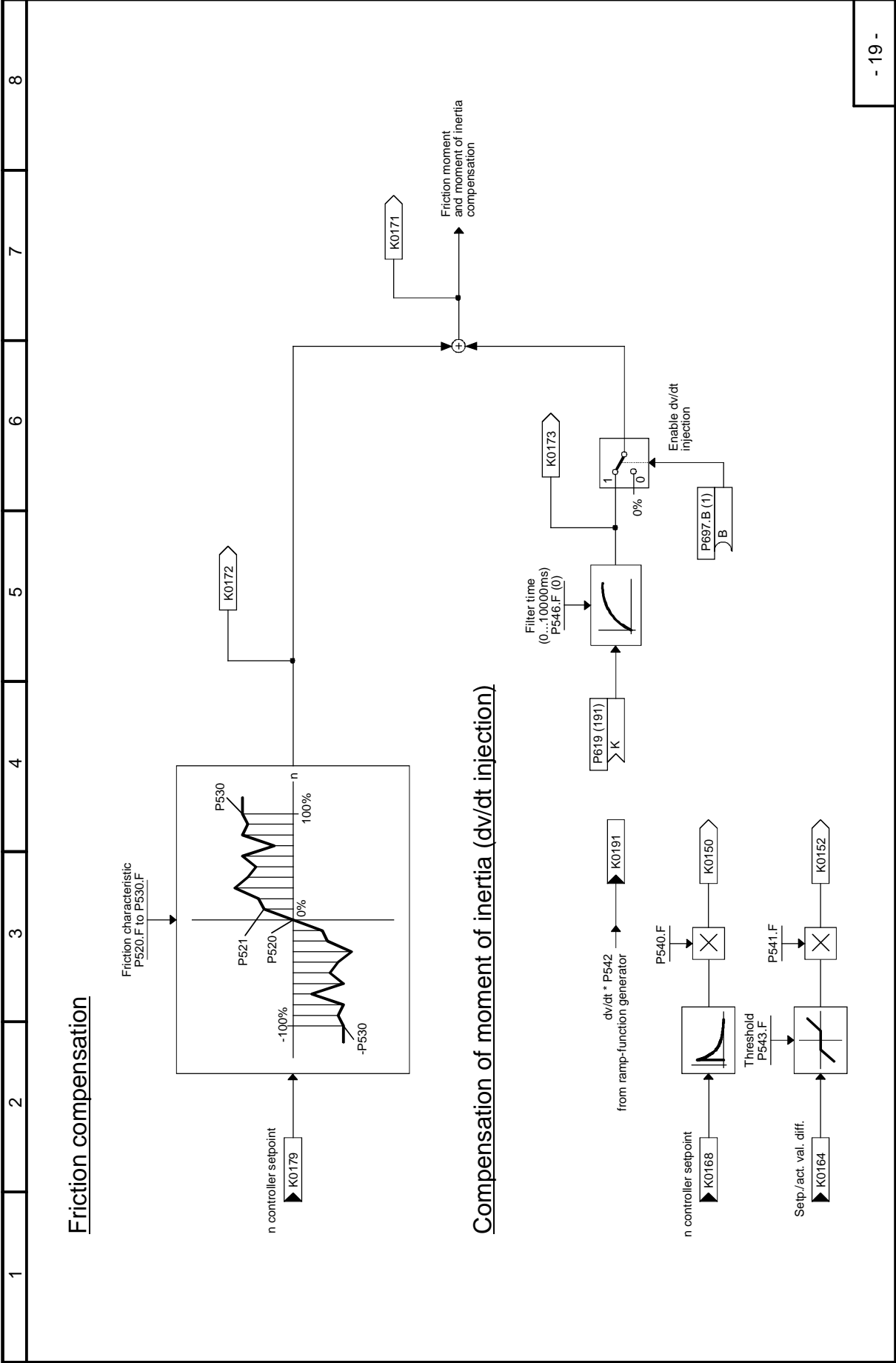
Sheet 19 Friction compensation  
Compensation of moment of inertia (dv/dt injection)



SIEMENS AG 6RX1700-0AD76  
SIMOREG DC Master Operating Instructions




Sheet 21 Current limitation

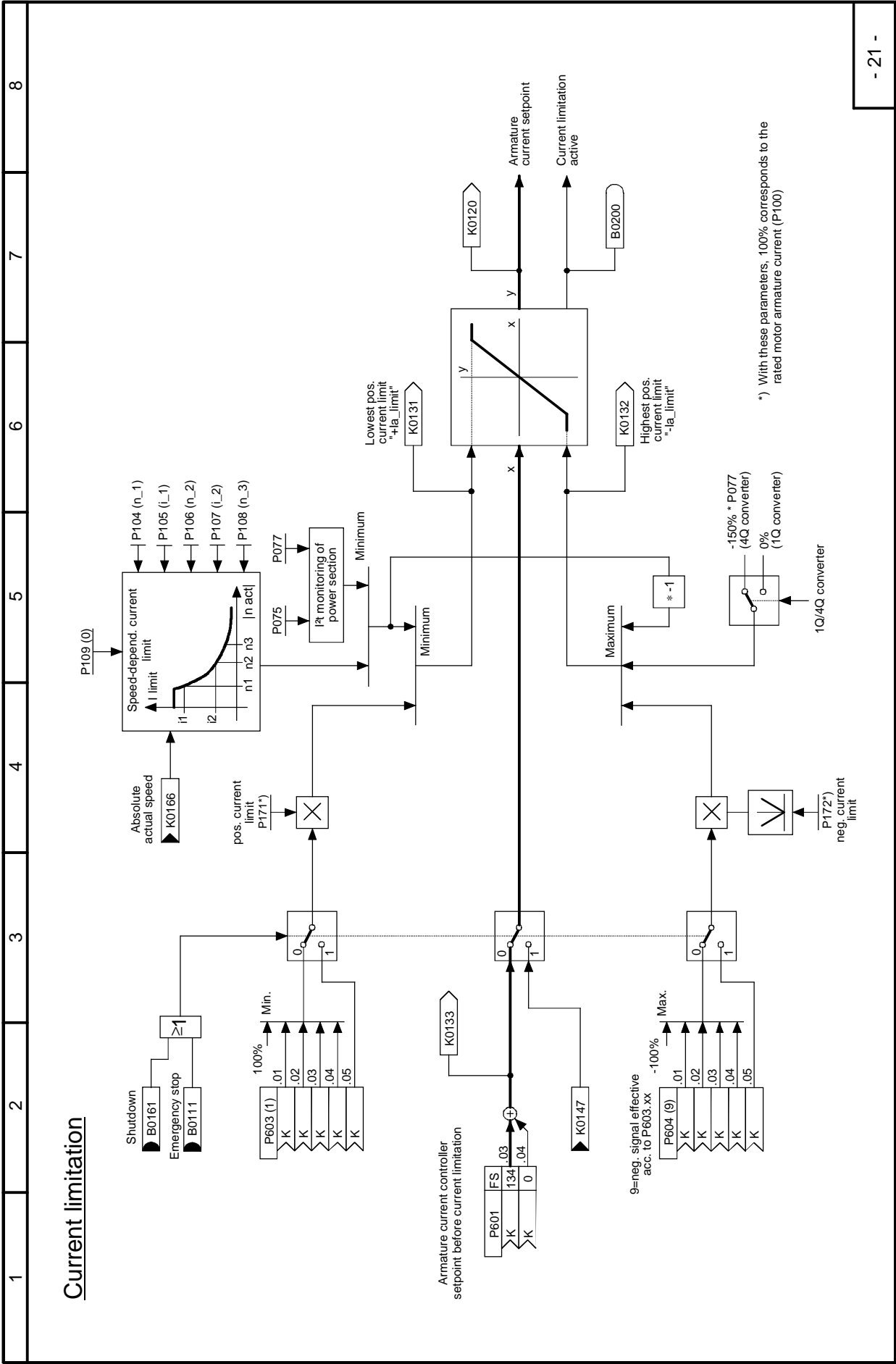




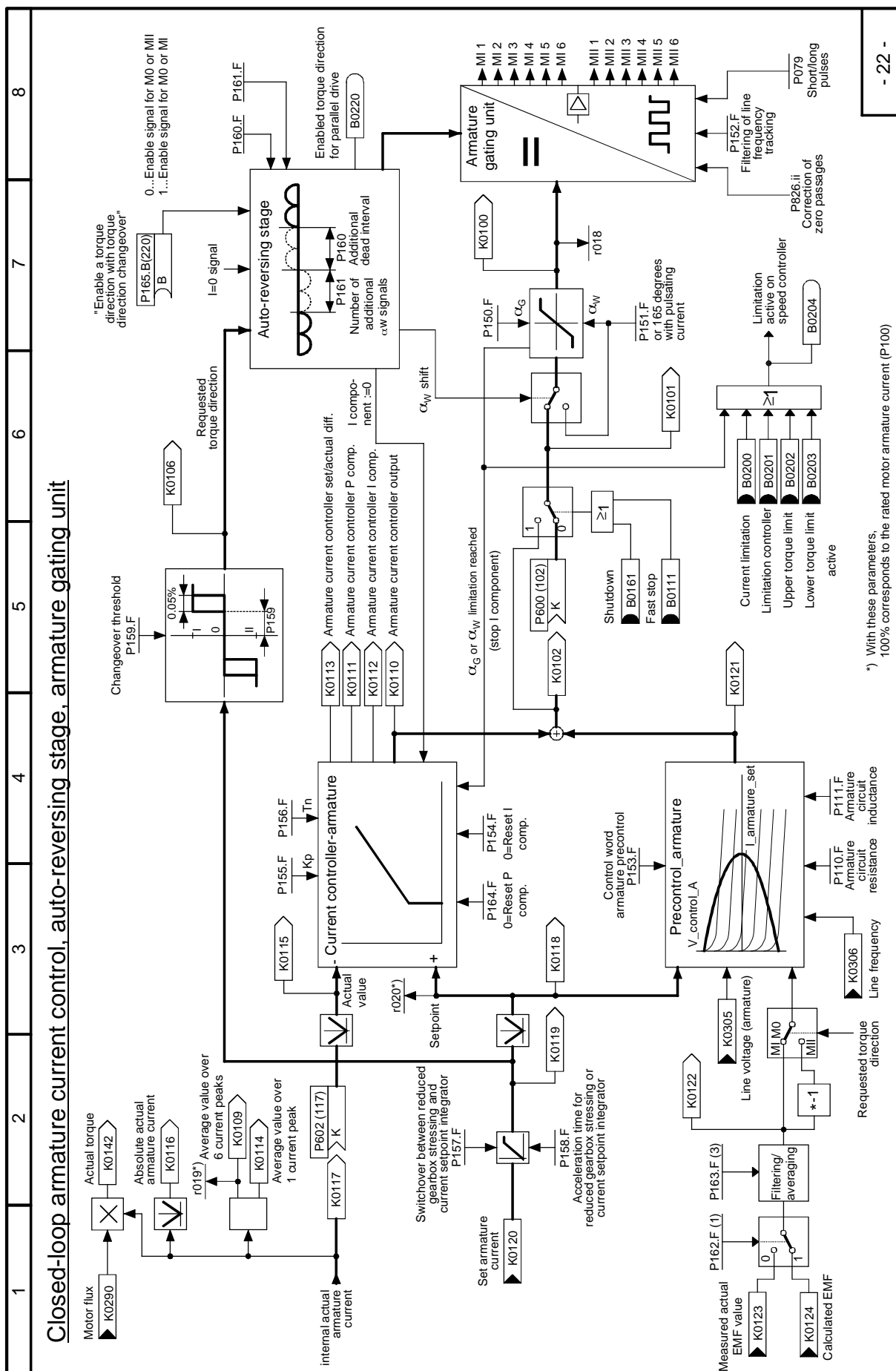
**Sheet 22 Closed-loop armature current control, auto-reversing stage, armature gating unit**



## 8-26

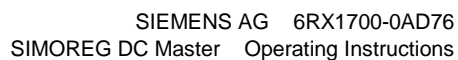

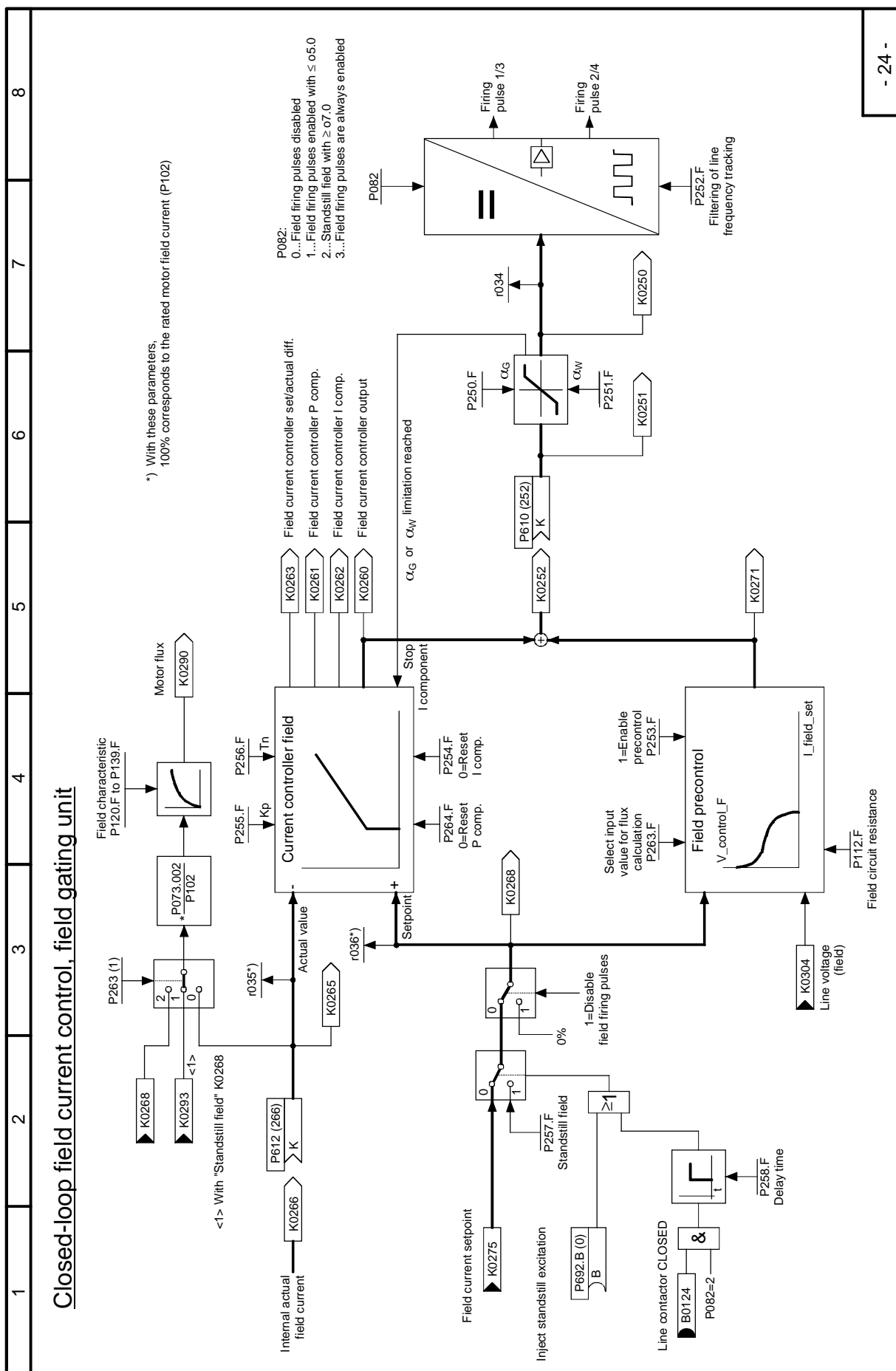
## Sheet 24 Closed-loop field current control, field gating unit




- 24 -

## 8-28

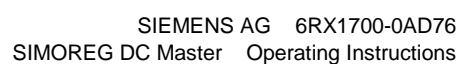


## Sheet 26 USS interface 2

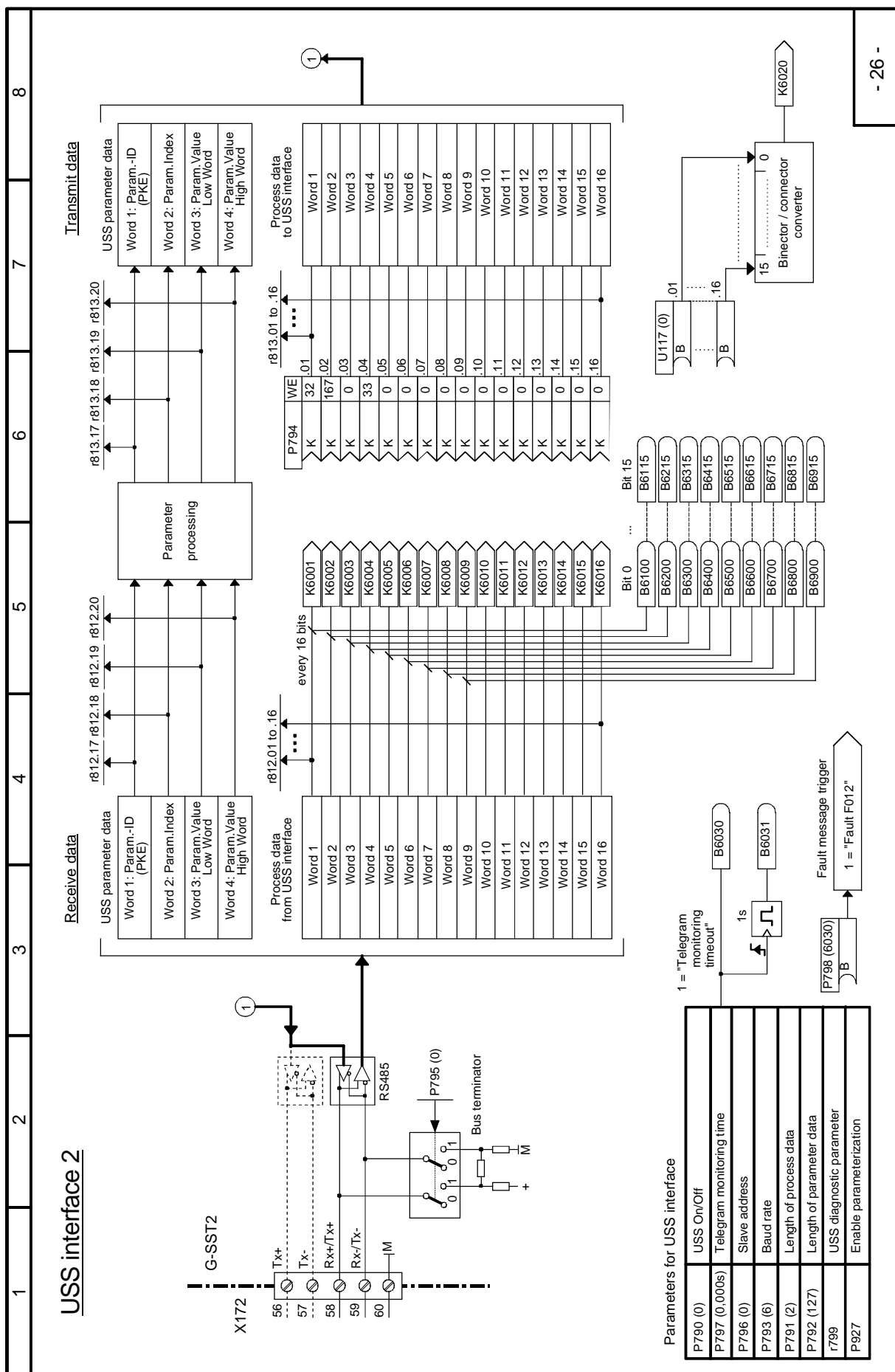


- 26 -


## 8-30

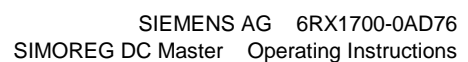

## Sheet 28 Peer-to-Peer interface 2

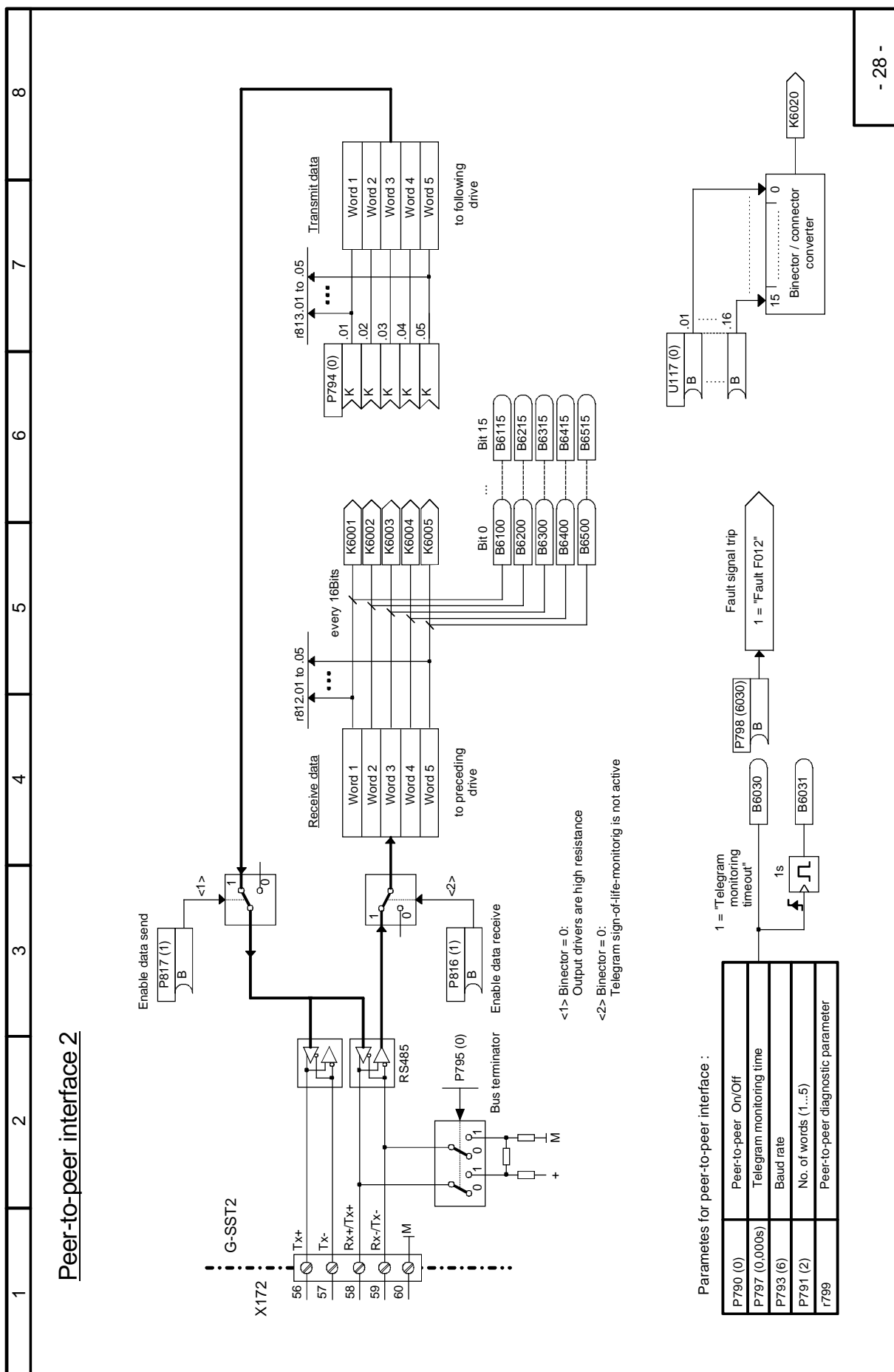


## 8-32

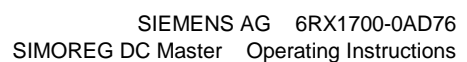




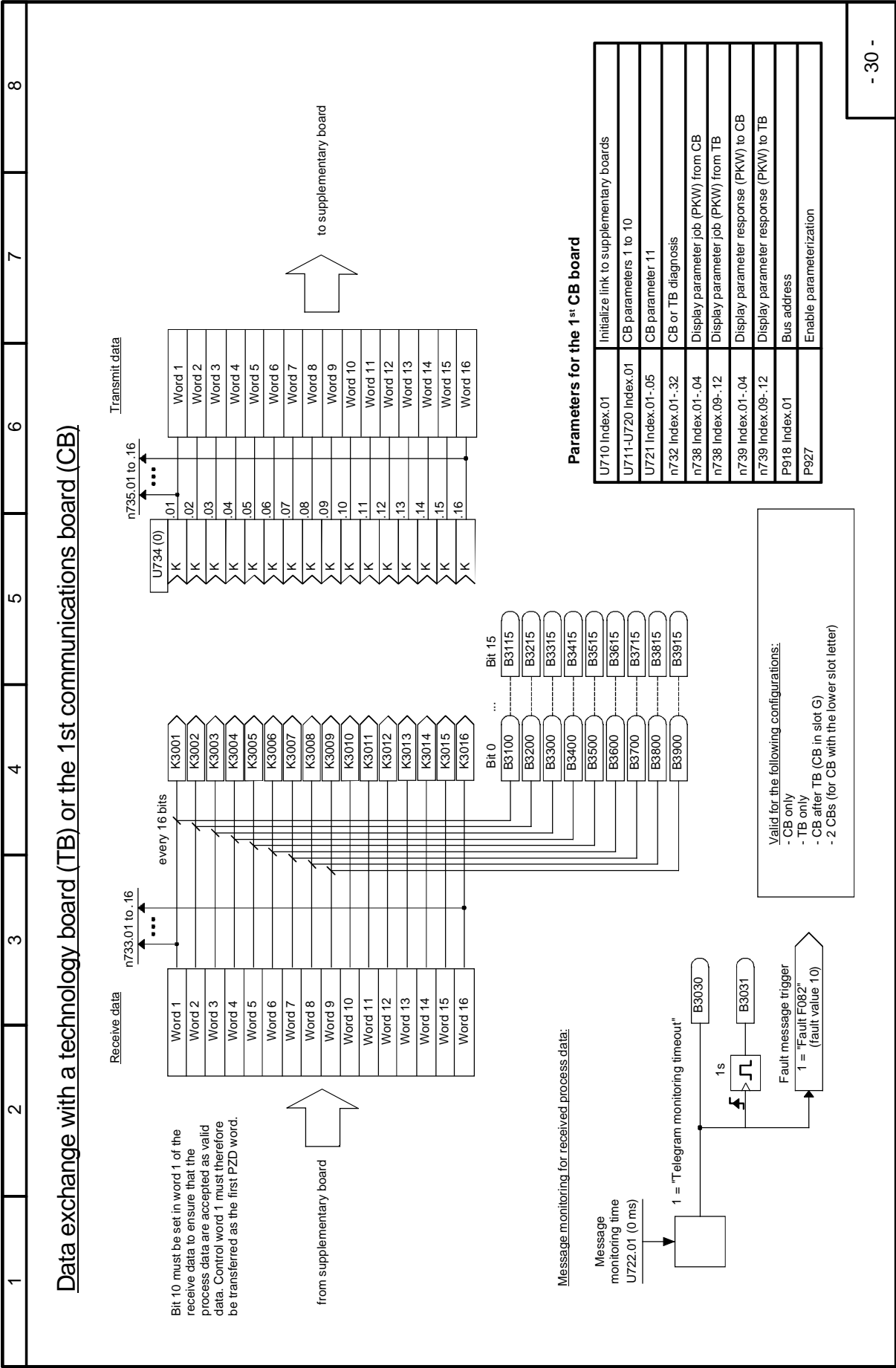
Sheet 30 Data exchange with a technology board (TB) or the 1<sup>st</sup> communications board (CB)



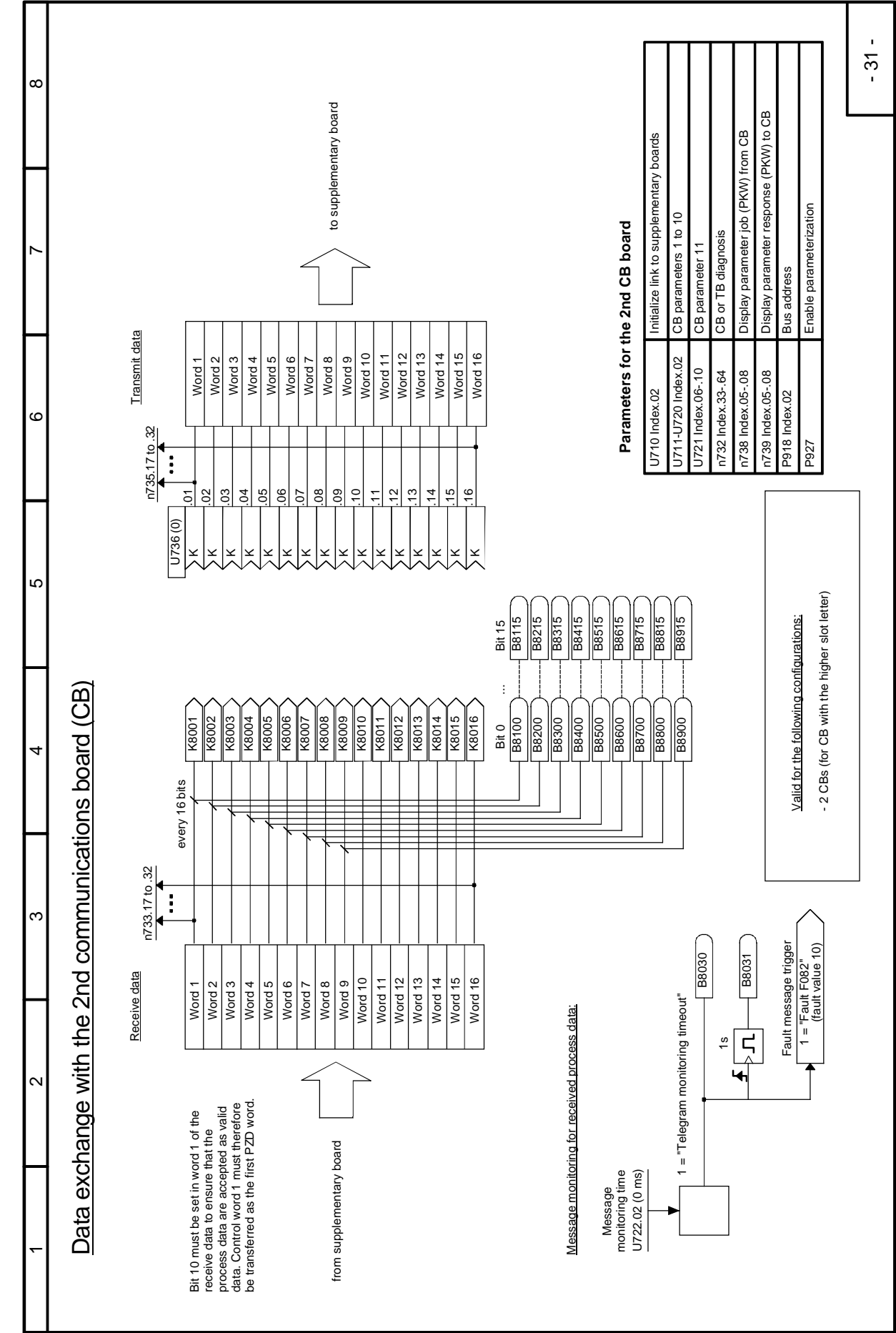
Sheet 31 Data exchange with the 2<sup>nd</sup> communications board (CB)




Sheet 32 Data sets

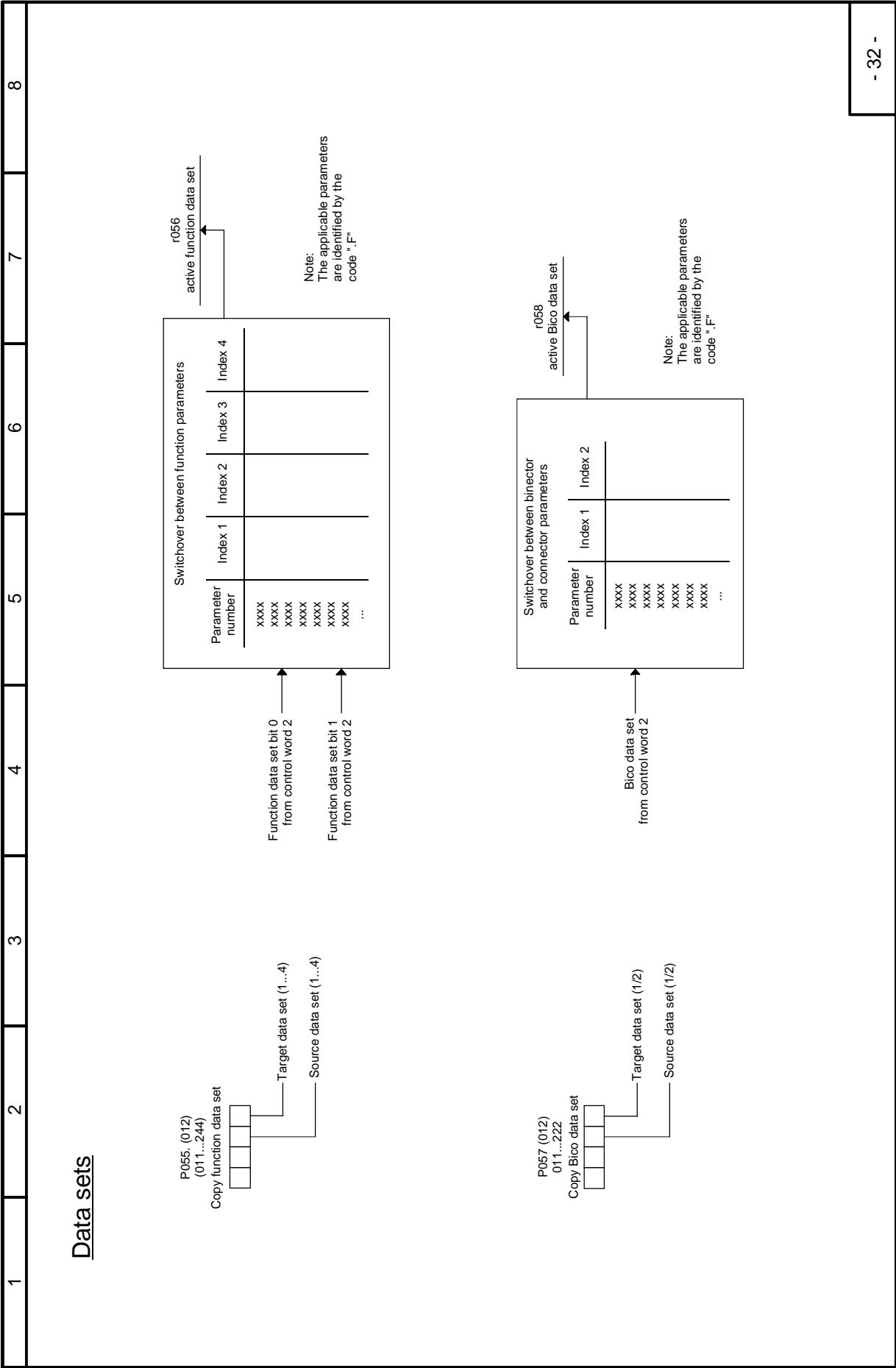

Sheet 33 Control word 1

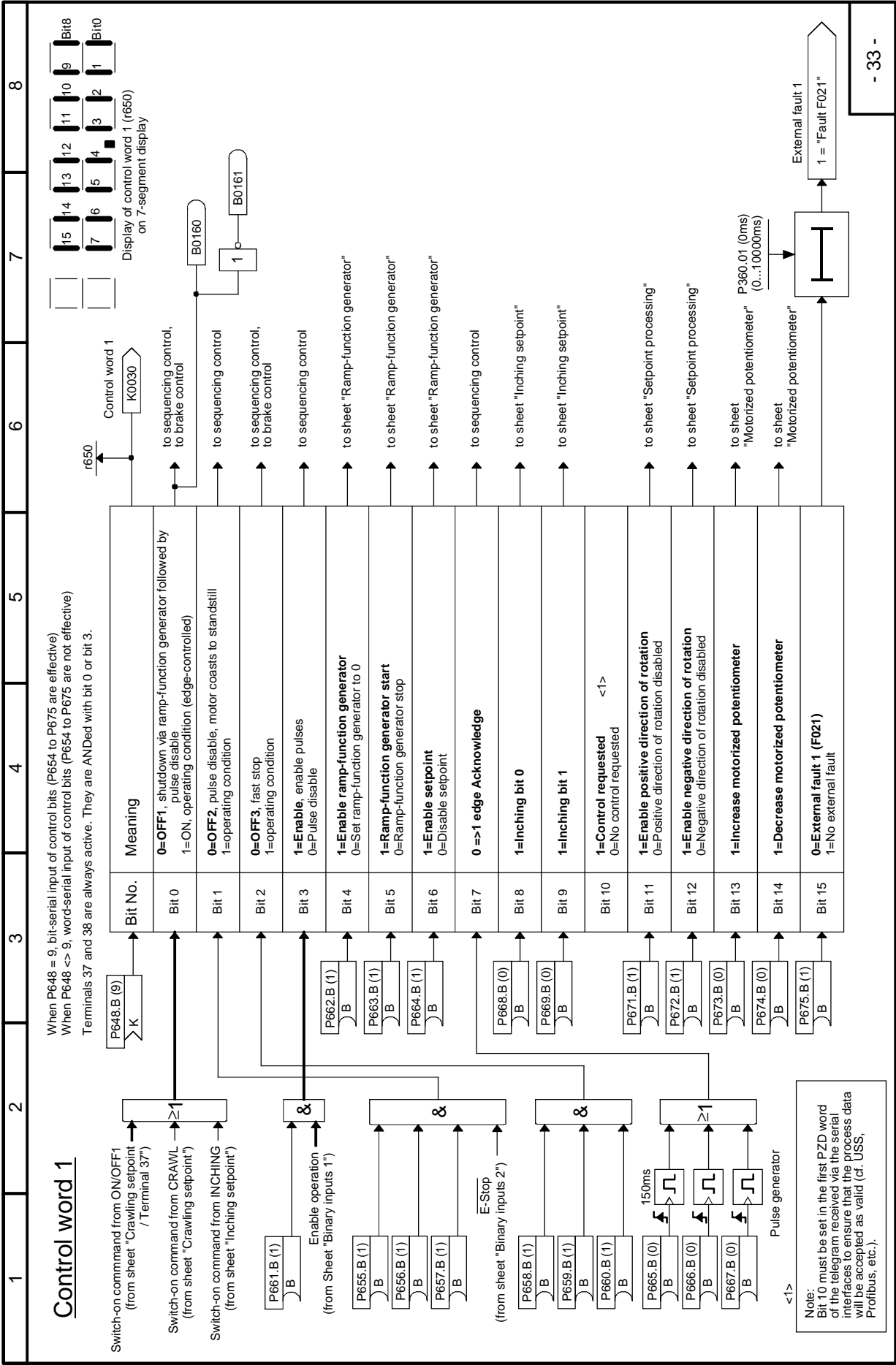

## Sheet 34 Control word 2

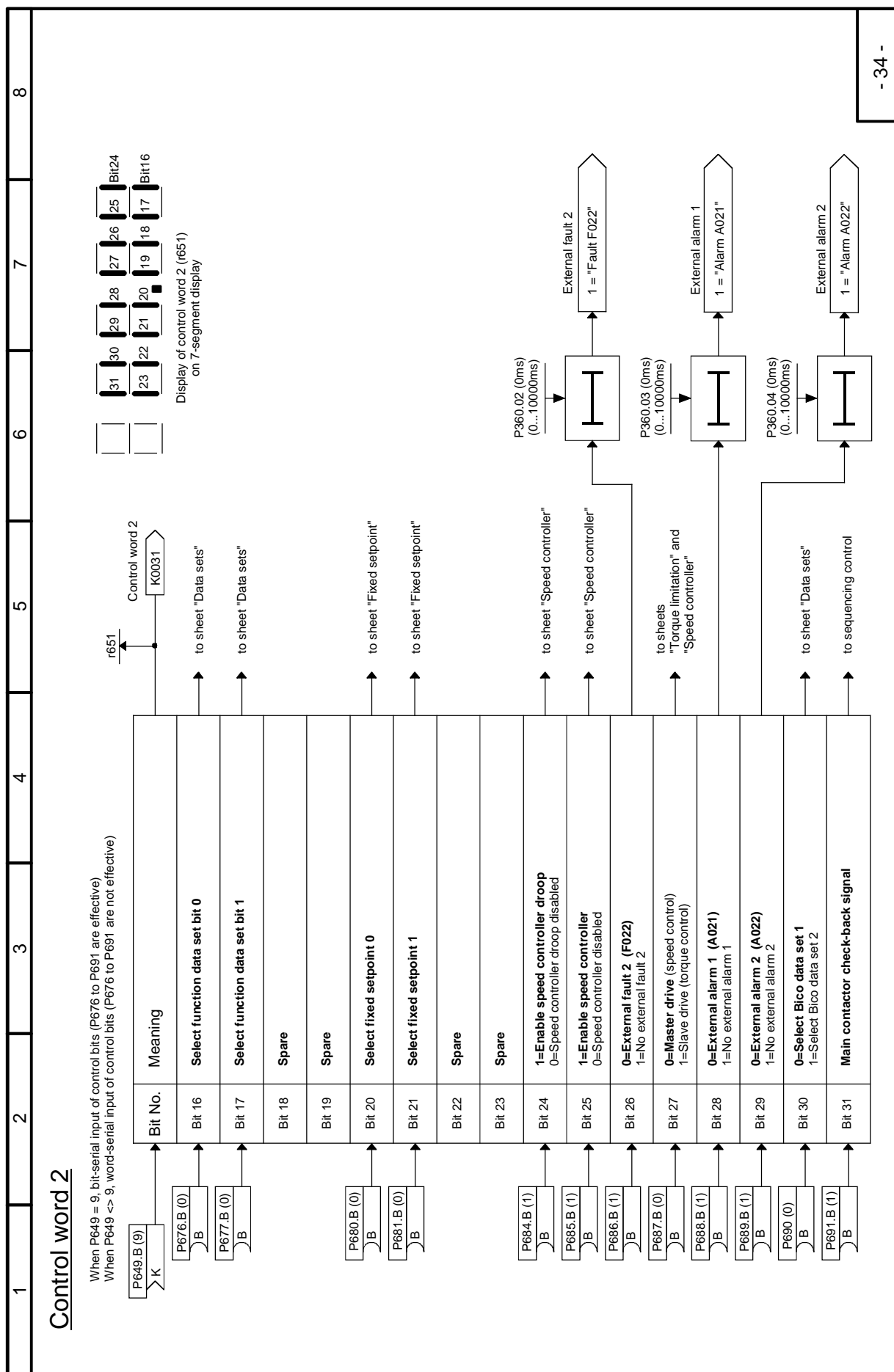


## 8-38

SIEMENS AG 6RX1700-0AD76  
SIMOREG DC Master Operating Instructions


## Status word 2




## 8-40

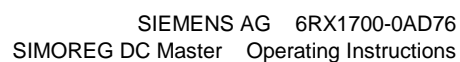

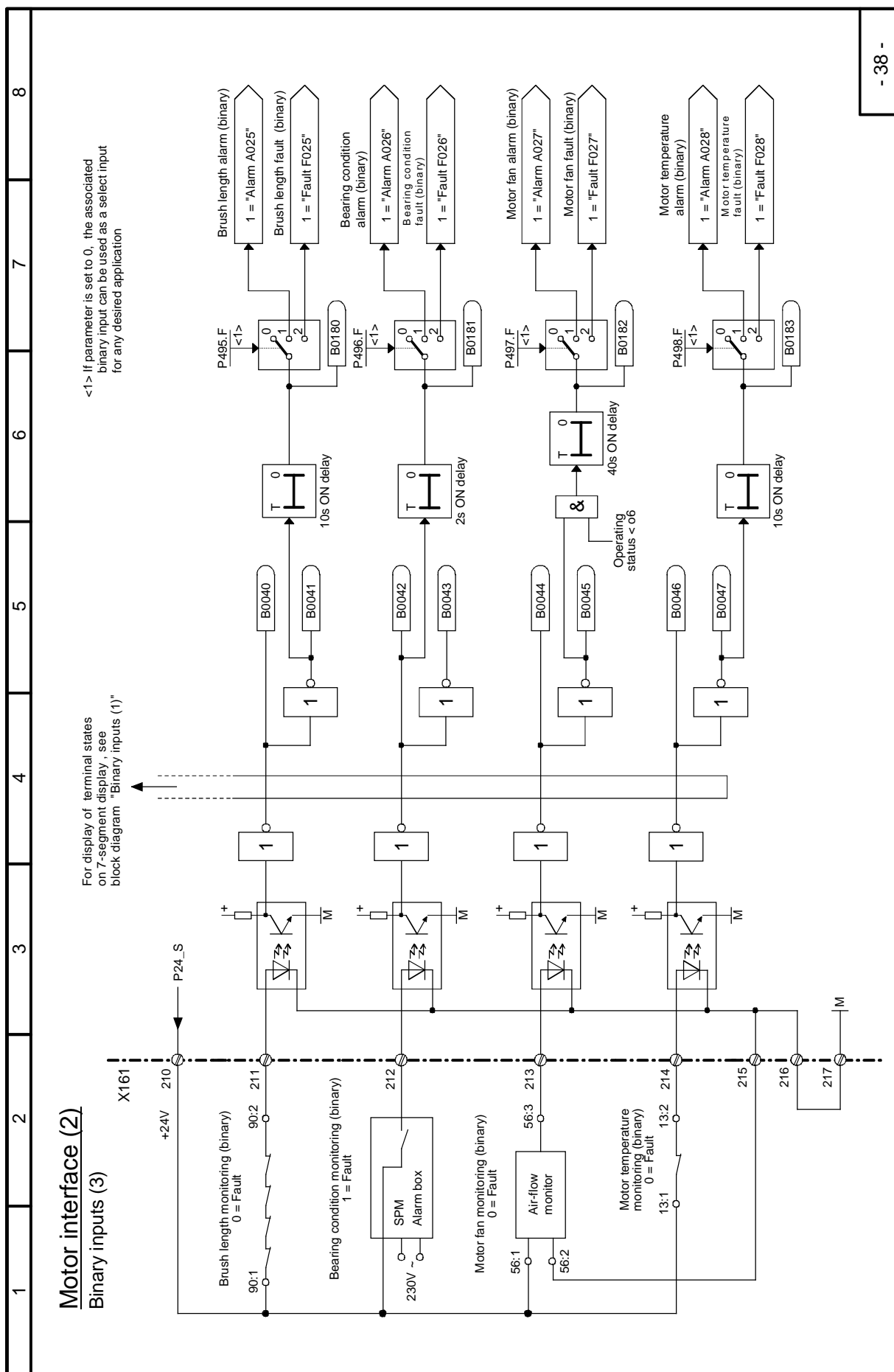


**Sheet 38 Motor interface (2) / binary inputs, terminals 211 to 214**


## Sheet 39 Signals

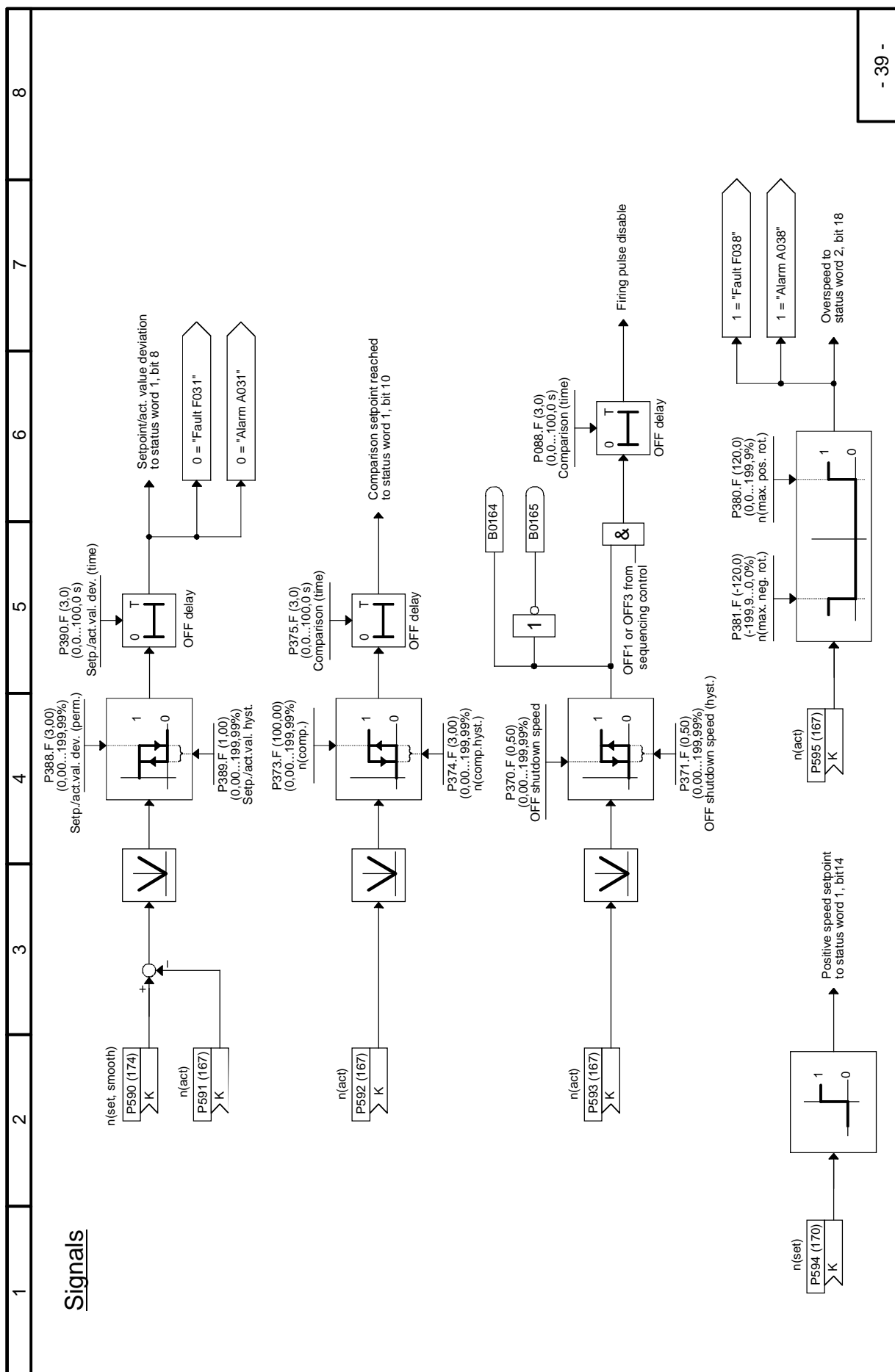


- 39 -


## Sheet 40 Fault memory

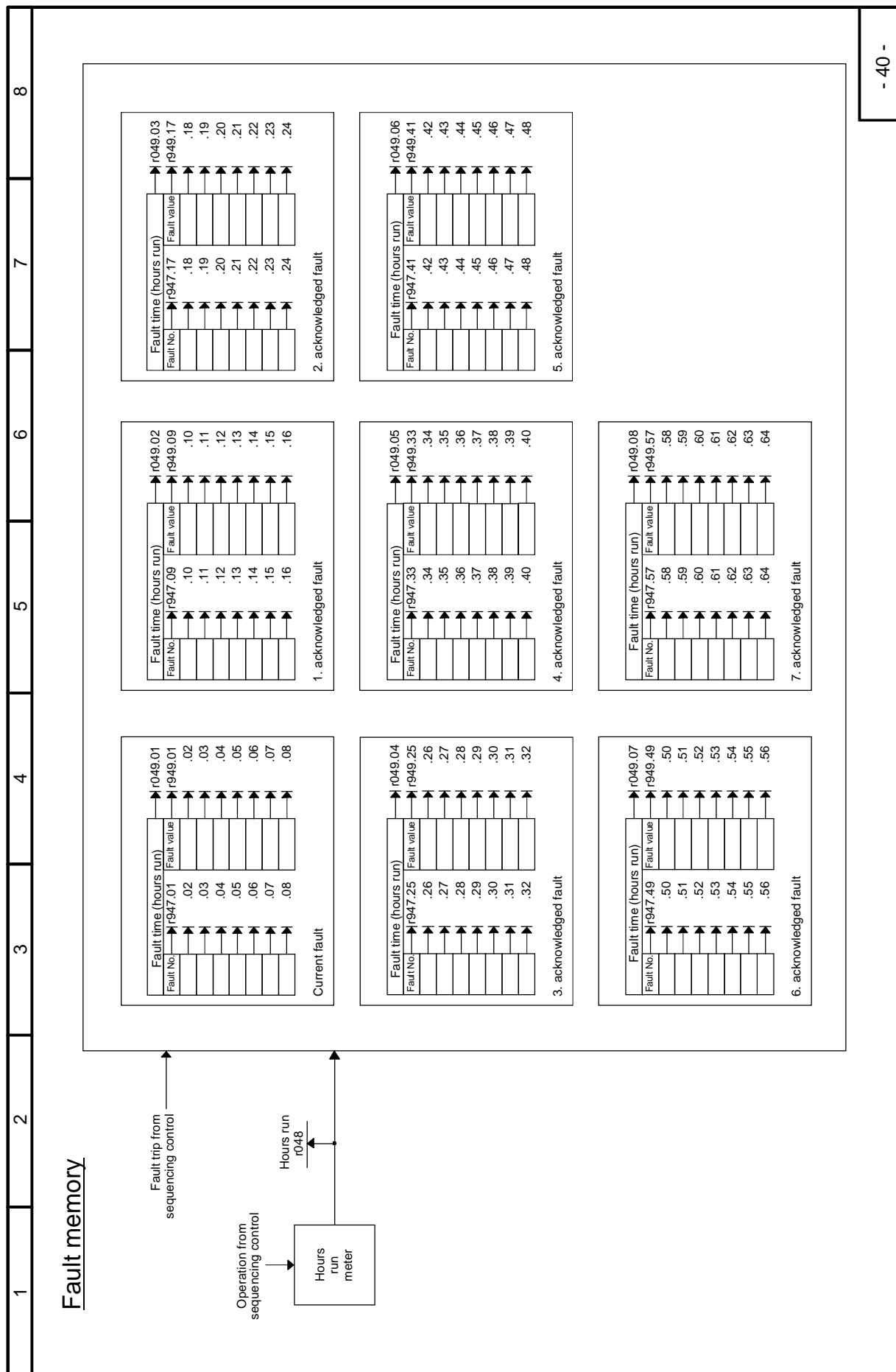

Sheet 41 Paralleling interface

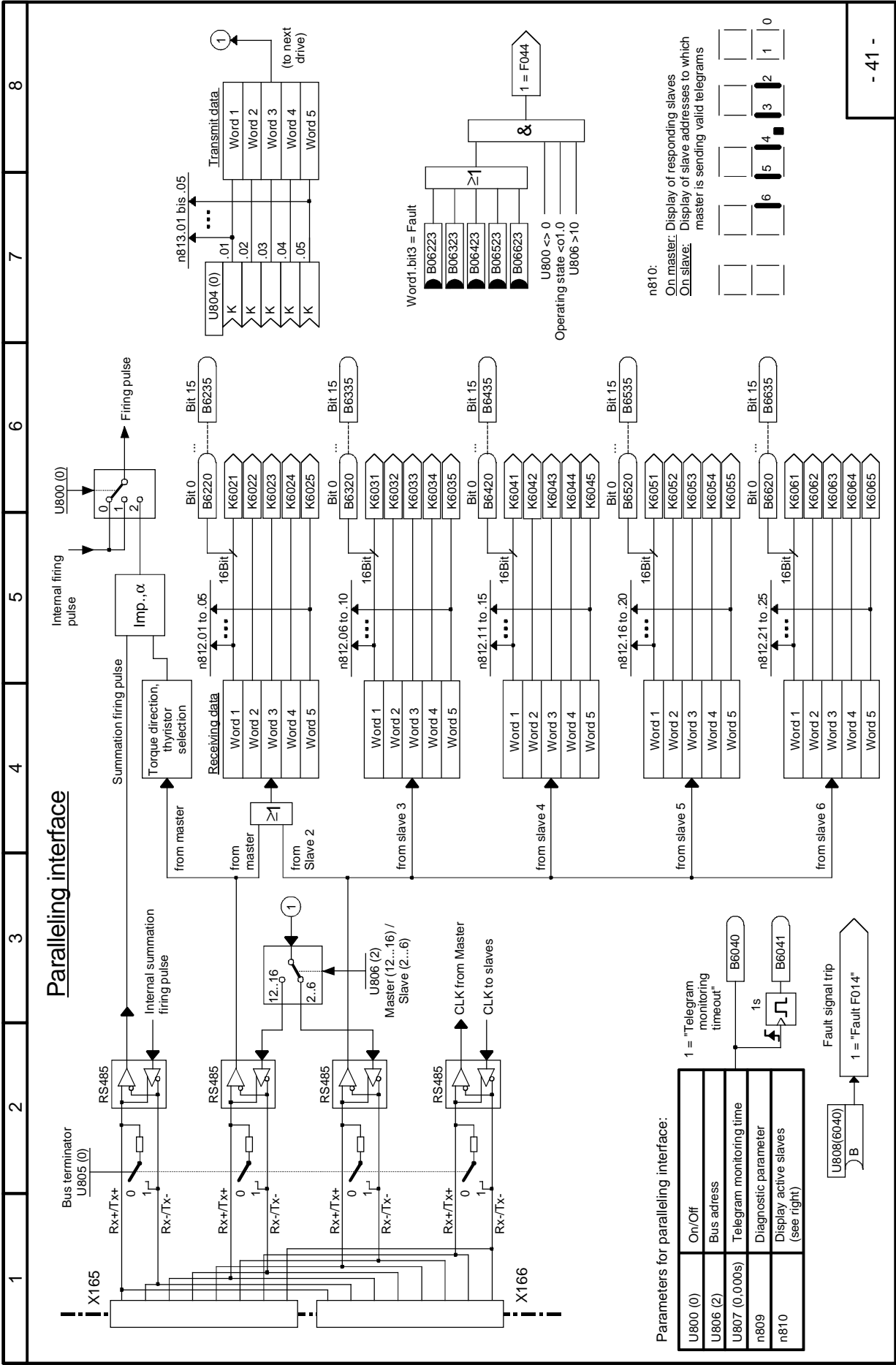
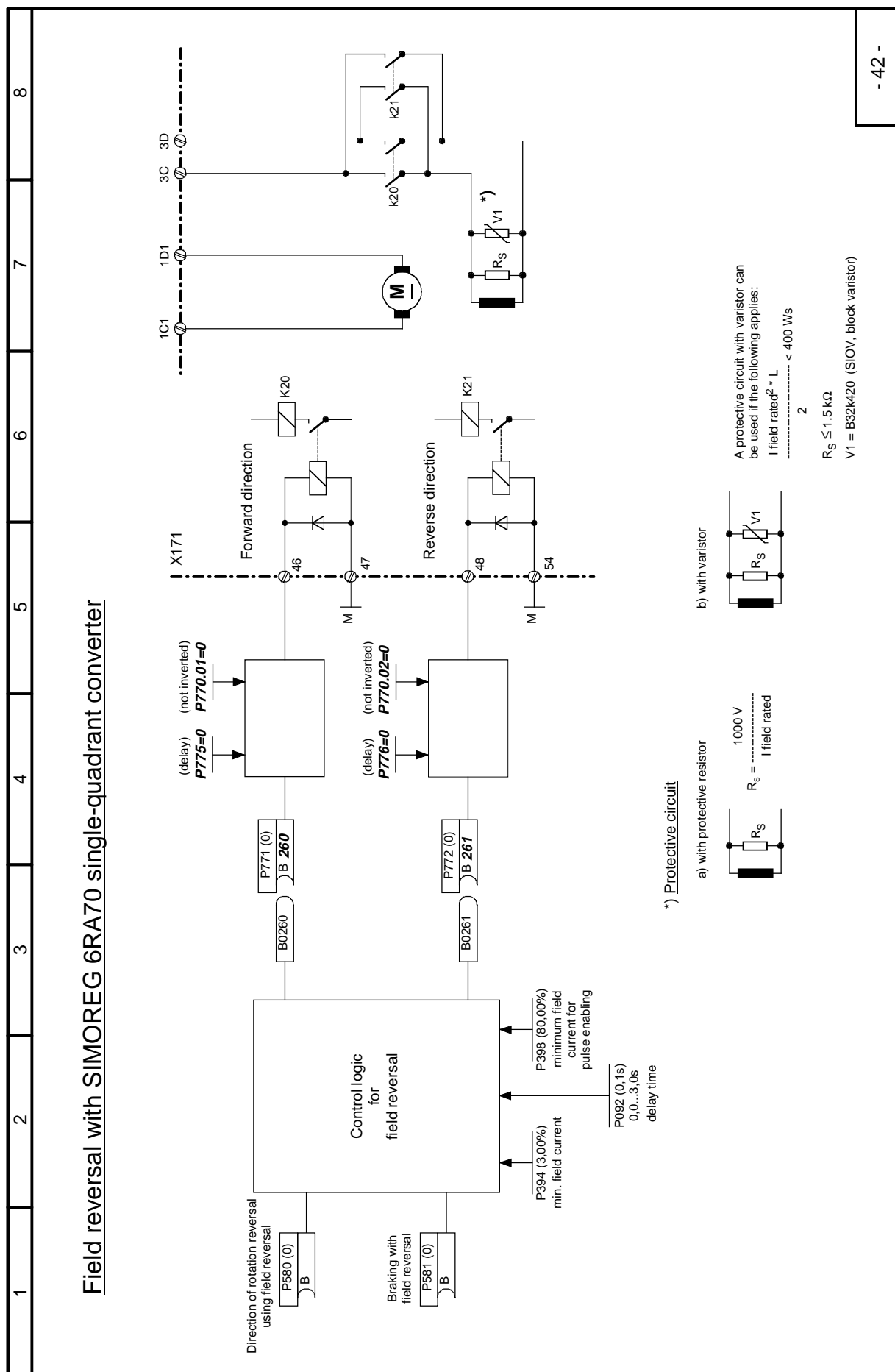
## Sheet 42 Field reversal with SIMOREG 6RA70 single-quadrant converter





## Freely assignable function blocks Sheets B1 to B24


(Technology software in the basic converter, S00 option)
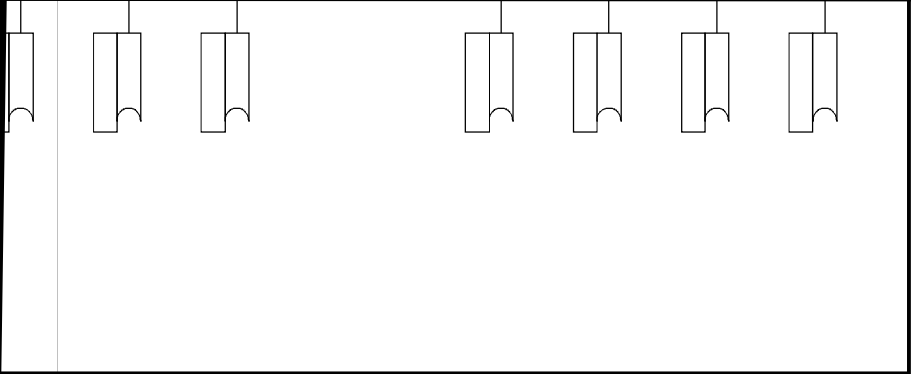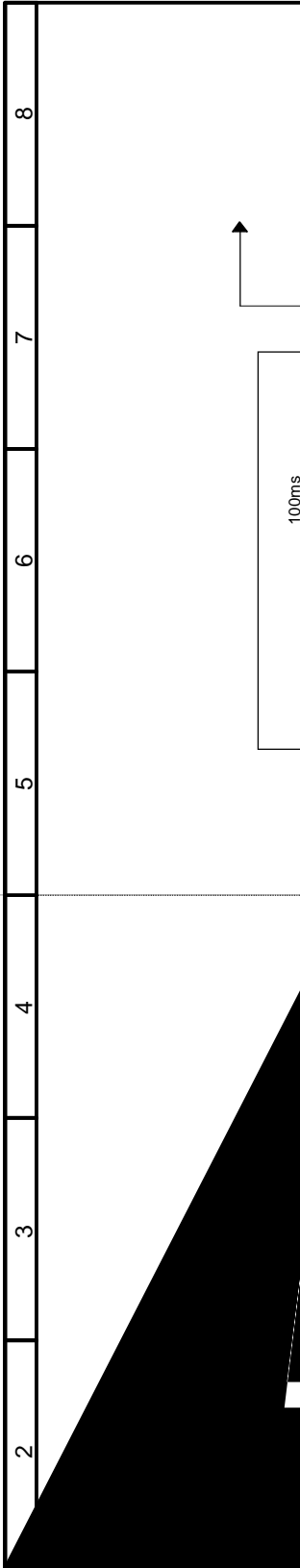
### NOTE

Freely assignable function blocks are enabled in parameter U977.  
For enabling instructions, please refer to Section 11, Parameter List, description of parameters U977 and n978.





Sheet B2 Connector / binector converters

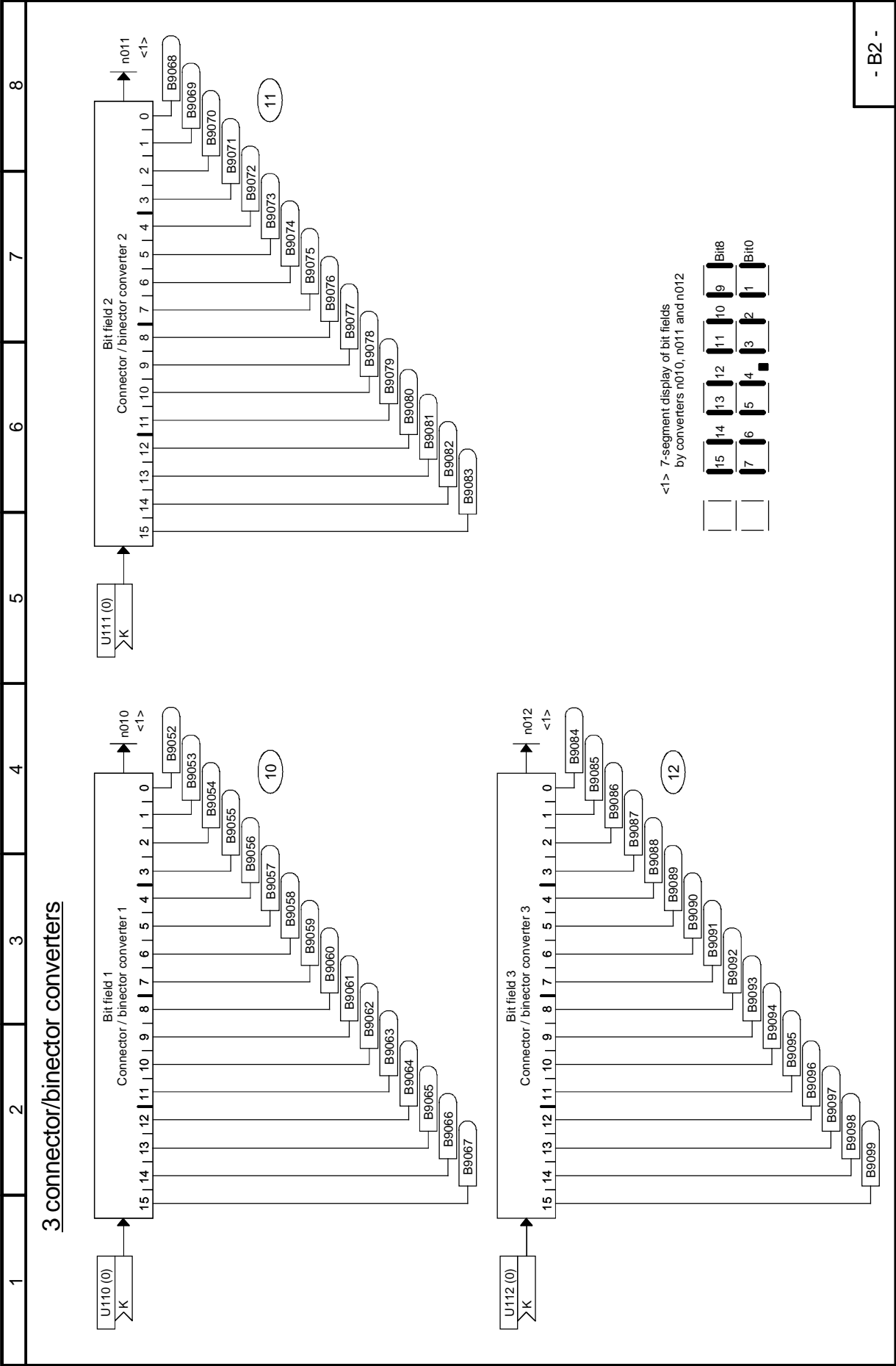



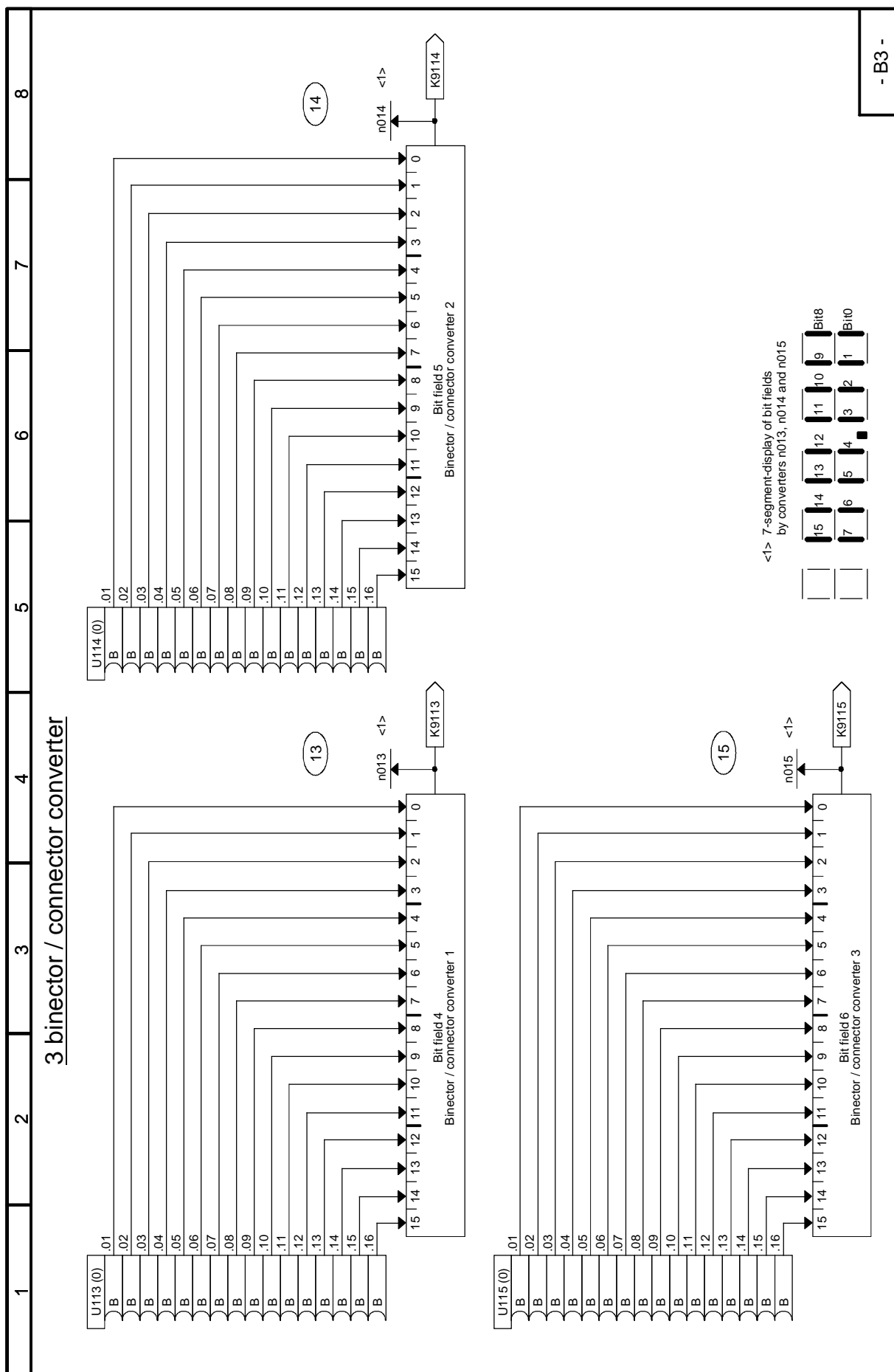
## Sheet B3 Binector / connector converters



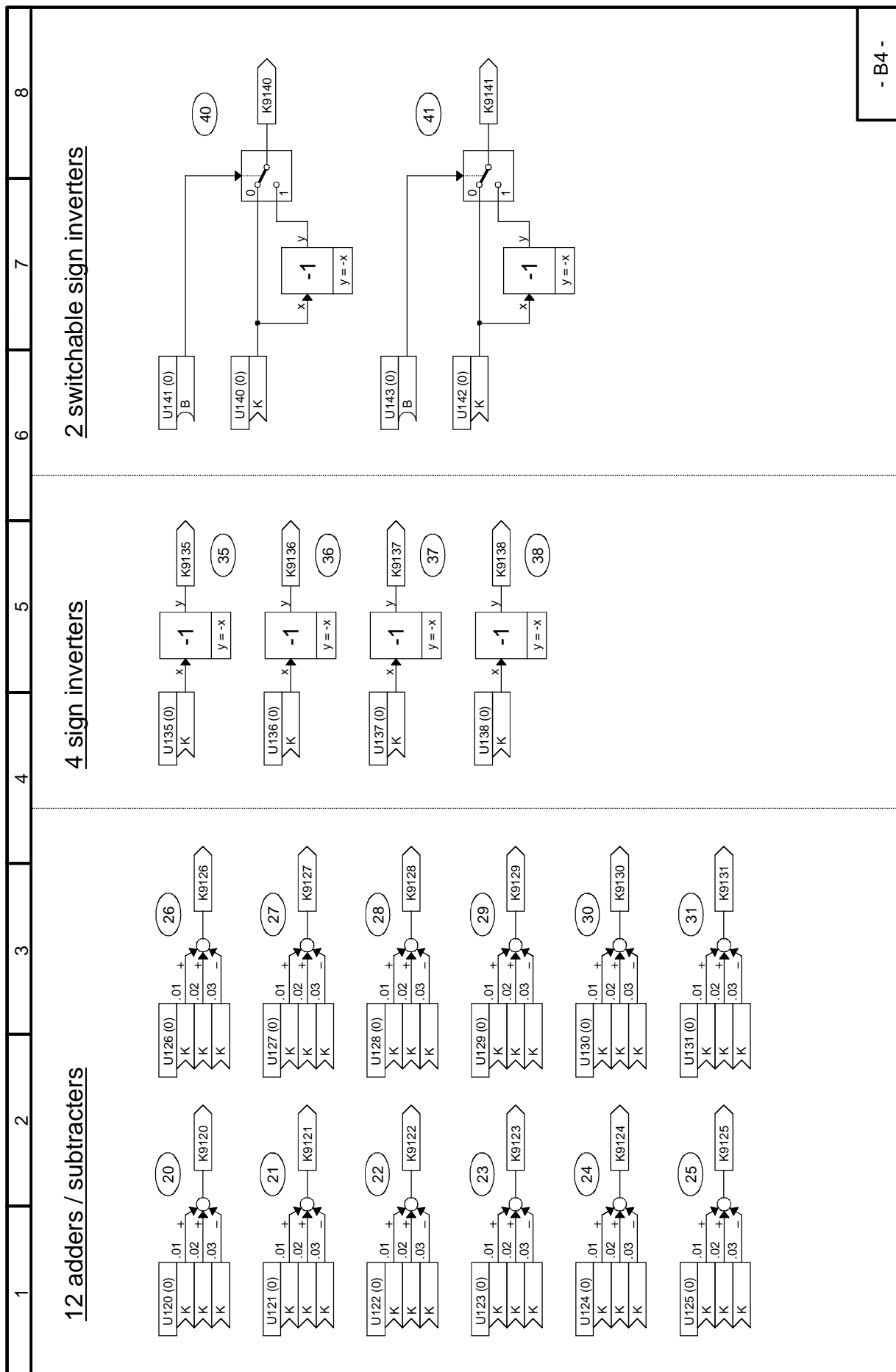
**Sheet B4 Adders / subtracters, sign inverters**


- B4 -

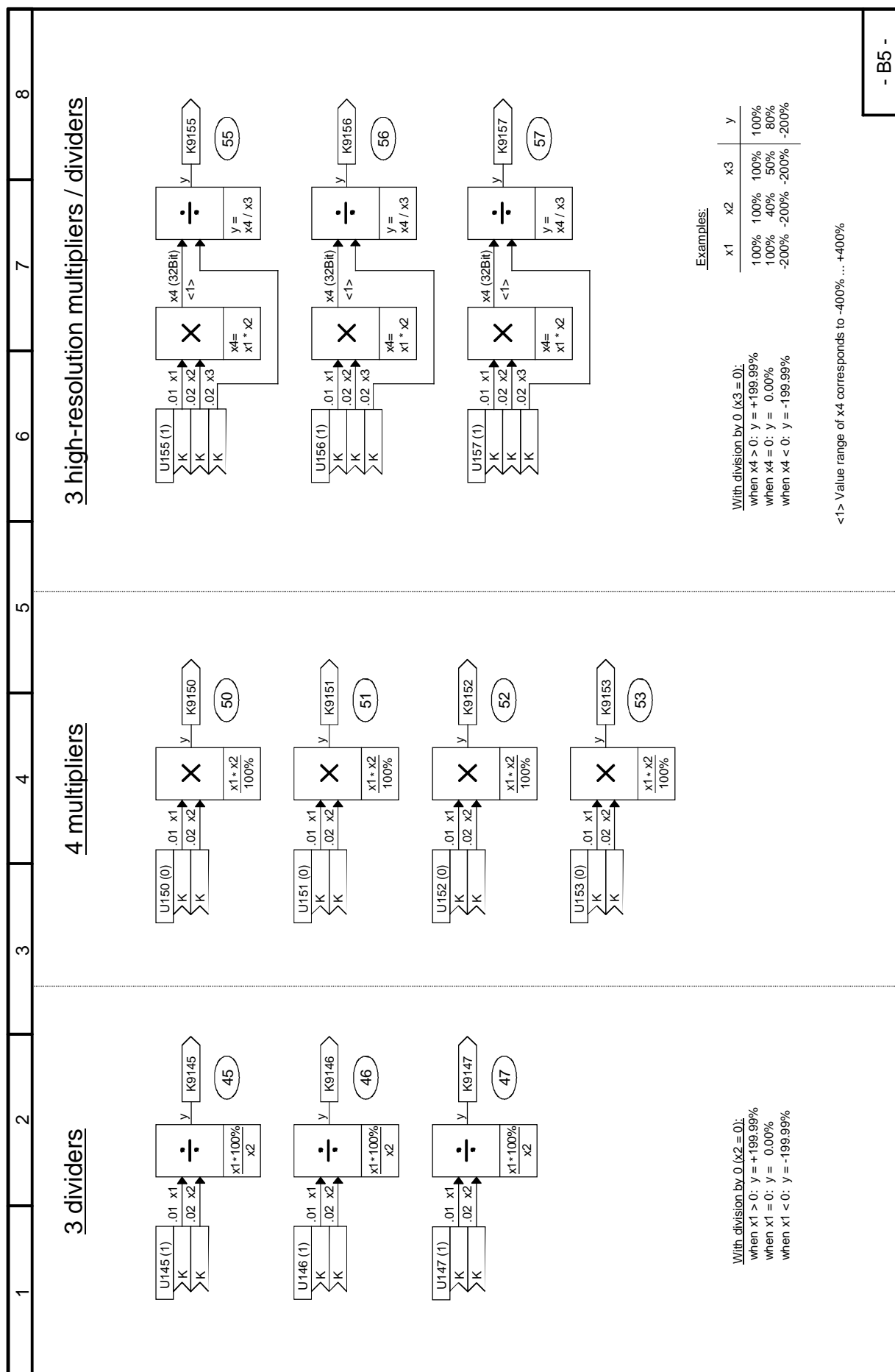
**Sheet B5 Dividers, multipliers, high-resolution multipliers / dividers**


- B5 -

## 8-52

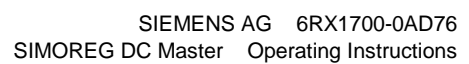
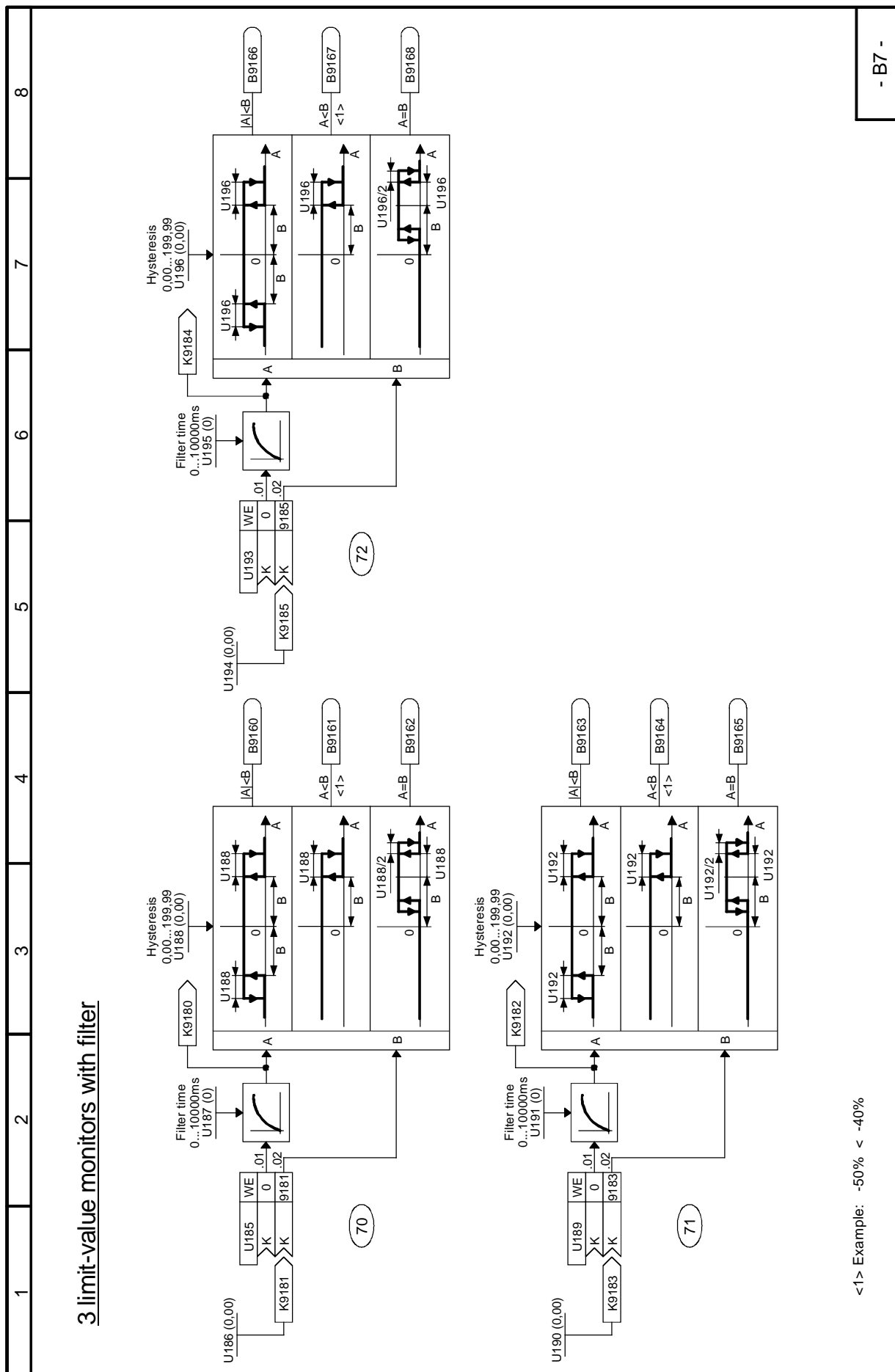
## Sheet B7 Limit-value monitors with filter




SIEMENS AG 6RX1700-0AD76  
SIMOREG DC Master Operating Instructions

**4 limit-value monitors without filter**

The diagrams illustrate four limit-value monitors (73, 74, 75, 76) without a filter. Each monitor consists of three rungs for comparison and a hysteresis block.


- Monitor 73:** Uses comparators U199 and U205. The hysteresis block is labeled "Hysteresis 0.00...199.99 U199 (0.00)". The limit switch block is K9186.
- Monitor 74:** Uses comparators U202 and U208. The hysteresis block is labeled "Hysteresis 0.00...199.99 U202 (0.00)". The limit switch block is K9187.
- Monitor 75:** Uses comparators U205 and U205/2. The hysteresis block is labeled "Hysteresis 0.00...199.99 U205 (0.00)". The limit switch block is K9188.
- Monitor 76:** Uses comparators U208 and U208/2. The hysteresis block is labeled "Hysteresis 0.00...199.99 U208 (0.00)". The limit switch block is K9189.

Each diagram shows the logic for monitoring the difference between two signals, A and B, and triggering an alarm when the difference exceeds a setpoint (K9186, K9187, K9188, or K9189) within a specified hysteresis range.

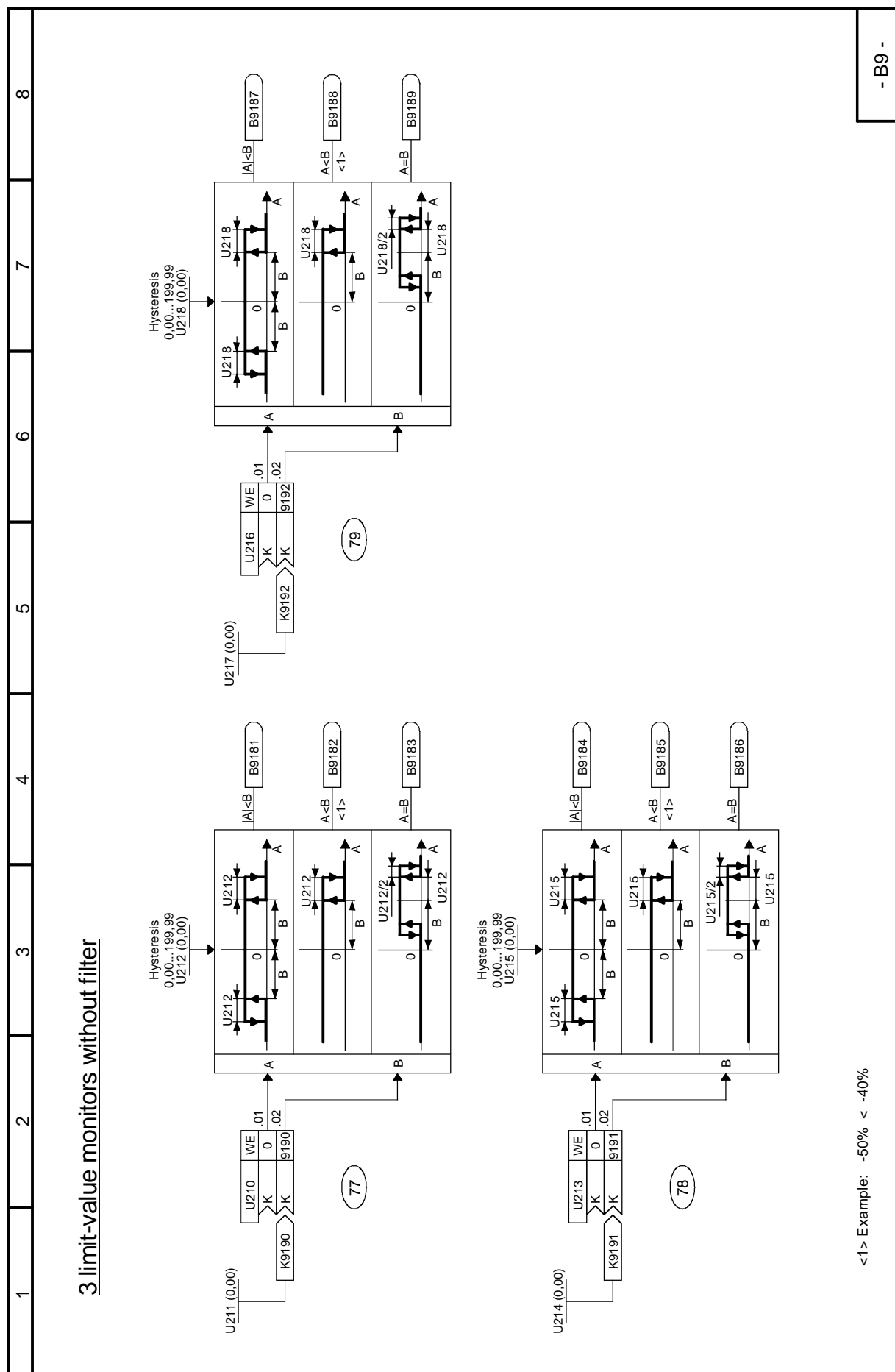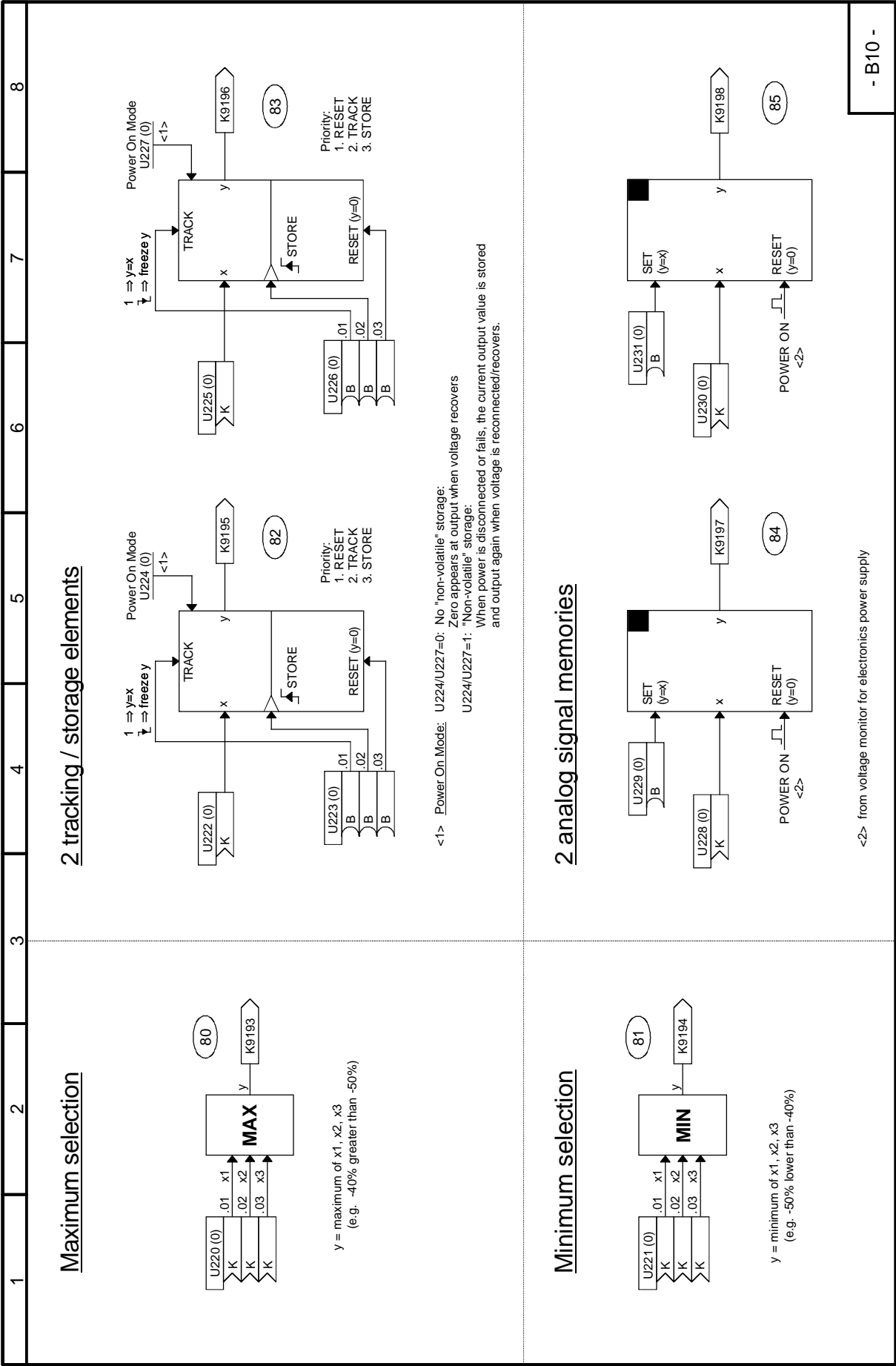**Sheet B9**    **Limit-value monitors without filter**


Sheet B10

Maximum selection, minimum selection, tracking / storage elements,  
analog signal memories




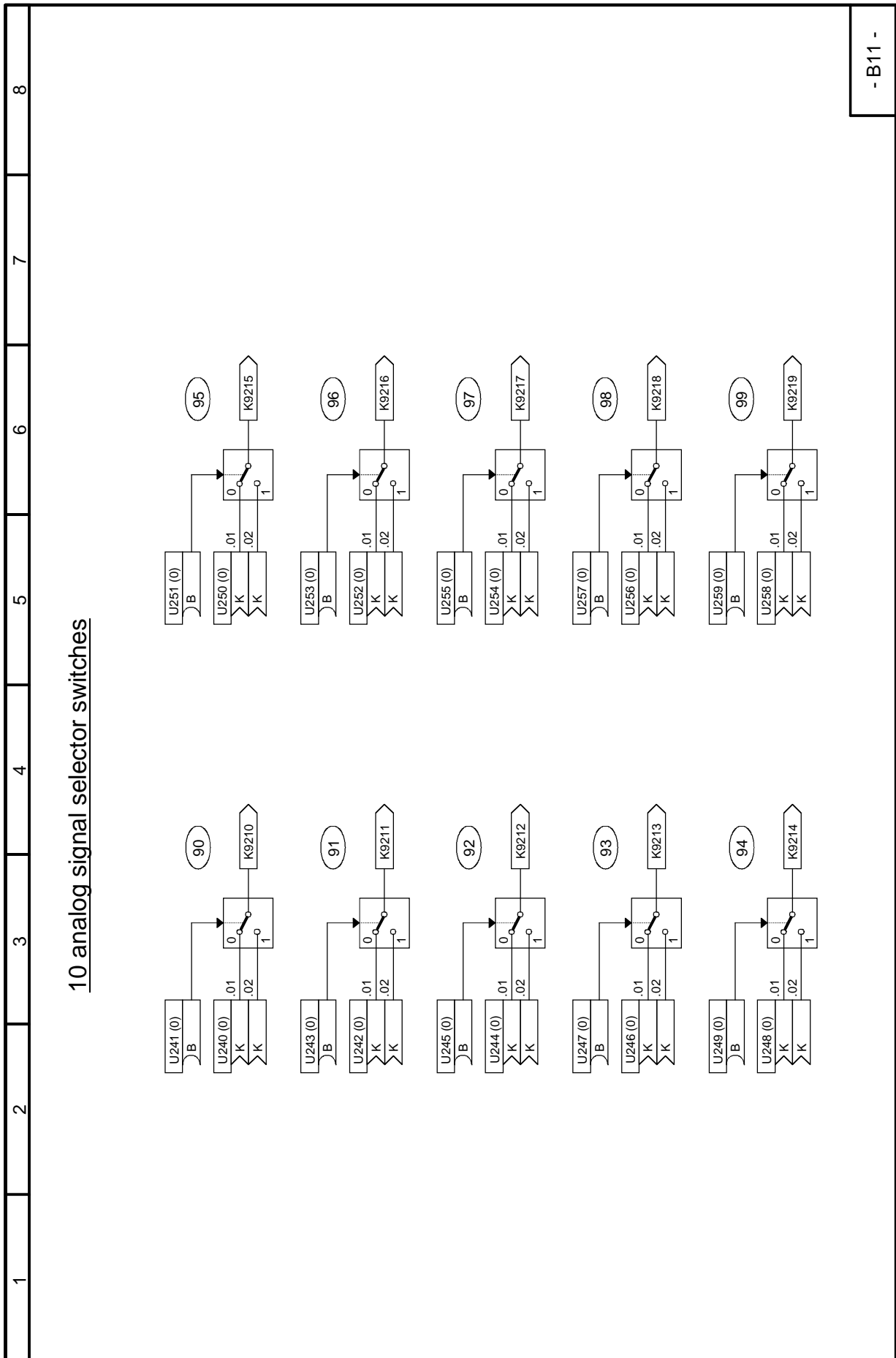
## Sheet B11 Analog signal selector switches



8-58

SIEMENS AG 6RX1700-0AD76  
SIMOREG DC Master Operating Instructions

## Sheet B13 Characteristic blocks, dead zones, setpoint branching

1

2

3

4

5

6

7

8

### 3 characteristic blocks


### 3 dead zones

### Setpoint branching


- B13 -


		3	4
--	--	---	---

Simple ramp-function generator

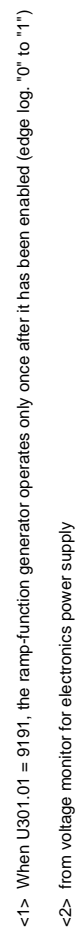


## Sheet B15 Technology controller

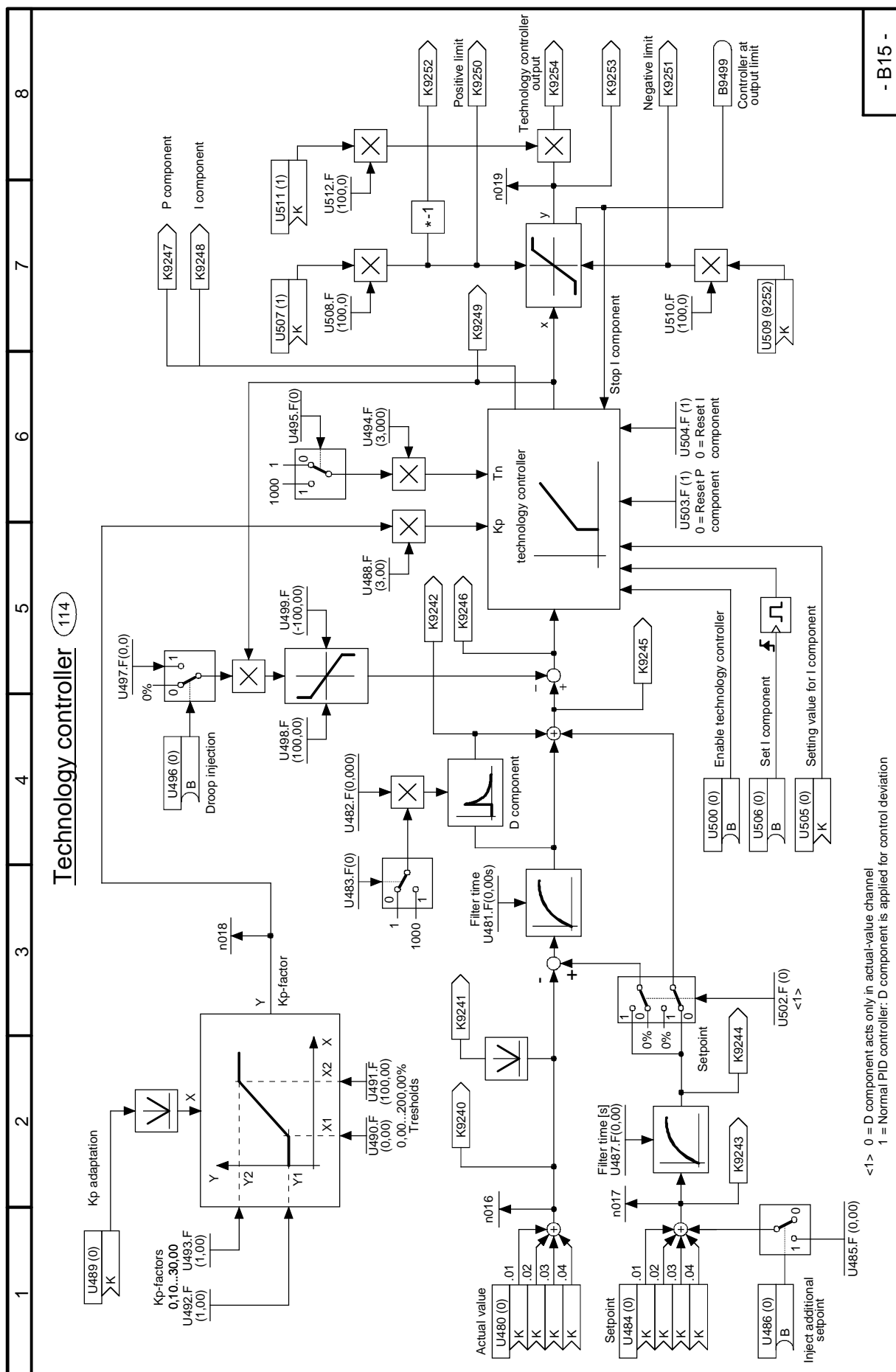

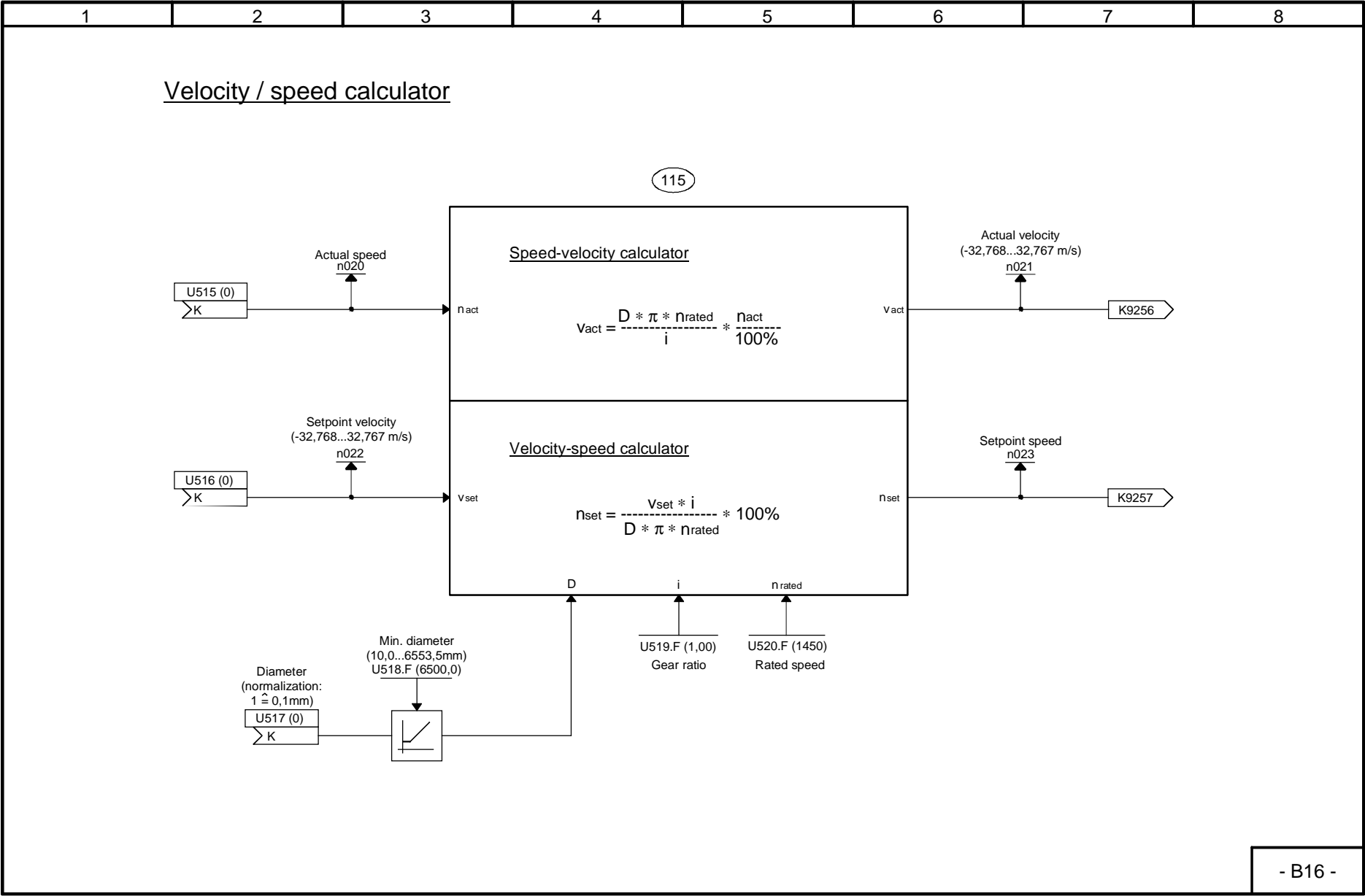

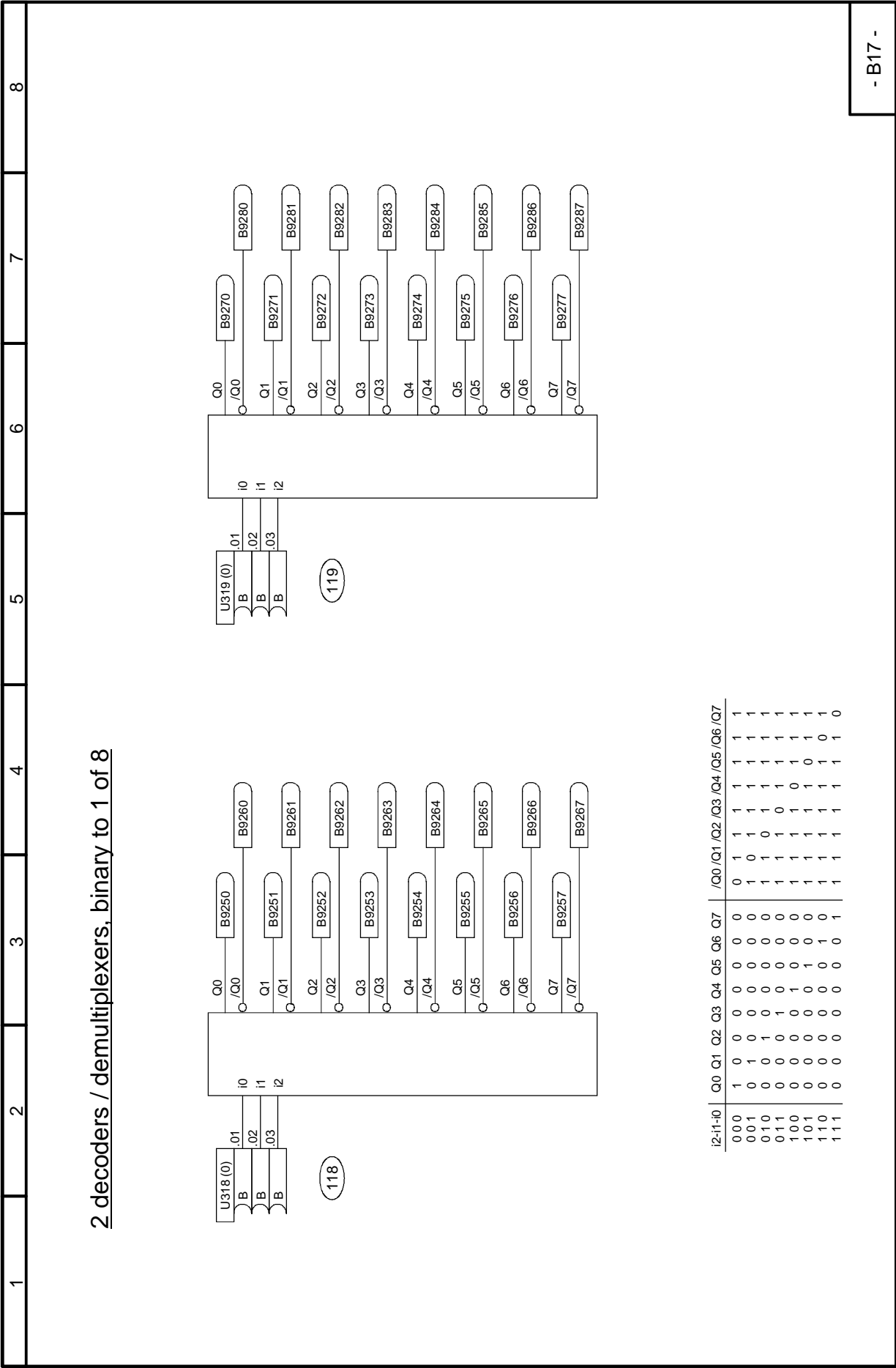Sheet B17    Decoders / demultiplexers, binary to 1 of 8



Sheet B18 AND elements

1	2	3	4	5	6	7	8
28 AND elements with 3 inputs each							
							- B18 -



## Sheet B19 OR-elements, EXCLUSIV OR elements

1	2	3	4	5	6	7	8
20 OR elements with 3 inputs each				4 EXCLUSIV OR elements with 2 inputs each			

- B19 -

Sheet B20    Inverters, NAND elements

1	2	3	4	5	6	7	8
16 inverters				12 NAND elements with 3 inputs each			
<div><div>U380 (0) B</div><div>1</div><div>B9450</div><div>180</div></div> <div><div>U381 (0) B</div><div>1</div><div>B9451</div><div>181</div></div> <div><div>U382 (0) B</div><div>1</div><div>B9452</div><div>182</div></div> <div><div>U383 (0) B</div><div>1</div><div>B9453</div><div>183</div></div> <div><div>U384 (0) B</div><div>1</div><div>B9454</div><div>184</div></div> <div><div>U385 (0) B</div><div>1</div><div>B9455</div><div>185</div></div> <div><div>U386 (0) B</div><div>1</div><div>B9456</div><div>186</div></div> <div><div>U387 (0) B</div><div>1</div><div>B9457</div><div>187</div></div> <div><div>U388 (0) B</div><div>1</div><div>B9458</div><div>188</div></div> <div><div>U389 (0) B</div><div>1</div><div>B9459</div><div>189</div></div> <div><div>U390 (0) B</div><div>1</div><div>B9460</div><div>190</div></div> <div><div>U391 (0) B</div><div>1</div><div>B9461</div><div>191</div></div> <div><div>U392 (0) B</div><div>1</div><div>B9462</div><div>192</div></div> <div><div>U393 (0) B</div><div>1</div><div>B9463</div><div>193</div></div> <div><div>U394 (0) B</div><div>1</div><div>B9464</div><div>194</div></div> <div><div>U395 (0) B</div><div>1</div><div>B9465</div><div>195</div></div>				<div><div>U400 (1) B B B</div><div>&amp;</div><div>B9470</div><div>200</div></div> <div><div>U401 (1) B B B</div><div>&amp;</div><div>B9471</div><div>201</div></div> <div><div>U402 (1) B B B</div><div>&amp;</div><div>B9472</div><div>202</div></div> <div><div>U403 (1) B B B</div><div>&amp;</div><div>B9473</div><div>203</div></div> <div><div>U404 (1) B B B</div><div>&amp;</div><div>B9474</div><div>204</div></div> <div><div>U405 (1) B B B</div><div>&amp;</div><div>B9475</div><div>205</div></div> <div><div>U406 (1) B B B</div><div>&amp;</div><div>B9476</div><div>206</div></div> <div><div>U407 (1) B B B</div><div>&amp;</div><div>B9477</div><div>207</div></div> <div><div>U408 (1) B B B</div><div>&amp;</div><div>B9478</div><div>208</div></div> <div><div>U409 (1) B B B</div><div>&amp;</div><div>B9479</div><div>209</div></div> <div><div>U410 (1) B B B</div><div>&amp;</div><div>B9480</div><div>210</div></div> <div><div>U411 (1) B B B</div><div>&amp;</div><div>B9481</div><div>211</div></div>			
- B20 -							

U382 (0)

B

1

B9452

182

U383 (0)

B

1

B9453

183

U384 (0)

B

1

B9454

184

U385 (0)

B

1

B9455

185

U386 (0)

B

1

B9456

186

U387 (0)

B

1

B9457

187

U388 (0)

B

1

B9458

188

U389 (0)

B

1

B9459

189

U390 (0)

B

1

B9460

190

U391 (0)

B

1

B9461

191

U392 (0)

B

1

B9462

192

U393 (0)

B

1

B9463

193

U394 (0)

B

1

B9464

194

U395 (0)


B

1

B9465


195

14 RS flops

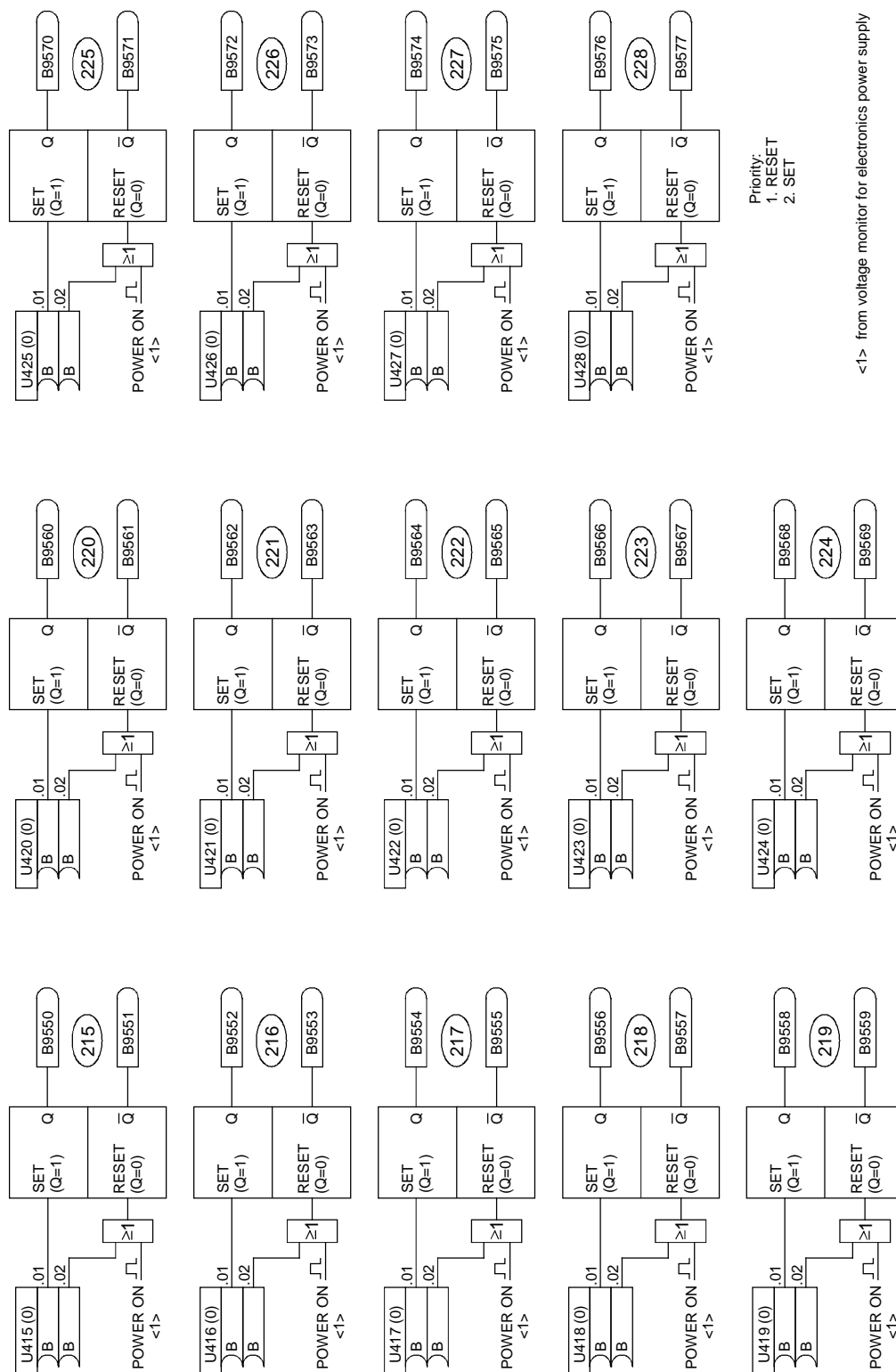


-B21 -


Sheet B22 D flipflops

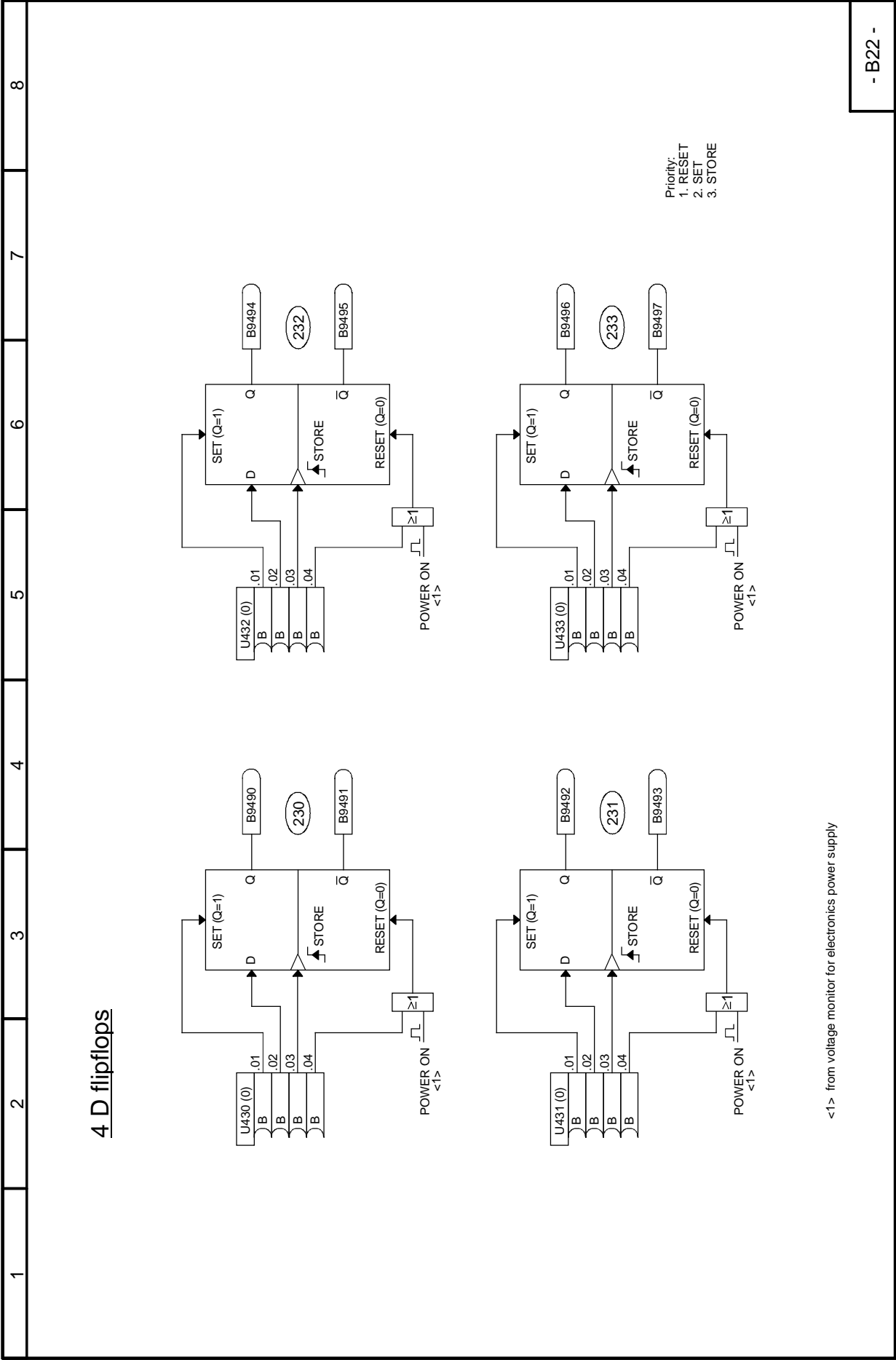

## Sheet B23 Timers (0,000...60,000s)

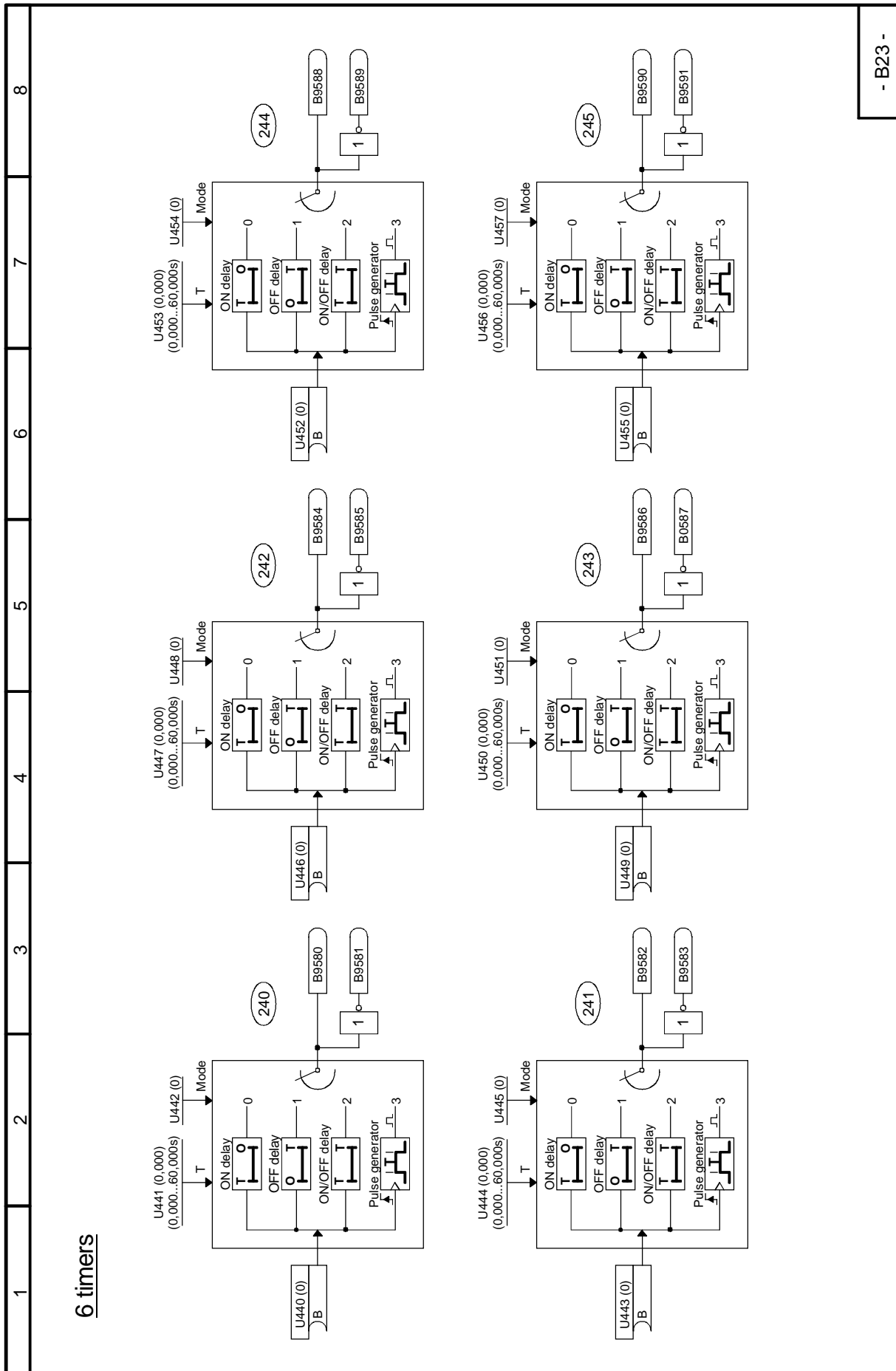


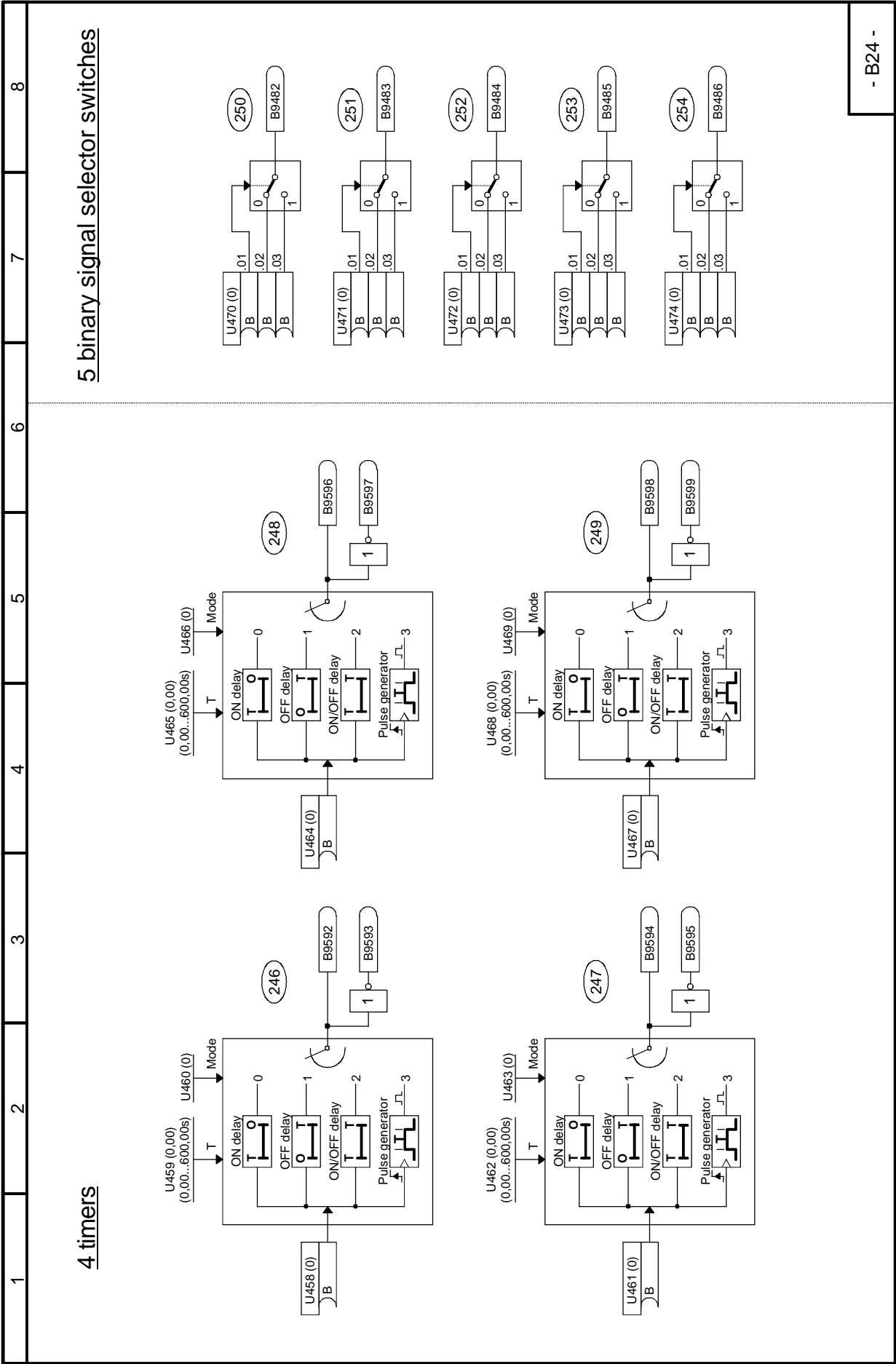Sheet B24 Timers (0,00...600,00s), binary signal selector switches




## Optional supplementary boards    Sheets Z1 to Z12

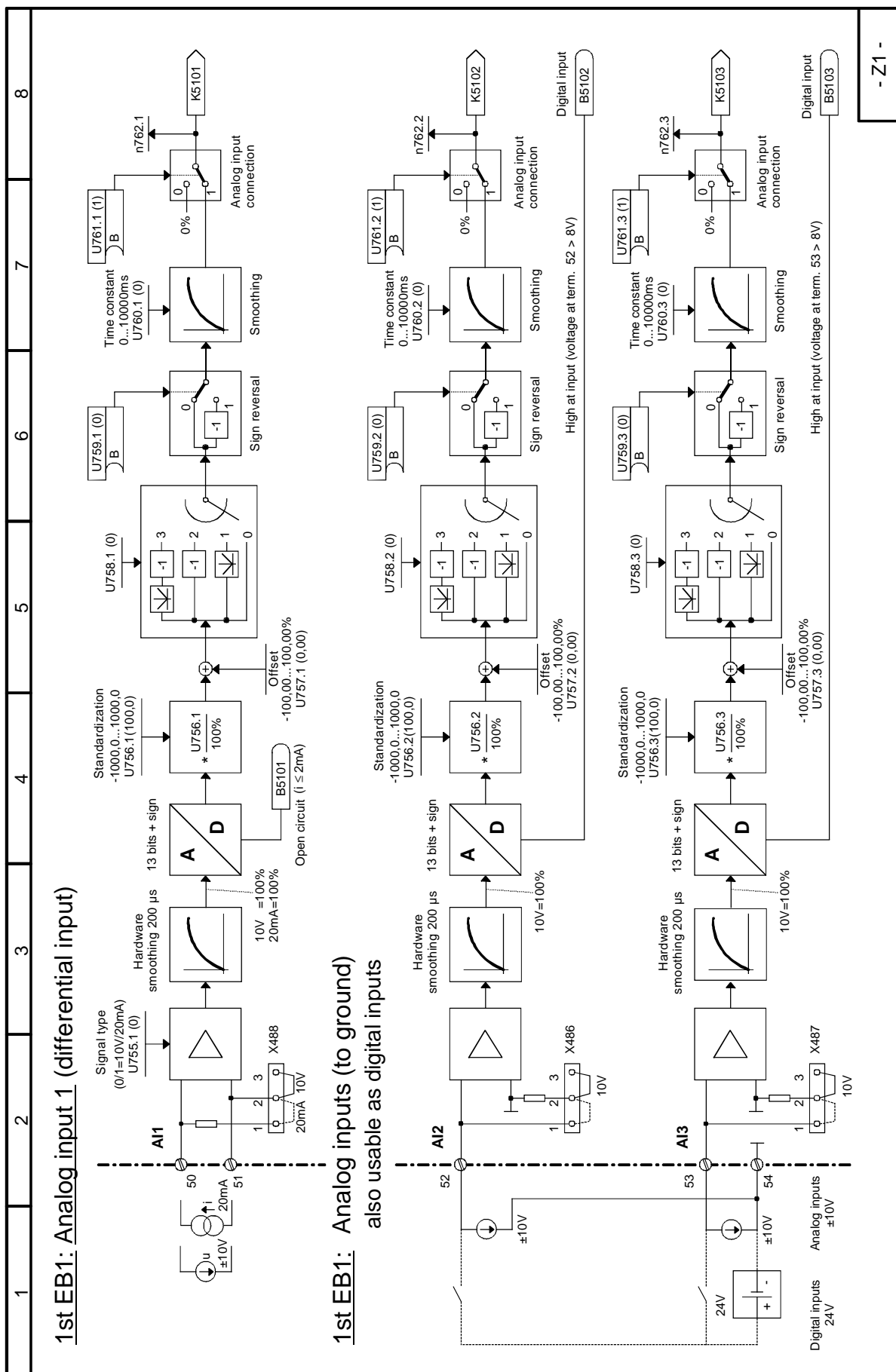**Sheet Z1    1<sup>st</sup> EB1: Analog inputs**




Sheet Z2 1<sup>st</sup> EB1: Analog outputs


1<sup>st</sup> EB1: Analog outputs

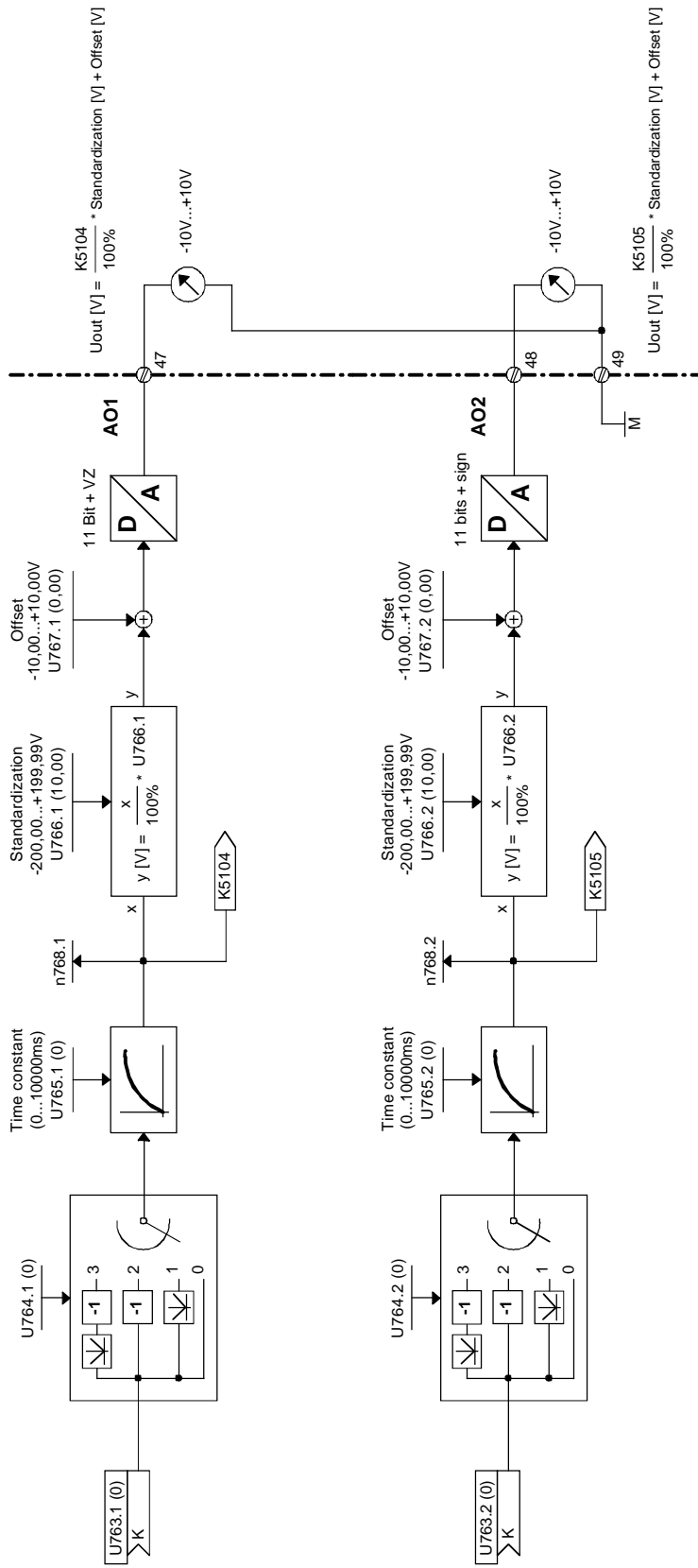


- Z2 -

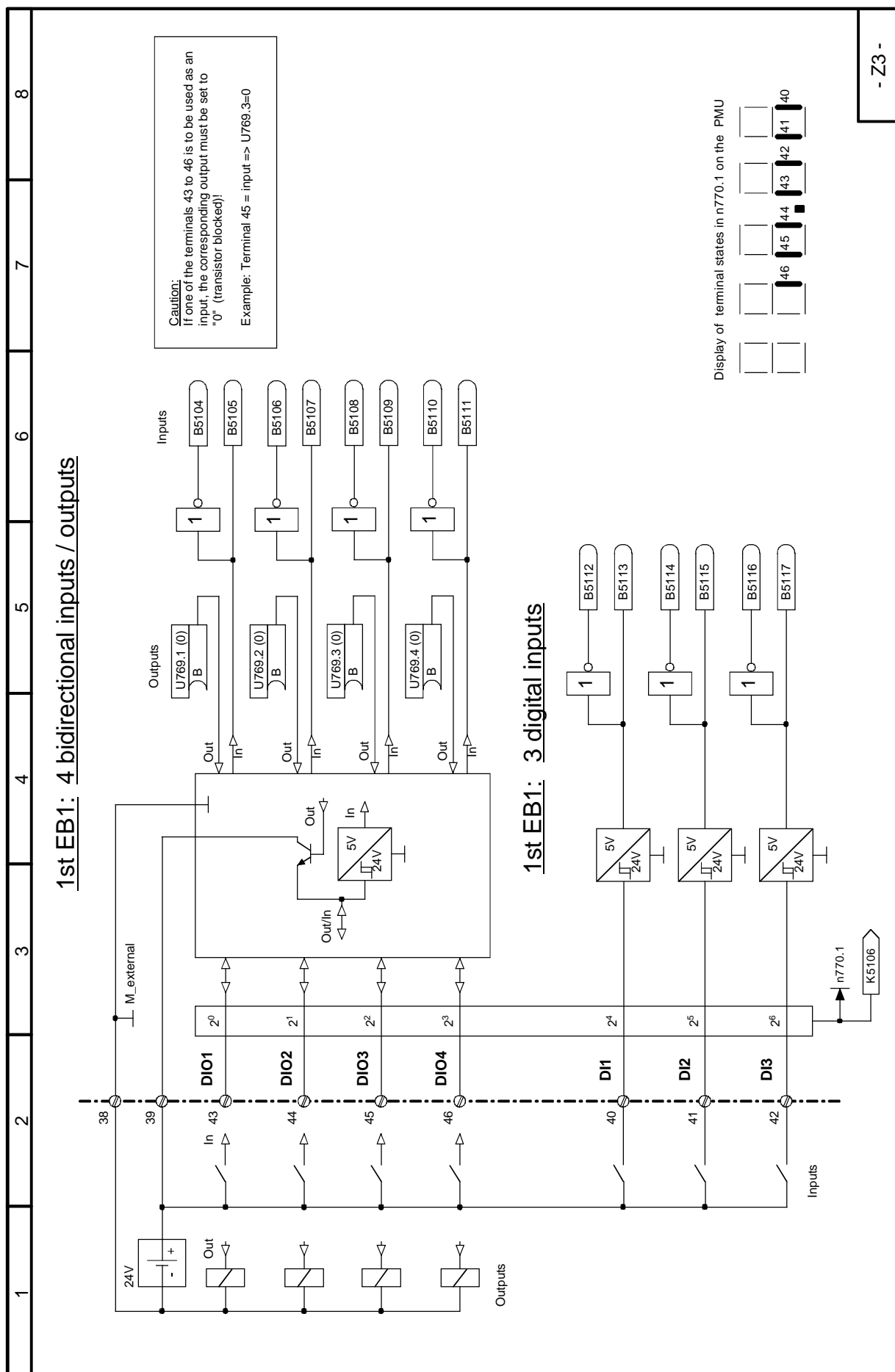

**Sheet Z3 1<sup>st</sup> EB1: 4 bidirectional inputs- / outputs, 3 digital inputs**

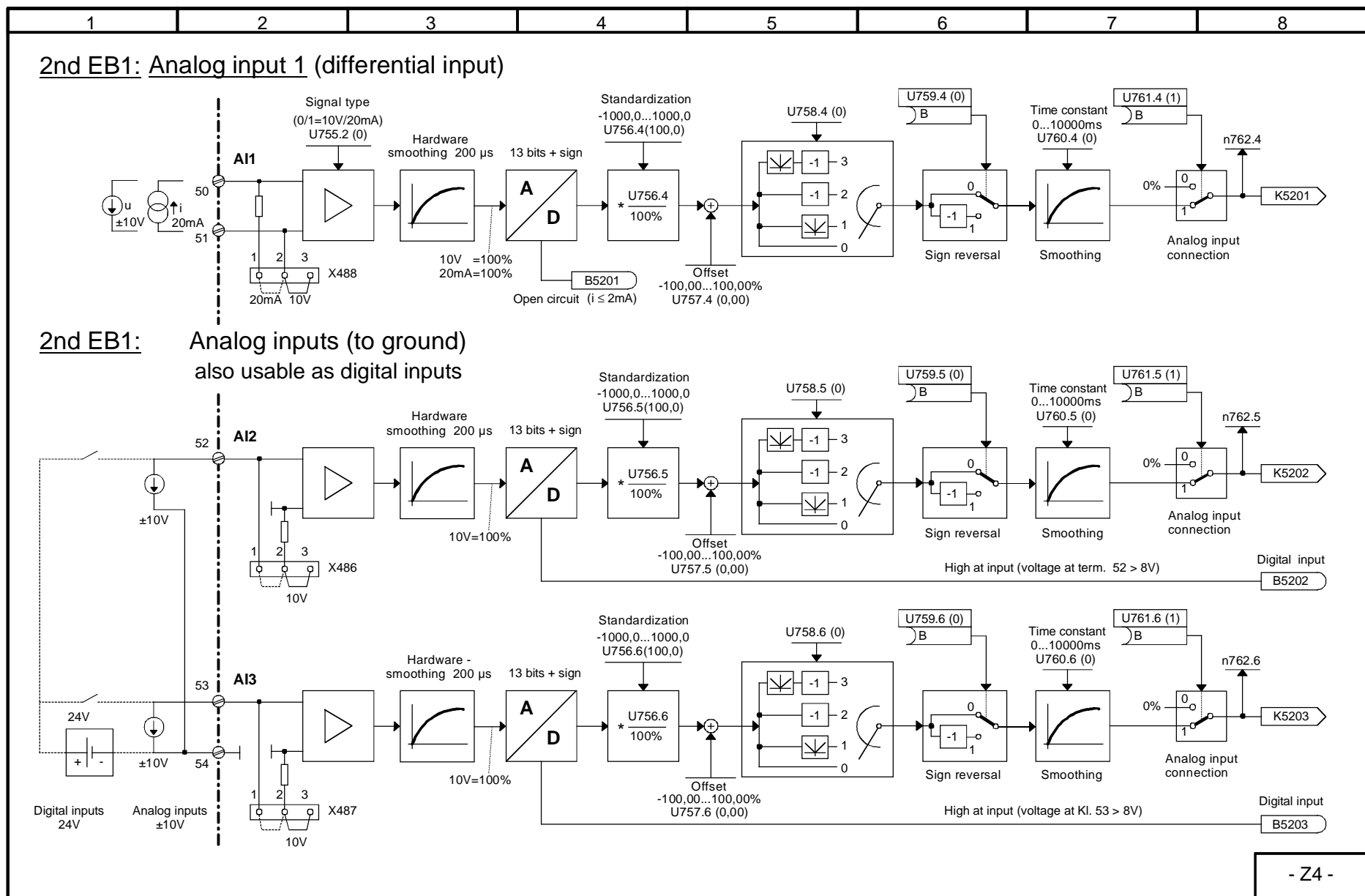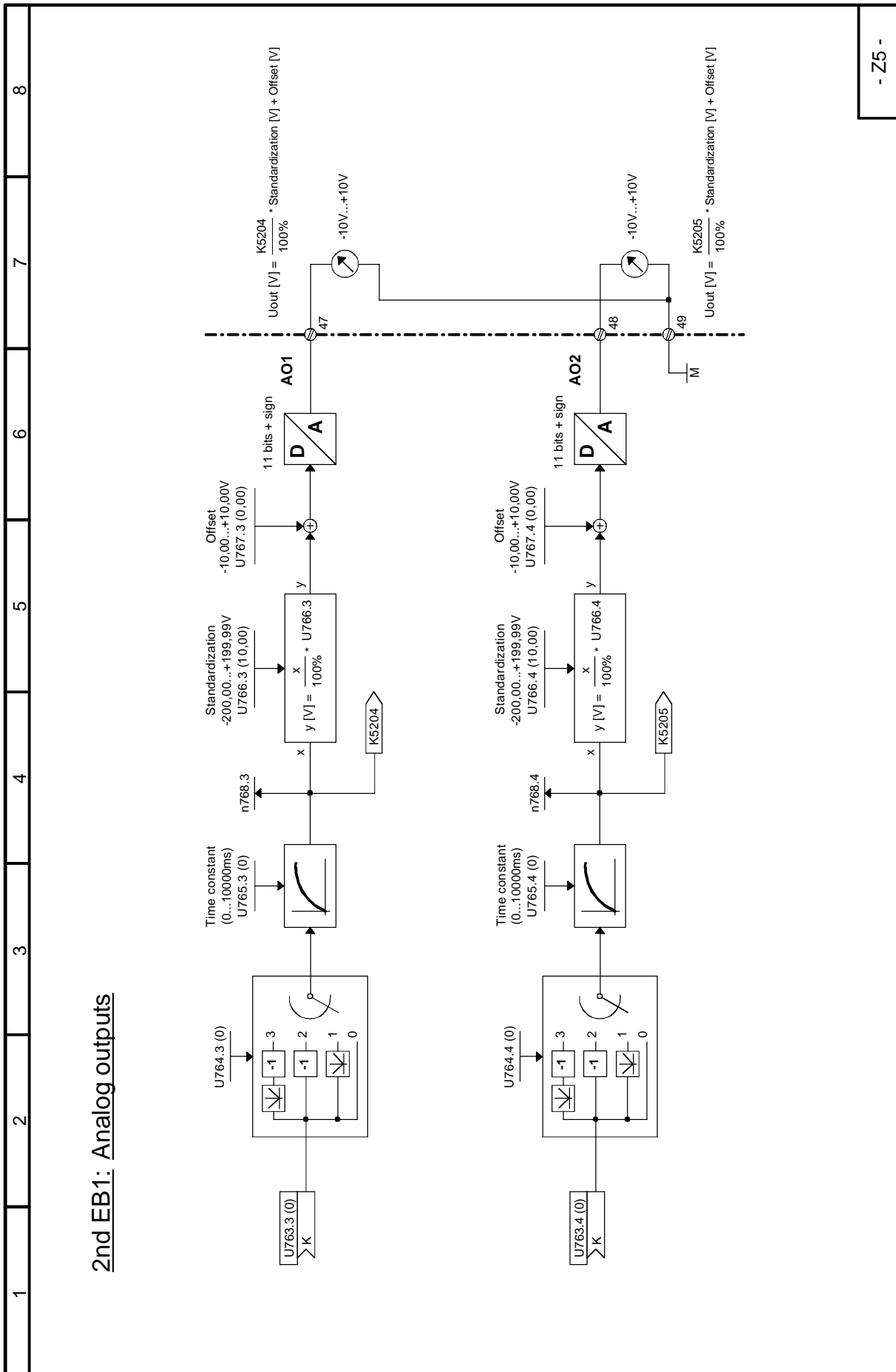
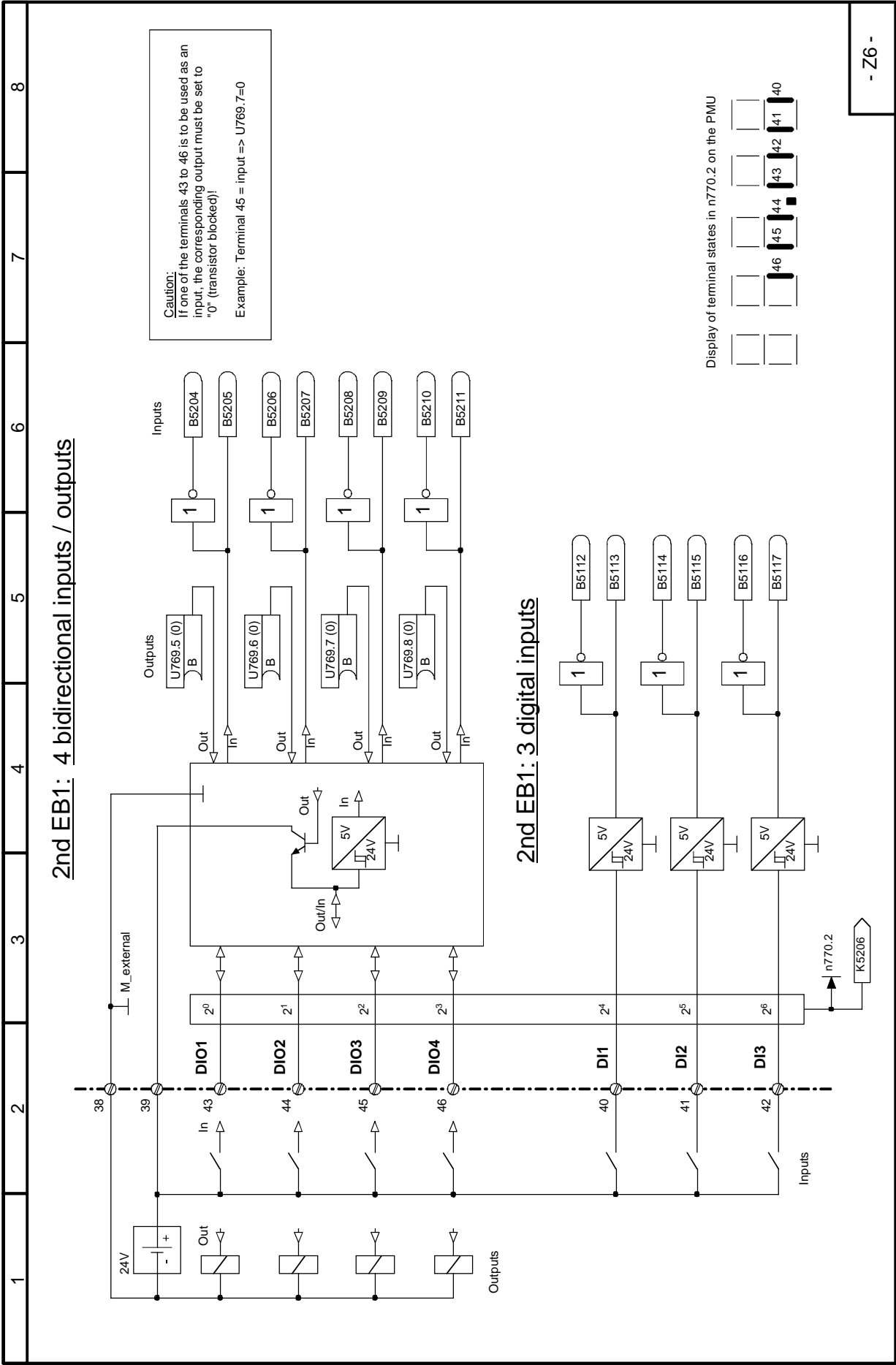


Sheet Z5 2<sup>nd</sup> EB1: Analog outputs


- Z5 -

Sheet Z6


2<sup>nd</sup> EB1: 4 bidirectional inputs- / outputs, 3 digital inputs


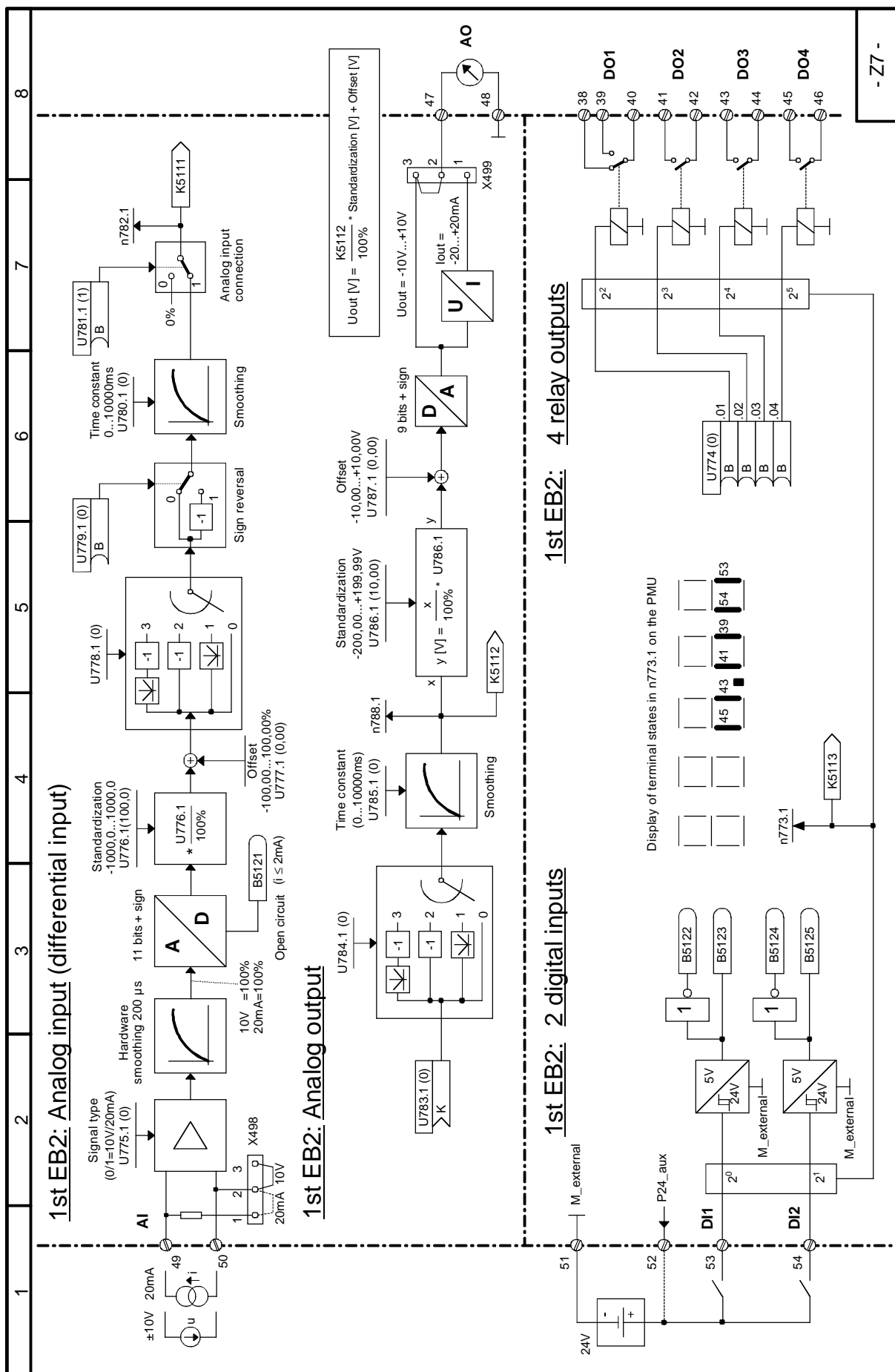
# Sheet Z7 1<sup>st</sup> EB2: Analog input, Analog output, 2 digital inputs, 4 relay outputs




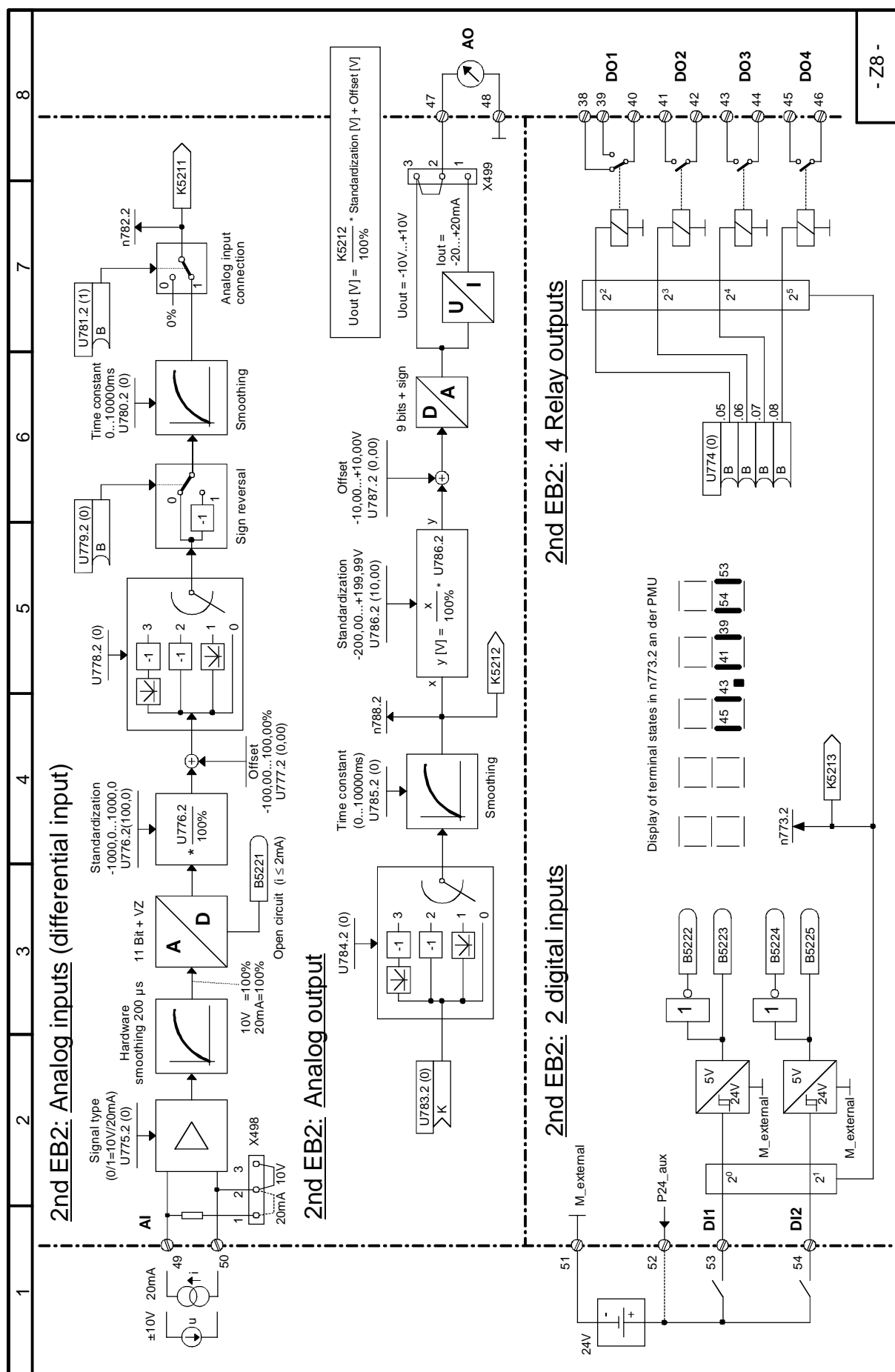SIEMENS AG 6RX1700-0AD76  
SIMOREG DC Master Operating Instructions



**Sheet Z9      SBP pulse encoder evaluation**

## SBP\_pulse encoder evaluation

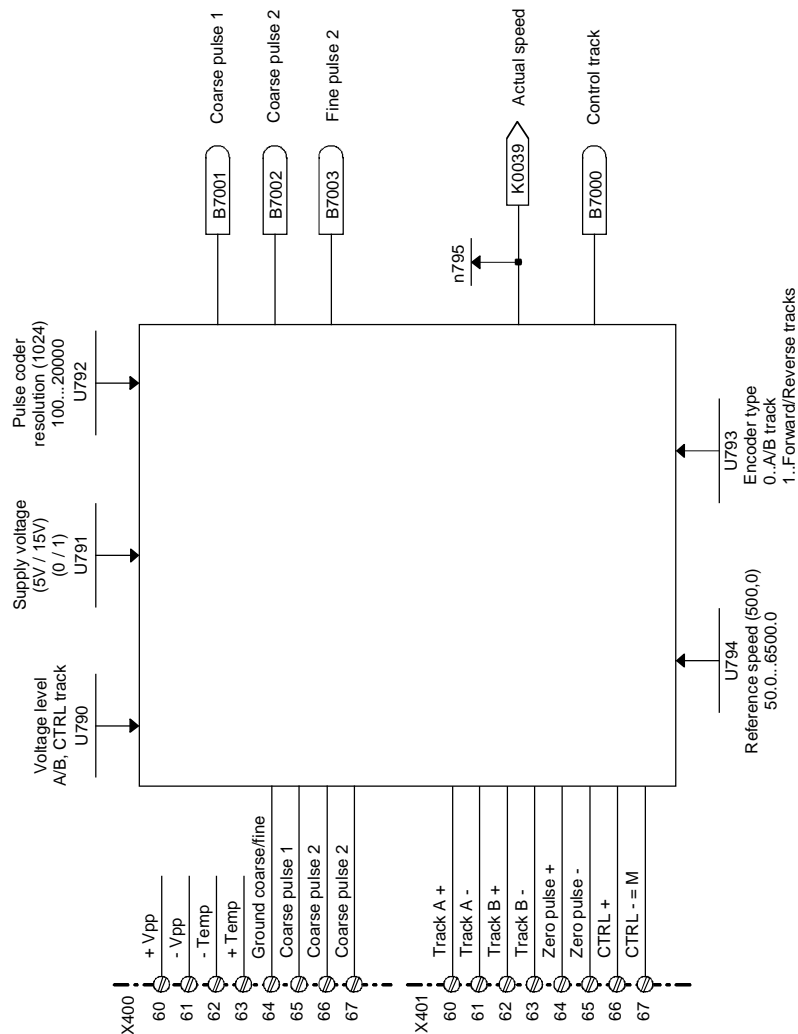

**X400 terminal assignments:**


Term.	Name	Meaning
60	+ Vpp	Pulse encoder power supply
61	- Vpp	Power supply ground
62	- Temp	Neg. (-) term. KTY84/PTC100
63	+ Temp	Pos. (+) term. KTY84/PTC100
64	Ground coarse/fine	Ground
65	Coarse pulse 1	Digital input coarse pulse 1
66	Coarse pulse 2	Digital input coarse pulse 2
67	Fine pulse 2	Digital input fine pulse 2

X401 terminal assignments:

Term.	Name	Meaning
68	Track A +	Pos. (+) term. track A
69	Track A -	Neg. (-) term. track A
70	Track B +	Pos. (+) term. track B
71	Track B -	Neg. (-) term. track B
72	Zero pulse +	Pos. (+) zero pulse
73	Zero pulse -	Neg. (-) zero pulse
74	CTRL +	Pos. (+) term. control track
75	CTRL -	Neg. (-) term. control track (=ground)


- 67 -

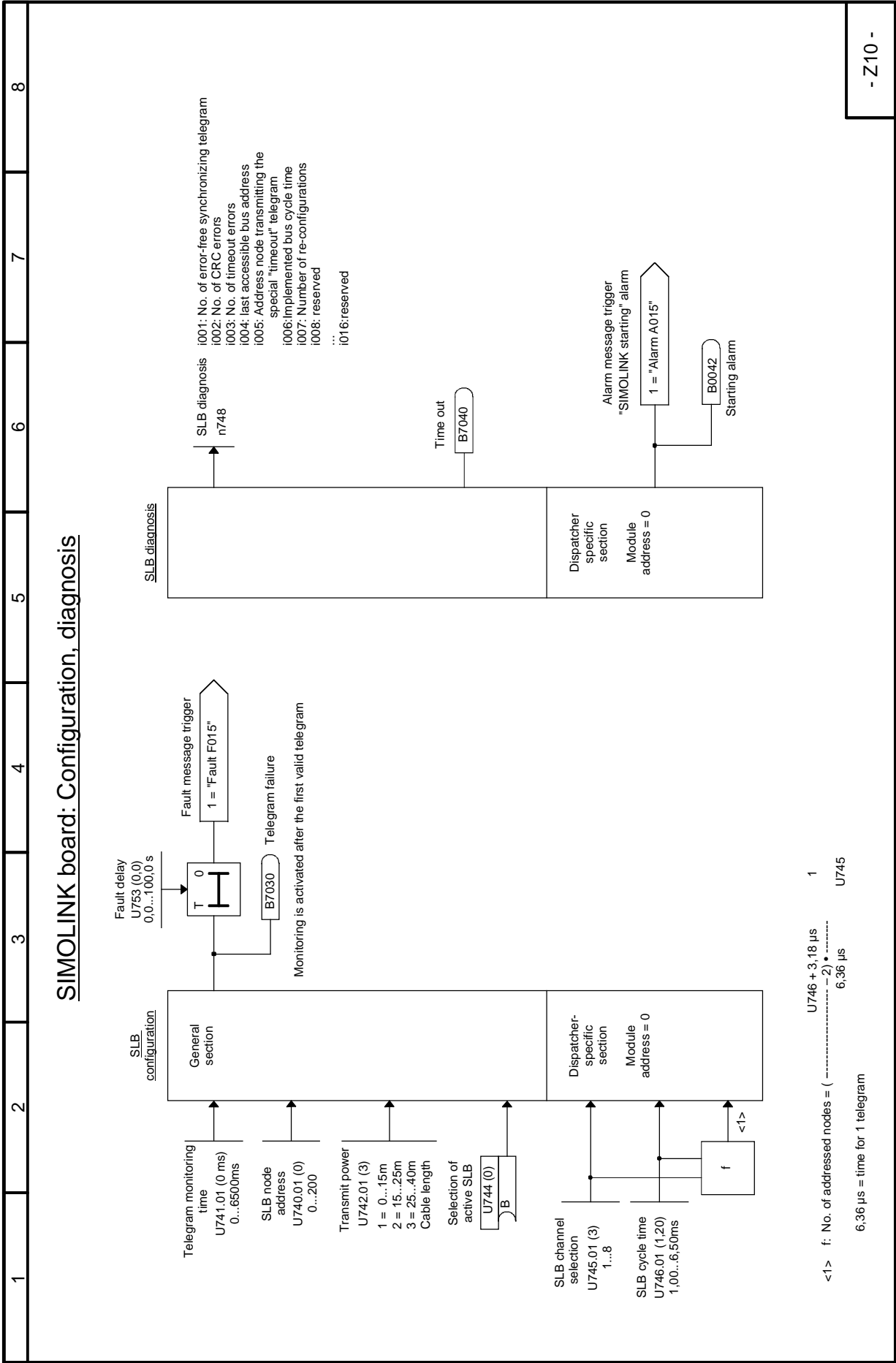Sheet Z10    SIMOLINK board: Configuration, diagnosis




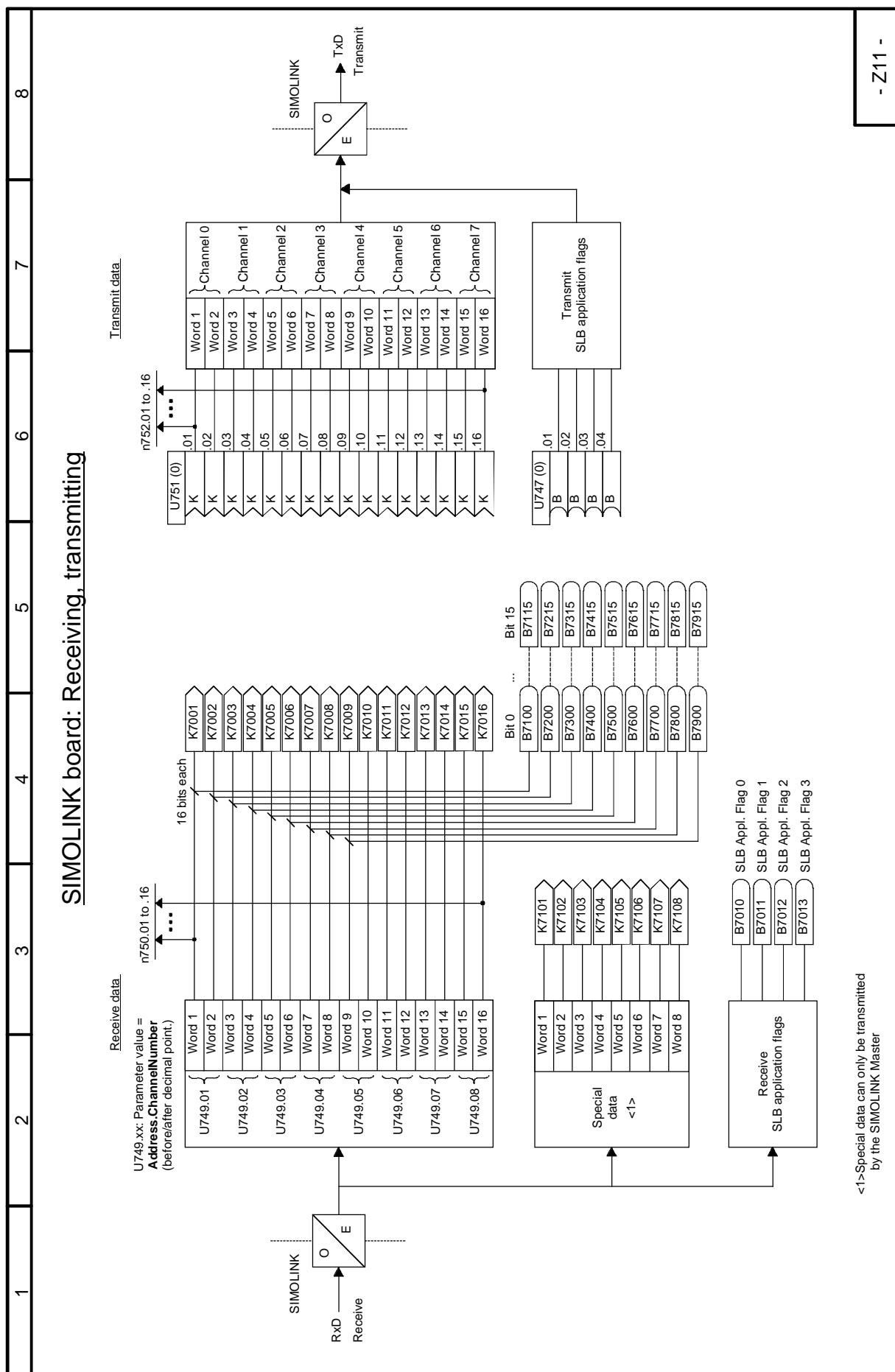
## Sheet Z11 SIMOLINK board: Receiving, transmitting



- Z11 -

Sheet Z12    OP1S operator panel

